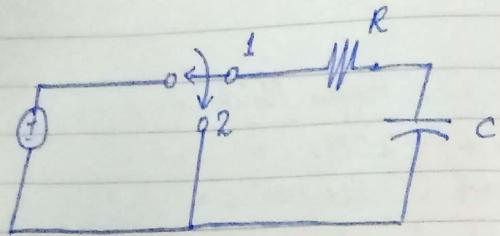


# Source Free RC Circuit Analysis




Case 1:  $t < 0$  (switch at 1)

Case 2:  $t = 0$  (switch is at 2)

Case 3:  $t > 0$  (switch is at 2 for  $t \rightarrow \infty$ )

Source free RC circuit

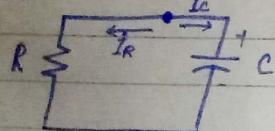

Applying KCL  $i_R + i_C = 0$

$$i_R = -i_C$$

$$\therefore i_C = C \frac{dV_{(t)}}{dt}$$

$$\therefore i_R = \frac{V_{(t)}}{R}$$

$$\frac{V_{(t)}}{R} = -C \frac{dV_{(t)}}{dt}$$

$$-\frac{1}{RC} dt = \frac{1}{V_{(t)}} dV_{(t)}$$

$$\begin{aligned} -\frac{1}{RC} \int_0^t dt &= \int_{V_0}^{V_{(t)}} \frac{1}{V_{(t)}} dV_{(t)} \\ -\frac{t}{RC} \Big|_0^t &= \ln V_{(t)} \Big|_{V_0}^{V_{(t)}} \end{aligned}$$

$$-\frac{t}{RC} = \ln V_{(t)} - \ln V_0$$

$$-\frac{t}{RC} = \ln \left( \frac{V_{(t)}}{V_0} \right)$$


Applying Anti-log.

$$e^{-\frac{t}{RC}} = \frac{V_{(t)}}{V_0}$$

$$V_{(t)} = V_0 e^{-\frac{t}{RC}} \rightarrow @ \quad \text{without any source}$$

L, Natural Response or external excitation

Plotting graph b/w  $V_{(t)}$  and  $t$

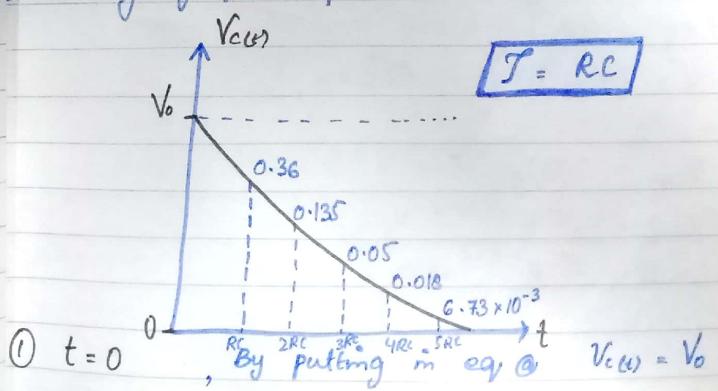


$$\textcircled{1} \quad t = 0$$

$$\text{By putting in eq. @} \quad V_{(t)} = V_0 e^{-\frac{t}{RC}}$$

$$\begin{array}{l} \textcircled{2} \quad t = RC \quad \textcircled{3} \quad t = 2RC \quad \textcircled{4} \quad t = 3RC \quad \textcircled{5} \quad t = 4RC \\ \textcircled{6} \quad t = 5RC \end{array}$$

Problem 7.1.

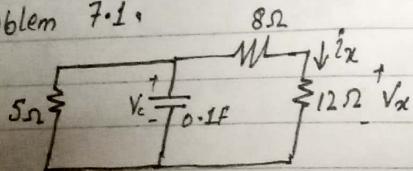

Let  $V_c(0) = 15V$ . Find  $V_c$ ,  $V_x$  and  $i_x$  for  $t > 0$ .

Solution.

$$T = RC$$

$$T = R_{eq} C$$

$$R_{eq} = (8 + 12) \parallel 5$$

$$R_{eq} = (20) \parallel (5)$$

$$R_{eq} = \frac{1}{\frac{1}{20} + \frac{1}{5}} = \frac{1}{\frac{1}{5} + \frac{1}{20}} = \frac{20}{8} = 2.5 \Omega$$

$$R_{eq} = 4 \Omega$$

$$T = (4)(0.1) = 0.4 \text{ sec}$$

Now

$$V_{c(t)} = V(0)e^{-t/4}$$

$$V_{c(t)} = 15e^{-t/0.4} \text{ V}$$

$$[V_{c(t)} = 15e^{-2.5t} \text{ Volts.}]$$

(3)

$$\begin{array}{l} V_c(t) \\ V_c(0) \\ V_c(t) \end{array}$$

(4)

$$\begin{array}{l} V_x(t) \\ V_x(0) \\ V_x(t) \end{array}$$

4

Now for  $V_x$ .  
By voltage division rule

$$V_x = \frac{12}{(12+8)} \times V_c(t)$$

$$V_x = \frac{12}{20} \times 15 e^{-2.5t}$$

$$[V_x = 9e^{-2.5t} \text{ Volts.}]$$


Now for  $i_x$ .

$$i_x = \frac{V_x}{R} = \frac{9e^{-2.5t}}{12}$$

$$[i_x = 0.75e^{-2.5t} \text{ Amps.}]$$

Ans

Problem 7.1 a (Practice Question) a

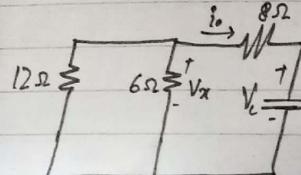

Let  $V_c(0) = 30V$   
Find  $V_{c(t)}$ ,  $V_x$  and  $i_o$   
 $t > 0$

Solution.

$$R_{eq} = (12 \Omega \parallel 6 \Omega) + 8 \Omega$$

$$R_{eq} = \left( \frac{1}{12} + \frac{1}{6} \right) + 8$$

$$R_{eq} = (4) + (8) = 12 \Omega$$

$$T = RC = (12)(\frac{1}{3}) = 4 \text{ sec}$$

Now

$$V_{c(t)} = V(0)e^{-t/4} = 30e^{-t/4}$$

$$[V_{c(t)} = 30e^{-0.25t} \text{ Volts.}]$$

For  $V_2$

Applying voltage divider rule.

$$V_2 = \left(\frac{4}{12}\right) V_{C(0)}$$

$$V_2 = \left(\frac{1}{3}\right) 30 e^{-0.25t}$$

34)

$$V_2 = 10 e^{-0.25t}$$

Now for  $i_1$

As  $4\Omega$  and  $8\Omega$  are in series so the current through them

is equal. Therefore

$$i_1 = V_2 = \frac{10}{e^{-0.25t}}$$

$$i_1 = 2.5 e^{-0.25t}$$

Ans

For  $V_2$


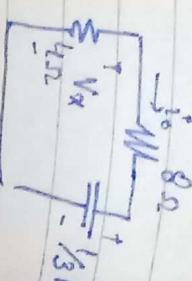



Fig 0

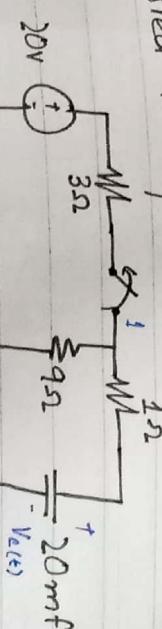Example 7.8  
The switch in the circuit has been closed for a long time and it is opened at  $t=0$ . Find  $V_{C(t)}$  for  $t \geq 0$ . Calculate initial energy stored in capacitor.




For  $V_C(0)$ : When  $t < 0$

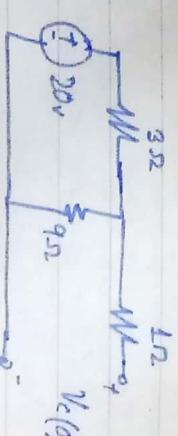By voltage divider rule  
 $V_C(0) = \left(\frac{9}{9+3}\right) \times 20$



$V_C(0) = 15$  Volts.

Now for  $V_C$ ,  $t > 0$

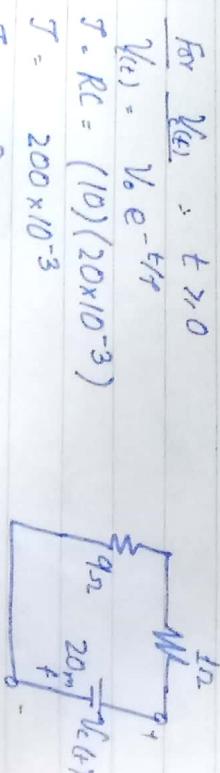

$V_C(t) = V_0 e^{-\frac{t}{RC}}$

$$T \cdot RC = (10)(20 \times 10^{-3})$$

$$T = 200 \times 10^{-3}$$

$$T = 0.2 \text{ sec}$$

$$V_C(t) = 15 e^{-\frac{t}{0.2}} \text{ Volts}$$

$$V_C(t) = 15 e^{-5t} \text{ Volts.}$$


Now for energy stored in capacitor initially.

$$E_C(0) = \frac{1}{2} C V_C(0)^2 = \frac{1}{2} (20 \times 10^{-3})(15)^2$$

$$E_C(0) = 2.25 J$$

Ans

Pratice Questions :

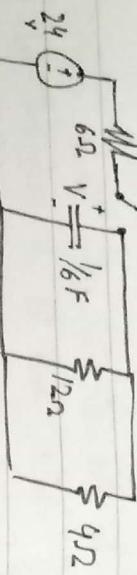

If the switch open at  $t=0$  find  $V_C(t)$  for  $t \geq 0$  and  $V_L(0)$ .


$$V_L(0) = \frac{1}{2} C (V_L(0))^2 = \left(\frac{1}{2}\right)\left(\frac{1}{6}\right)(8)^2$$

$$V_L(0) = \frac{64}{12}$$


$$V_L(0) = 5.33 J$$

Ans .

Solution :  
For  $V_L(0)$ .

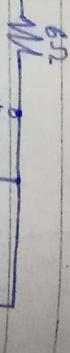

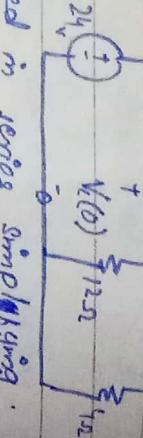By voltage divider  
By as voltage divider can be applied in series simplifying circuit



$$V_C(0) = \frac{3}{6+3} \times 24 = \frac{3}{9} \times 24 = 8 V$$

$V_C(0) = 8$  volts

Now  $V_C(t)$ :

$$V_C(t) = V_C(0) e^{-t/RC}$$

$$T = RC = \frac{1}{12 \times 4} = \frac{1}{48} \text{ sec}$$

$$Req = 3\Omega$$

$$T = (3)(\frac{1}{12}) = 0.25 \text{ sec} \text{ gives}$$

$$V_C(t) = 8 e^{-t/0.25} = V_{C(t)} = 8 e^{-4t}$$

(10)



f

gno.

Determine

Response at  $t > 0$   
Applying KVL assume that

$$\frac{V_{(t)} - V_s}{V_0 - V_s} = e^{-\frac{t}{RC}}$$

$$t=0 \quad V(0) = V_0 \quad , \quad V(t) \text{ at } t > 0$$

$$-V_s + iR + V = 0$$

$$-V_s + RC \frac{dV}{dt} + V = 0 \quad \therefore \quad \ddot{V} = \dot{V}_c = C \frac{dV}{dt}$$

$$RC \frac{dV}{dt} = V_s - V$$

$$RC \frac{dV}{dt} = -(V - V_s)$$

$$\frac{dV}{V - V_s} = -\frac{1}{RC} dt$$

Applying integral.

$$\int_{V_0}^{V(t)} \frac{dV}{V - V_s} = - \int_0^t -\frac{1}{RC} dt$$

$$\ln \frac{V(t)}{V_0 - V_s} = -\frac{t}{RC} \Big|_0^t$$

$$\ln [V(t) - V_s] - \ln [V_0 - V_s] = -\frac{t}{RC}$$

$$\ln \left[ \frac{V(t) - V_s}{V_0 - V_s} \right] = -\frac{t}{RC}$$

Applying Analog

$$\frac{V_{(t)} - V_s}{V_0 - V_s}$$

$$\frac{V_{(t)} - V_s}{V_0 - V_s} = \frac{V_0 - V_s}{V_0 - V_s} e^{-\frac{t}{RC}}$$

Steady state  
response

The steady state response is the behavior of the circuit  
 $t \rightarrow \infty$  response is the behavior of the circuit  
for every long time

Transient Response.

for every short time  
it's a temporary response  
that will die out with time.

→ Complete  
Response


$$V_{(t)} = V_0 e^{-\frac{t}{RC}} + V_s [1 - e^{-\frac{t}{RC}}]$$

Natural Response  
Without any source  
or excitation

Forced Resistor  
Response with some  
excitation source.

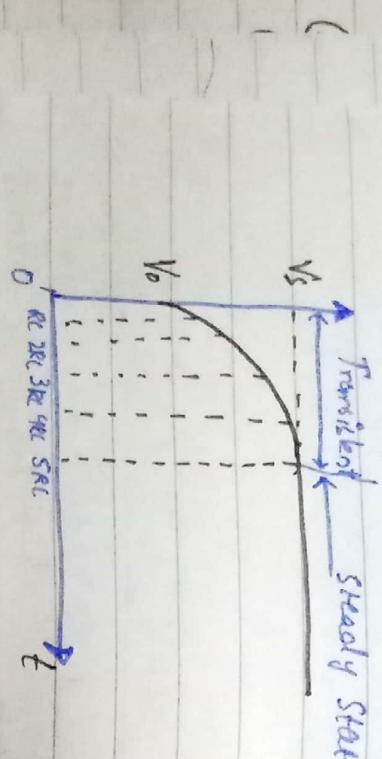(11)

For  $V_0 > 0$  any more initially charged  
when capacitor is initially charged.




$$u(t) = \begin{cases} 1 & t \geq 0 \\ 0 & t < 0 \end{cases} \quad \text{Unit Step}$$

$$\begin{aligned} \text{Unit}^{\text{st}} \\ \text{Impulse} \end{aligned} \quad \delta(t) = \begin{cases} 1 & t=0 \\ 0 & \text{other value of } t \end{cases}$$

$$\begin{aligned} \text{Unit Ramp} \\ \text{Step Input graph} \end{aligned} \quad r(t) = \begin{cases} t & t \geq 0 \\ 0 & t < 0 \end{cases}$$

$$V_0 = 1, \quad RC = 1, \quad V_s = 10$$
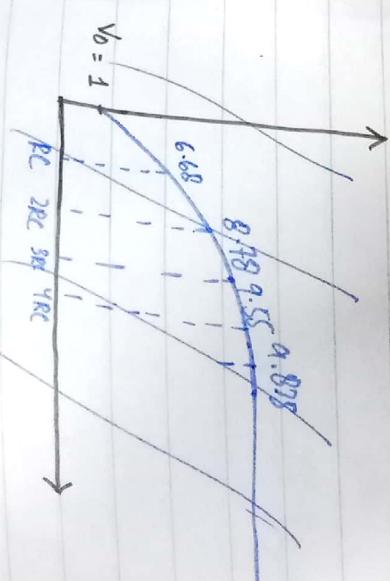
$$\begin{array}{l} \text{Ramp Input: } r(t) \\ \text{Step Input: } u(t) \end{array}$$





(12)

(1/3)

f

(1/4)

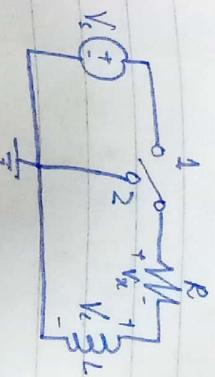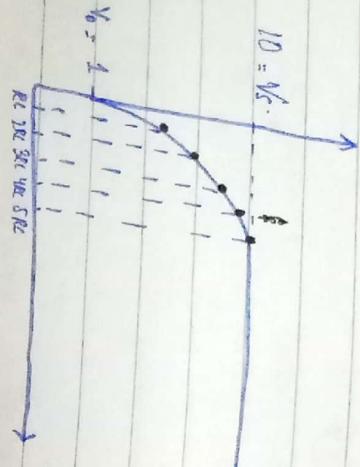Topic - Source Free Response of RC Network



Let assume that inductor of 'L' Henry, is attached with resistor 'R', and the after  $t=0$  the switch contact moved towards '2' position and inductor discharges

- At  $t = 1$   $V_{(t)} = 6.68$
- At  $t = 2$   $V_{(t)} = 8.78$
- At  $t = 3$   $V_{(t)} = 9.55$

Applying KVL  
 $V_R + V_L = 0$

$$V_R = iR$$

$$\frac{dV_L}{dt} + iR + L \frac{di}{dt} = 0$$

$$\frac{dV_L}{dt}$$

$$L \frac{di}{dt} = -Ri$$

$$\frac{di}{dt} = -\frac{Ri}{L}$$

$$\frac{di}{i} = -\frac{R}{L} dt$$

$$\int_{I_0}^{i(t)} \frac{di}{i} = -\frac{R}{L} \int_0^t dt$$

(15)

$$\ln(i^o) \Big|_{I_0}^{i(t)} = -\frac{R}{L} t \Big|_0^t$$

$$\ln(i^o) - \ln(I_0) = -\frac{R}{L} t + \frac{R}{L} I_0$$

$$\ln\left(\frac{i^o(t)}{I_0}\right) = -\frac{R}{L} t$$

Applying Antilog

$$i^o(t) = e^{-\frac{R}{L} t}$$

$$I_o = \frac{V_s}{R}$$

$$\begin{aligned} \text{Applying KVL} \\ -V_s + V_R + V_L = 0 \\ -V_s + iR + L \frac{di^o}{dt} = 0 \end{aligned}$$

$$\begin{aligned} i^o(t) &= I_o e^{-\frac{R}{L} t} \\ i(t) &= I_o e^{-\frac{R}{L} t} \end{aligned}$$


Here  $I_o$  is initial current and  $\left(\frac{L}{R}\right)$  is time constant

$$V_L = L \frac{di^o}{dt}$$

inductor oppose change of current  
capacitor oppose change of voltage

$$\begin{aligned} * i_C &\propto \frac{dV}{dt} \\ * V_L &\propto \frac{di^o}{dt} \end{aligned}$$

Source Response Of  $R-L$  Network

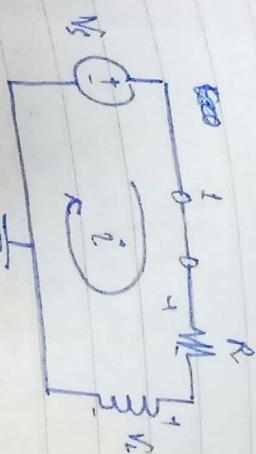

(16)

$$\begin{aligned} \frac{dV_L}{dt} &= \frac{R}{L} (I_s - i^o) \\ \frac{dV_L}{dt} &= -\frac{R}{L} (i^o - I_s) \\ \frac{dV_L}{dt} &= -R \frac{di^o}{dt} \end{aligned}$$

(17)

$$\int_{I_0}^{\hat{i}(t)} \frac{dt}{\hat{i}-I_S} = -\frac{R}{L} \int_{I_0}^t dt$$

$$\ln \left( \frac{\hat{i}(t)}{I_0 - I_S} \right) = -\frac{R}{L} t$$

$$\ln \left( \frac{\hat{i}(t)}{I_0 - I_S} \right) = -\frac{R}{L} t + \frac{R}{L} I_0$$

$$\ln \left( \frac{\hat{i}(t)}{I_0 - I_S} \right) = -\frac{R}{L} t + \frac{R}{L} I_0$$

$$\ln \left( \frac{\hat{i}(t)}{I_0 - I_S} \right) = -\frac{R}{L} t$$

$$\begin{aligned} & \text{Applying Analog} \\ & \frac{\hat{i}(t)}{I_0 - I_S} = e^{-\frac{R}{L} t} \end{aligned}$$

$$\hat{i}(t) = I_S + (I_0 - I_S) e^{-\frac{R}{L} t}$$

$$\hat{i}(t) = I_S + (I_0 - I_S) e^{-\frac{R}{L} t}$$

$$\hat{i}(t) = I_S e^{-\frac{R}{L} t} + I_S (1 - e^{-\frac{R}{L} t})$$

(18)

\* Natural Response part  
 $\hat{i}(t) = I_S e^{-\frac{R}{L} t}$


Forced Response part  
 $\hat{i}(t) = I_S (1 - e^{-\frac{R}{L} t})$

Transient Response part  
 $\hat{i}(t) = (I_0 - I_S) e^{-\frac{R}{L} t}$

Steady state Response part  
 $\hat{i}(t) = I_S$

$$\hat{i}(t)$$



Transient  $\rightarrow$  Steady State

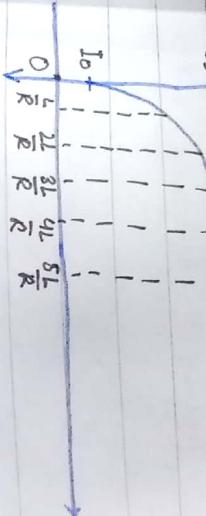

\* For DC Inductors behaves like short  
 and capacitor behaves like open

# Topic :- The Response a.


Q. Problem related to RL circuit.

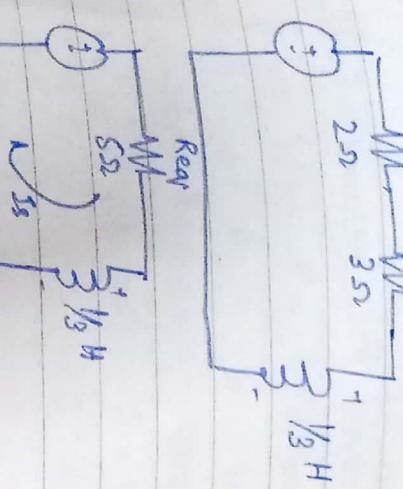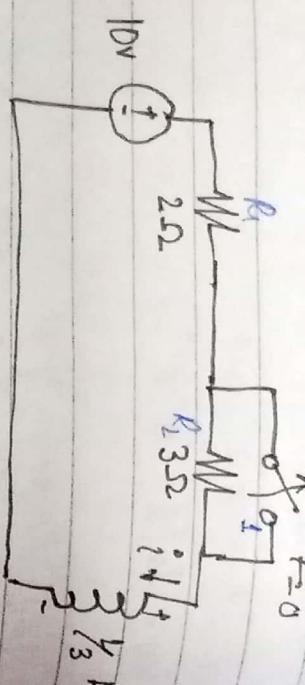

**Step # 01.**


At  $t < 0$ , we can calculate

$I_0$  when switch is at 1

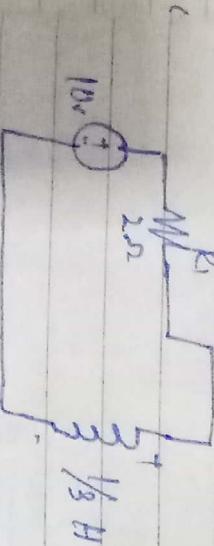

$$i(t) = I_0 e^{-t/(L/R)} + I_s (1 - e^{-t/(L/R)})$$

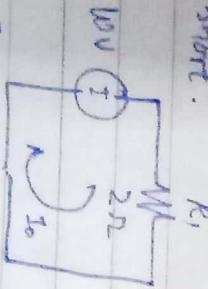After some time inductor behaves like short.



$$i(t) = 5e^{-15t} + 2(1 - e^{-15t})$$

$$i(t) = 5e^{-15t} - R e^{-15t} + 2$$

$$i(t) = 2 + 3e^{-15t}$$

Ans

$$I_0 = \frac{V_s}{R} = \frac{10}{2} = 5$$

$I_0$  = 5amps

Now when switch is open  
 $R_1$        $R_2$   
 $L_1$        $M$   
 $M$        $3\Omega$

## TOPIC :- RLC Response

Let assume that RLC network having inductor and capacitor with initial value of voltages at  $V_0$  &  $I_0$  the voltage of capacitor ~~across~~ current through inductor at  $t = 0$ . Now Applying KVL

$$iR + V_L + V_C = 0$$

$$iR + L \frac{di}{dt} + \frac{1}{C} \int i^0 dt = 0$$

$$\boxed{\frac{d^2 i^0}{dt^2} + \frac{R}{L} \frac{di^0}{dt} + \frac{1}{LC} i^0 = 0}$$

The 2nd order differential equation

Now solution of differential equation

are exponential in nature

Here - expected solutions can be obtained.

by plugging  $i^0 = A e^{st}$  where  $A$  &  $s$

$$\begin{aligned} \text{are constant } & \Rightarrow e^{st} \left[ \frac{d^2}{dt^2} (A e^{st}) + \frac{R}{L} \frac{d}{dt} (A e^{st}) + \frac{1}{LC} (A e^{st}) \right] \\ & \frac{d^2}{dt^2} (A e^{st}) + \frac{R}{L} \frac{d}{dt} (A e^{st}) + \frac{1}{LC} (A e^{st}) = 0 \end{aligned}$$

$$A e^{st} \left( s^2 + \frac{R}{L} s + \frac{1}{LC} \right) = 0$$

$$A e^{st} = 0$$

~~Ans~~ =

$$\frac{di^0}{dt} + \frac{R}{L} i^0 + \frac{1}{LC} \int i^0 dt = 0$$

Differentiate again w.r.t  $t$ ,

$$\frac{d}{dt} \left( \frac{di^0}{dt} \right) + \frac{R}{L} \frac{di^0}{dt} + \frac{1}{LC} \frac{d}{dt} \left( \int i^0 dt \right) = 0$$

(22)

$$\boxed{\left[ s^2 + \frac{R}{L} s + \frac{1}{LC} = 0 \right]} \text{ characteristic equation of system.}$$

## Applying Quadratic formula

$$s = \frac{-(R/L) \pm \sqrt{(R/L)^2 - 4(L)(1/\mu_c)}}{2(L)}$$

$$s = \frac{-R}{2L} \pm \frac{\sqrt{(R/L)^2 - 4/\mu_c}}{2}$$

$$s = \frac{-R}{2L} \pm \sqrt{\left(\frac{R}{L}\right)^2 - \frac{4}{\mu_c}}$$

$$s = \frac{-R}{2L} \pm \sqrt{\left(\frac{R}{L}\right)^2 - \left(\frac{4}{\mu_c}\right)^2}$$

$$s = \frac{-R}{2L} \pm \sqrt{\left(\frac{R}{L}\right)^2 - \left(\frac{4}{\mu_c}\right)^2}$$

Let

$$\alpha = \frac{R}{2L}, \quad \omega_0 = \frac{1}{\sqrt{\mu_c}}$$

$$s = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2}$$

$$\begin{aligned} s_1 &= -\alpha + \sqrt{\alpha^2 - \omega_0^2} \\ s_2 &= -\alpha - \sqrt{\alpha^2 - \omega_0^2} \end{aligned}$$

Now here

$s = \alpha$  called the Natural Frequency (Napier)  
 $\alpha$  called undamping Natural frequency (Rod),  
 $\alpha$  called damping factor (frequency Rod),


Decaying of energy  $\rightarrow$  Damping.

# R Source Free RL Circuits

Power

(26)

① Example 7.4.

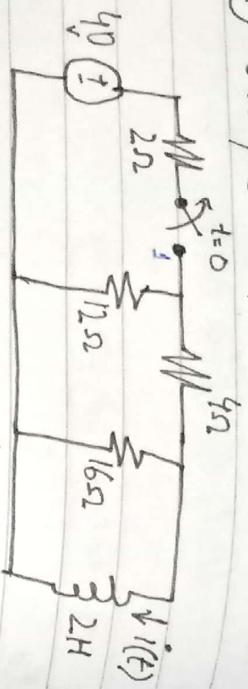


Calculate  $i(t)$  for  $t > 0$

Solution

When  $t < 0$  and switch is at 1

we have circuit

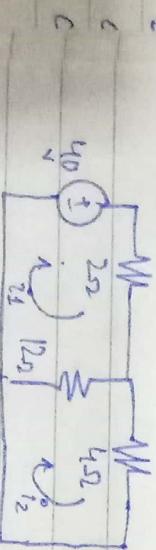

Here after some time inductor behave like short, and current always choose less resistive path therefore

current will always choose short instead of path with 16Ω resistor therefore discarding 16Ω resistor

By mesh analysis.

In mesh 1.

$$-40 + 2i_1 + 12i_2 - 12i_2 = 0$$

$$14i_1 - 12i_2 = 40$$

$$7i_1 - 6i_2 = 20 \rightarrow (1)$$

$$\text{In mesh 2}$$

$$12i_2 - 12i_1 + 4i_2 = 0$$

$$-12i_1 + 16i_2 = 0$$

$$-12 \begin{bmatrix} 7 & -6 \\ 16 & 0 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \end{bmatrix} = \begin{bmatrix} 20 \\ 0 \end{bmatrix}$$

$$(7)(16) - (-6)(-12)$$

$$D = 40$$

$$D = \begin{bmatrix} 20 & -6 \\ 0 & 16 \end{bmatrix} = (20)(16) - (6)(-6)$$

$$D_1 = 320$$

$$D_2 = \begin{bmatrix} 7 & 20 \\ -12 & 0 \end{bmatrix} = (7)(0) - (20)(-12)$$

$$D_2 = 240$$

$$i = \frac{320}{40}, \quad i_2 = \frac{240}{16}$$

$$i_1 = 8 \text{ Amps}$$

$$i_2 = 6 \text{ Amps}$$

The current through inductor is  $i_2 = 6 \text{ Amps}$  and it cannot change instantaneously

$$I_o = i(0) = i_2$$

$$I_o = 6 \text{ Amps.}$$

(27)

New when  $t > 0$  and switch is open

we have circuit


$$R_{eq} = (12 + 4) // 16$$

$$R_{eq} = (16) // (16)$$

$$R_{eq} = 8\Omega$$

New time constant

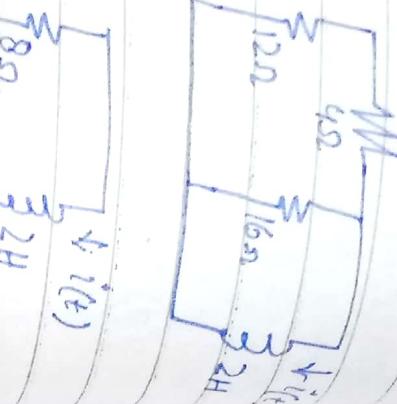
$$T = \left(\frac{L}{R}\right) = \frac{2}{8\Omega} = \frac{1}{4} \text{ s}$$



$$i(t) = I_0 e^{-t/T} = 6 e^{-t/4\Omega}$$

$$i(t) = 6 e^{-4t} \text{ Amps.}$$

7.4 practice problems.

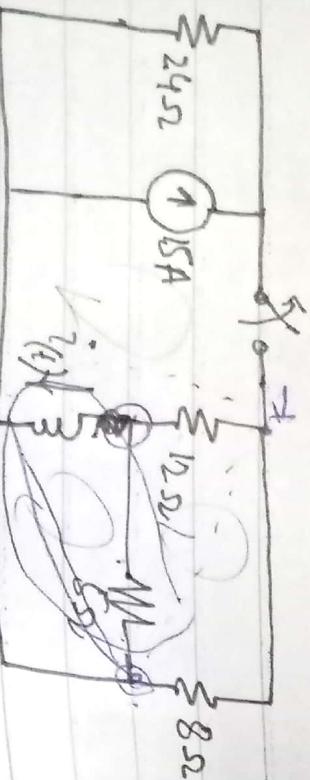

# Topic: SOURCE RLC Circuit

## Free Response of Series

(28)

$$S_1, S_2 = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2}$$

$$S^2 + \frac{R}{L}S + \frac{1}{LC} = 0$$

Characteristic Equation of System.  
Depending on Nature of Root

- (i) If Roots are Real and Unequal.  $|\alpha > \omega_0|$
- (ii) If Roots are Real and equal  $|\alpha = \omega_0|$
- (iii) If roots are Complex.  $|\alpha < \omega_0|$

- (i)  $\alpha > \omega_0$  (this response is called over damped)
- (ii)  $\alpha = \omega_0$  (this response is called critically damped) (Most desirable condition).
- (iii)  $\alpha < \omega_0$  (this response is called under damped)

Case 1: ( $\alpha > \omega_0$ )

$\therefore$  2nd order system must have 2 initial conditions

$$i(t) = A_1 e^{S_1 t} + A_2 e^{S_2 t}$$

$$i(t) = A_1 e^{(-\alpha + \sqrt{\alpha^2 - \omega_0^2})t} + A_2 e^{(-\alpha - \sqrt{\alpha^2 - \omega_0^2})t}$$

$$\stackrel{\text{at } t=0}{=} i(0) = I_0, V_0$$

$$\stackrel{\text{and at } t=0}{=} \frac{di(0)}{dt} = -\frac{1}{L}(RI_0 + V_0)$$

$$i(t) = A_1 e^{-\alpha t} e^{(\sqrt{\alpha^2 - \omega_0^2})t}$$

$$i(t) = e^{-\alpha t} [A_1 e^{(\sqrt{\alpha^2 - \omega_0^2})t} + A_2 e^{(-\sqrt{\alpha^2 - \omega_0^2})t}]$$

(34)

ye parallel sat  
agy pula

Karna kauf idr

Case 3rd ( $d < \omega_0$ )

Now

putting  $R$ 

$$d = \frac{R}{2L}$$

,  $\omega_0 = \frac{1}{\sqrt{LC}}$ 

$$S_1, S_2 = -d \pm \sqrt{\omega_0^2 - d^2}$$

$$S_1, S_2 = -d \pm \sqrt{-1} \left( \omega_0^2 - d^2 \right)$$

$$S_1, S_2 = -d \pm j \sqrt{\omega_0^2 - d^2}$$

$$\text{Ad} = \sqrt{\omega_0^2 - d^2}$$

called ~~damping~~  
damp Natural freq.

$$\frac{di^o}{dt^2} + 2d \frac{di^o}{dt} + \omega_0^2 i^o = 0$$

$$\frac{di^o}{dt^2} + 2d \frac{di^o}{dt} + d^2 i^o = 0$$

so  $d = \omega_0$ 

$$\text{Ad} = \sqrt{\omega_0^2 - d^2}$$

all values in eqn (1)

$$\frac{di^o}{dt^2} + 2d \frac{di^o}{dt} + \omega_0^2 i^o = 0$$

$$\frac{di^o}{dt^2} + 2d \frac{di^o}{dt} + d^2 i^o = 0$$

so  $d = \omega_0$ CASE 2ND e. ( $d = \omega_0$ ) critical damping

$$S_1, S_2 = -d$$

$$d = \omega_0$$

The equation

$$\frac{di^o}{dt^2} + \frac{R}{L} \frac{di^o}{dt} + \frac{1}{LC} i^o = 0 \rightarrow ①$$

$$\frac{d^2 i^o}{dt^2} + \frac{d}{dt} \frac{di^o}{dt} + \frac{1}{LC} i^o = 0$$

$$\frac{d}{dt} \left( \frac{di^o}{dt} + \frac{1}{LC} i^o \right) + \frac{1}{LC} i^o = 0$$

$$\text{let } f = \frac{di^o}{dt} + \frac{1}{LC} i^o$$

$$\frac{df}{dt} + df = 0$$

Actually

$$i^o(t) = A_1 e^{st} + A_2 e^{s_2 t}$$

$$\text{If we have } S_1 = S_2 = -d$$

$$i^o(t) = A_1 e^{-dt} + A_2 e^{-dt}$$

$i^o(t) = e^{-dt} (A_1 + A_2 e^{-dt})$   
 $i^o(t) = A e^{-dt}$  New equation has single initial condition (single Constant) which is not justify initial term (initial condition).

(31)

Now as the 1st order differential eqn

$$i = Ae^{-\alpha t}$$

$$\frac{di}{dt} + \alpha i = Ae^{-\alpha t}$$

$$e^{\alpha t} \left[ \frac{di}{dt} + \alpha i \right] = A$$

$$\alpha t \cdot di + i \cdot \alpha e^{\alpha t} = A$$

$$\frac{d}{dt}$$

Now we can suppressed if

$$\frac{d}{dt} (i^* \cdot e^{\alpha t}) = A$$


$$\begin{aligned} d(i^* \cdot e^{\alpha t}) &= A dt \\ \int d(i^* \cdot e^{\alpha t}) &= A \int dt \end{aligned}$$

$$i^* \cdot e^{\alpha t} = At + C$$

$$i^* = (At + C) e^{-\alpha t}$$

$$i^* = Ate^{-\alpha t} + Ae^{-\alpha t} -$$

Topic - Parallel RLC  

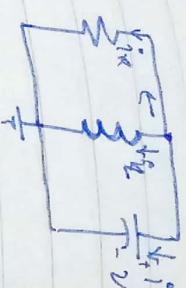

at node 4

$$i_R + i_L + i_C = 0$$

$$\frac{V}{R} + \frac{1}{L} \int V dt + \frac{C}{V} \frac{dV}{dt} = 0$$

$$\frac{dV}{dt} + \frac{V}{RC} + \frac{1}{LC} \int V dt = 0$$

$$\frac{d^2V}{dt^2} + \frac{1}{RC} \frac{dV}{dt} + \frac{1}{LC} V = 0$$

$$\boxed{\frac{d^2V}{dt^2} + \frac{1}{RC} \frac{dV}{dt} + \frac{1}{LC} V = 0}$$

$$V = A \text{est}$$

$$\frac{d^2A_{\text{est}}}{dt^2} + \frac{1}{RC} \frac{dA_{\text{est}}}{dt} + \frac{1}{LC} A_{\text{est}} = 0$$

$$A_{\text{est}}^2 + \frac{1}{RC} A_{\text{est}} + \frac{1}{LC} A_{\text{est}} = 0$$

$$A_{\text{est}} \left( s^2 + \frac{1}{RC} + \frac{1}{LC} \right) = 0$$

Now characteristics equation.

$$s^2 + \frac{1}{RC} + \frac{1}{LC} = 0$$

(33)

By quadratic formula

$$\zeta = \frac{(-\frac{1}{RC}) \pm \sqrt{(\frac{1}{RC})^2 - 4(\frac{1}{L})(\frac{1}{RC})}}{2}$$

$$\zeta = \frac{-1}{2RC} \pm \sqrt{\frac{1}{(RC)^2} - \frac{4}{LC}}$$

$$j(A_1 - A_2) = B_2$$

$$\zeta = \frac{-1}{2RC} \pm \sqrt{\frac{1}{(2RC)^2} - \frac{1}{LC}}$$

$$\zeta = \frac{-1}{2RC} \pm \sqrt{\frac{1}{(2RC)^2} - \frac{1}{LC}}$$

Let:

$$\alpha = \frac{1}{2RC}, \omega = \frac{1}{\sqrt{LC}}$$

$$\zeta = -\alpha \pm \sqrt{\alpha^2 - \omega^2}$$

$$\dot{i}(t) = [A_1 e^{-(\alpha t + j\omega t)} + A_2 e^{-(\alpha t - j\omega t)}] \times e^{-\alpha t}$$

① Case (i) Over damped response  $\alpha > \omega$ 

$$v(t) = A_1 e^{\zeta_1 t} + A_2 e^{\zeta_2 t}$$

② Case (ii) Critically damped response  $\alpha = \omega$ 

$$v(t) = A_1 e^{-\alpha t} + A_2 t e^{-\alpha t}$$

(3) Under damped Response  $\alpha < \omega$ .

$$v(t) = (B_1 \cos \omega t + B_2 \sin \omega t) e^{-\alpha t}$$

From previous

$$(A_1 + A_2) = B_1$$

$$S_1, S_2 = -\alpha \pm j\omega$$

$$\dot{i}(t) = A_1 e^{-(\alpha t + j\omega t)} + A_2 e^{-(\alpha t - j\omega t)}$$

$$\dot{i}(t) = \begin{cases} A_1 e^{(-\alpha t + j\omega t)} \\ A_2 e^{(-\alpha t - j\omega t)} \end{cases}$$

$$\dot{i}(t) = A_1 e^{(-\alpha t + j\omega t)} + A_2 e^{(-\alpha t - j\omega t)}$$


$$\dot{i}(t) = A_1 e^{-\alpha t} e^{j\omega t} + A_2 e^{-\alpha t} e^{-j\omega t}$$

$$\dot{i}(t) = (A_1 e^{j\omega t} + A_2 e^{-j\omega t}) e^{-\alpha t}$$

(34)

(35)

## Topic - Step RESPONSE Of SERIES RLC

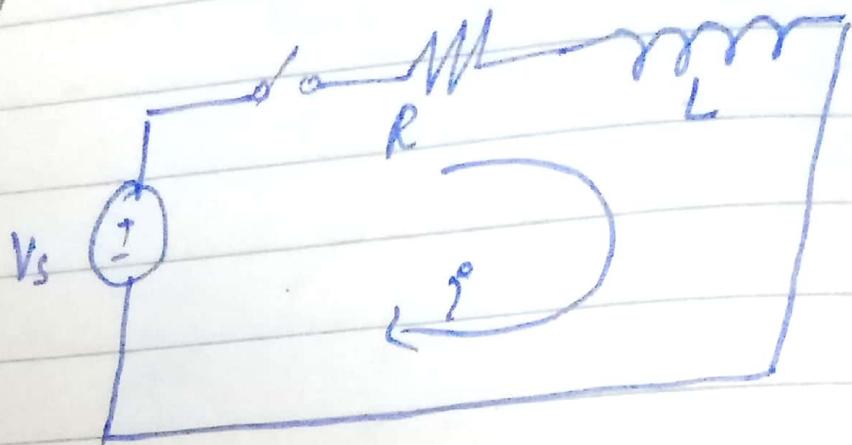

Using KVL -

$$iR + L \frac{di}{dt} + V = V_s$$

$$\therefore i = \frac{cdv}{dt}$$


$$Rc \frac{dv}{dt} + L \frac{d}{dt} \left[ \frac{cdv}{dt} \right] + V = V_s$$

$$LC \frac{d^2v}{dt^2} + RC \frac{dv}{dt} + V = V_s$$

$$\frac{d^2v}{dt^2} + \frac{R}{L} \frac{dv}{dt} + \frac{V}{LC} = \frac{V_s}{LC}$$

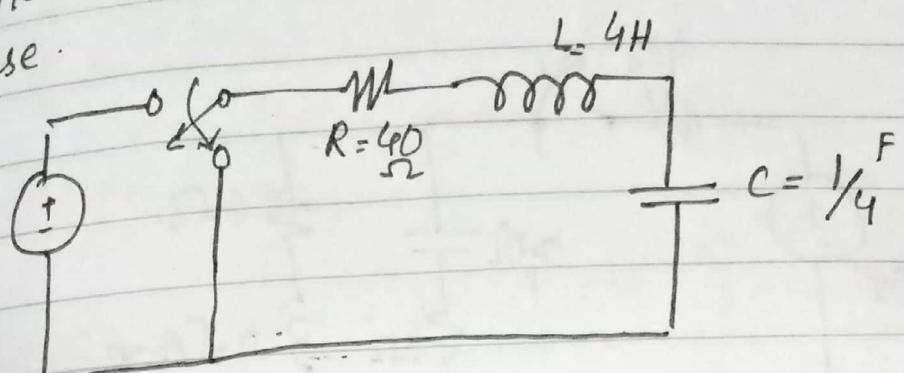(36)

Qe. Determine the characteristics equation of Network show & find roots and nature of Response.



Solution =

$$\alpha = \frac{R}{2L}$$

$$\omega_0 = \frac{1}{\sqrt{LC}}$$

$$\alpha = \frac{40}{2(4)} = 5$$

$$\boxed{\alpha = 5}$$

$$\omega_0 = \frac{1}{\sqrt{(4)(1/4)}} = 1$$

$$\boxed{\omega_0 = 1}$$

$$S_1 = -\alpha + \sqrt{\alpha^2 - \omega_0^2}$$

$$S_2 = -\alpha - \sqrt{\alpha^2 - \omega_0^2}$$

$$S_1 = -5 + \sqrt{(5)^2 - (1)^2} = -5 + \sqrt{25-1}$$

$$\boxed{S_1 = -5 + \sqrt{24}}$$

$$S_2 = -5 - \sqrt{(25)^2 - (1)^2} = -5 - \sqrt{25-1}$$

$$\boxed{S_2 = -5 - \sqrt{24}}$$

As here  $\alpha = 5$  and  $\omega_0 = 1 \Rightarrow \alpha > \omega_0$   
Therefore here is condition of overdamped



(39)

(40)

Now the Response -

$$\begin{aligned} i(t) &= e^{-qt} (A_1 \cos \omega t + A_2 \sin \omega t) \\ i(t) &= e^{-qt} (A_1 \cos 4.359t + A_2 \sin 4.359t) \end{aligned}$$

Now we need to determine  $A_1$  &  $A_2$  for complete solution.

$$\frac{di(t)}{dt} = -qA_1 + 4.359A_2 \quad \text{Now at } t=0 \quad \frac{di(0)}{dt} = -q(A_1(1) + A_2(0)) + (-4.359A_1(0) + 4.359A_2(1))$$

$$i(t) = e^{-qt} (A_1 \cos 4.359t + A_2 \sin 4.359t) \rightarrow$$

$$\text{as } t=0$$

$$i(0) = e^{-q(0)} (A_1 \cos 4.359(0) + A_2 \sin 4.359(0))$$

$$i(0) = (1) [A_1(1) + A_2(0)]$$

$$i(0) = A_1$$

$$\therefore i(0) = I_0 = 1 \text{ Amps}$$

$$[A_1 = 1]$$

Now the second Condition can be obtain by differentiating Eq①.

$$\frac{d}{dt} i(t) = \frac{d}{dt} [e^{-qt} (R \cos 4.359t + L \sin 4.359t)]$$

$$\frac{di(t)}{dt} = \frac{1}{L} [V - iR]$$

$$\text{Now at } t=0$$

$$\frac{di(0)}{dt} = \frac{1}{L} [V(0) - i(0)R]$$

$$\frac{di(0)}{dt} = \frac{1}{L} [V_0 - I_0 R]$$

$$\frac{di(0)}{dt} = \frac{1}{L} [6 - (1)(4)]$$

$$\frac{d}{dt} i(t) = -9e^{-qt} (A_1 \cos 4.359t + A_2 \sin 4.359t)$$

$$+ (-4.359A_1 \sin 4.359t + 4.359A_2 \cos 4.359t)$$

$$\frac{di(t)}{dt} = \frac{-3}{\mu_2} = -6$$

$$\text{Now putting value in eq ①}$$

$$-6 = -9A_1 + 4.359A_2$$

(41)

$$-6 = -9 + 4 \cdot 359 A_2$$

$$\boxed{A_2 = 0.688}$$

Now,

$$i(t) = e^{-9t} (\cos 4.359t + 0.688 \sin 4.359t)$$

Ans

Now  $S_1$  and  $S_2$

$$S_1, S_2 = -\alpha \pm \sqrt{\alpha^2 - (\omega_0)^2}$$

$$S_1, S_2 = -26 \pm \sqrt{(26)^2 - (10)^2}$$


$$S_1, S_2 = -26 \pm \sqrt{576}$$

$$S_1, S_2 = -26 \pm 24$$

$$S_1 = -2, \quad S_2 = -50$$

$\Rightarrow$  Response is overdamped because  $\alpha > \omega_0$ .

Q. Determine Response for Parallel RLC  
in the following condition.

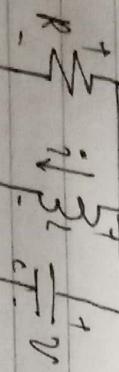where  $i(0) = 0$ ,  $v(0) = 5V$ ,  $L = 1H$ 

$$C = 10mF, \quad R = 1.0923 \Omega$$

$$\textcircled{a} R = 5\Omega, \quad \textcircled{b} R = 6.25\Omega$$

Solution:for  $t = 0$ 

$$d = \frac{1}{2RC} = \frac{1}{2(1.0923)(10 \times 10^{-3})}$$

$$d = 26$$

$$\omega_0 = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{15}(10m)^2} = 10$$

Applying KVL

$$\dot{i} + \dot{i}_L + \dot{i}_C = 0$$

$$v + \dot{i}_L + \frac{C \dot{v}}{R} = 0$$

$$C \frac{dv}{dt} = -\left(\dot{i} + \frac{v}{R}\right)$$

$$\frac{dv}{dt} = -\frac{1}{C} \left(\dot{i} + \frac{v}{R}\right)$$

for  $t = 0$ 

$$d = \frac{1}{2RC} = \frac{1}{2(1.0923)(10 \times 10^{-3})}$$

$$\frac{dv(0)}{dt} = -\frac{1}{C} \left(i(0) + \frac{v(0)}{R}\right)$$

$$\frac{dv(0)}{dt} = -\frac{1}{C} \left(10 + \frac{5}{1.0923 \times 10 \times 10^{-3}}\right) =$$

$$\frac{dV(t)}{dt} = -260 \cdot 0.01$$

$$\frac{dI}{dt}$$

for  $t = 0$

$$V(0) = A_1 + A_2 \quad \rightarrow \textcircled{1}$$

$$15 = A_1 + A_2$$

Now for second condition.

$$\frac{dV(t)}{dt} = \frac{d}{dt}(A_1 e^{-2t} + A_2 e^{-50t})$$

$$\frac{dV(t)}{dt} = -2A_1 e^{-2t} - 50A_2 e^{-50t}$$

$$\frac{dI}{dt}$$

for  $t = 0$

$$\frac{dV(t)}{dt} = -2A_1 - 50A_2$$

$$1 - 260 = -2A_1 - 50A_2 \quad \rightarrow \textcircled{2}$$

Solving Eq ① & ② we have

$$A_1 = 5 - A_2$$

$$\text{put in eq ②}$$

$$-260 = -2(5 - A_2) - 50A_2$$

$$-260 = -10 + 2A_2 - 50A_2$$

$$=$$

$$-250 = -48A_2$$

$$A_2 = \underline{-\frac{250}{48}}$$

$$P_2 = 5 \cdot 2$$

$$V(t) = A_1 e^{5t} + A_2 e^{-50t}$$

$$V(t) = -0.2 e^{-2t} + 5.2 e^{-50t}$$

Ans.

Topic - AC Circuit e-

$$V(t) = V_m \sin(\omega t + \phi) \quad \text{OR} \quad V(t) = V_m \cos(\omega t + \phi)$$


$V(t)$ :

$V(t)$  is instantaneous values of voltage.

$V_m$  is the maximum values of voltage  
 $\omega$  is the angular frequency of sinusoid

$\phi$  is the angular phase shift.

$$V(t) = V_m \sin(\omega t)$$

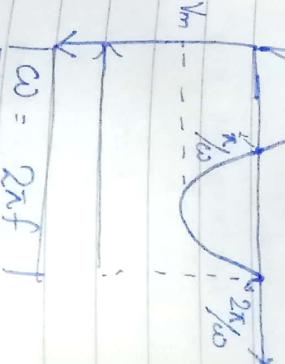

(45)

(46) 48

Q:-  
Find the amplitude and frequency of  
Signal when

$$V(t) = 20 \sin(2\pi 211t + 20)$$

Sol:-  
 $V(t) = V_m \sin(\omega t + \phi)$

here

By comparing given eq we have

$$V_m = 20 \rightarrow \text{Amplitude.}$$

$$\omega = 211 \rightarrow \text{Angular Frequency.}$$

$$\phi = 20 \rightarrow \text{Angular Phase Shift}$$

$$\omega = 2\pi f$$

$$f = \frac{\omega}{2\pi} = \frac{211}{2\pi}$$

$$f = 33.58 \text{ Hz}$$

$$V(t) = V_m \cos(\omega t + \phi) \quad \rightarrow \text{Time domain}$$

Now,  
 $V(t) = V_m R e^{j(\omega t + \phi)}$

$$V(t) = V_m R e^{j\phi} e^{j\omega t}$$

$$V(t) = R(V_m e^{j\phi}) \cdot (e^{j\omega t})$$

$e^{j\omega t}$  we suppressed time part

$$V(t) = R V_m e^{j\phi}$$

$$V(t) = V_m e^{j\phi}$$



$$\frac{V}{V_m} = V_m e^{j\phi}$$

$\Rightarrow$  PHASOR DOMAIN.

Phasor is a complex number that represents the amplitude and phase of the sinusoidal.

$$Z = x + jy \quad \text{Rectangular form}$$

$$Z = r \angle \phi \quad \text{Polar form}$$

$$Z = r e^{j\phi} \quad \text{Exponential form}$$

## Topic - Description of AC (RC & RL)

### • Phase Relation in passive devices

$$\begin{aligned} \text{For } R: V = I \cdot R \\ \text{For } \text{RL: } V = I \left( j\omega L \right) \end{aligned}$$

$$V = I X_L \quad \boxed{V = I \frac{1}{j\omega C}}$$

$$V = I X_C \quad \boxed{V = I \frac{1}{j\omega C}}$$

IMPEDANCE -

The overall effect of Resistance and Reactance in the flow of current

$$Z = R + jX$$

$R$  = Resistance (independent of frequency of signal)

$X$  = Reactance (depends on frequency of signal) also (Nature of device Inductance or Capacitance).

$$\begin{aligned} \text{Inductive Reactance} &= X_L \\ \text{Capacitive Reactance} &= X_C \end{aligned}$$

As we know that

$$V = L \frac{di}{dt}$$

$$i = I \cos(\omega t + \phi)$$

$$V = I \omega L \left[ \cos(\omega t + \phi) \right]$$

$$V = I \omega C \left[ \cos(\omega t + \phi + 90^\circ) \right]$$

$$V = I \omega C R e^{j\omega t} e^{j\phi} e^{j90^\circ}$$

$$V = I \omega C R e^{j\omega t} e^{j\phi} e^{j90^\circ}$$

In phasor domain

$$V = I \omega L \angle \phi + 90^\circ$$

$$X_L = j\omega L \quad j\omega L = |X_L| \angle 90^\circ$$

$$X_C = \frac{1}{j\omega C} \Rightarrow |X_C| \angle -90^\circ$$

(49)

Determine Impedance, Total current across each element and voltage phasor diagram

$$\bar{Z} = ? \quad \bar{\frac{V_R}{I}} = ? \quad \bar{\frac{V_L}{I}} = ?$$

$$10 \cos(\omega t + \phi) \quad \text{v} \quad \frac{V_R}{S_2} \quad \bar{I}$$

$$C = 0.01 F$$

Solution,

we have

$$V_S = 10 \cos(\omega t + 0^\circ) \Rightarrow 10 \cos(\omega t + 0^\circ)$$

In phasor domain

$$\bar{V}_S = 10 \angle 0^\circ$$

Let;

$$\bar{Z}_1 = R \quad \bar{Z}_2 = X_C$$

$$\bar{Z} = \bar{Z}_1 + \bar{Z}_2$$

$$X_C = \frac{1}{j\omega C}$$

$$\omega = 4$$

$$C = 0.01 F$$

$$\left[ \begin{array}{l} \frac{X_C}{X_C} = -j2.5 \\ \frac{X_C}{X_C} = 2.5 \end{array} \right] \quad |X_C| = \sqrt{(2.5)^2 + 2.5^2} = \sqrt{50} = 5 \Omega$$

$$\phi = \tan^{-1}\left(\frac{\text{Imaginary}}{\text{Real}}\right) = 90^\circ$$

$$\phi = -90^\circ$$

$$\boxed{\bar{Z} = 5 - j2.5 \Omega}$$

we know that

$$\bar{Z} = |Z| / \phi_2 \rightarrow \textcircled{1}$$

$$|Z| = \sqrt{(5)^2 + (2.5)^2}$$

$$|Z| = 5.59 \Omega$$

Imaginary part

$$\phi_2 = \tan^{-1}\left(\frac{\text{Imaginary}}{\text{Real}}\right) = \tan^{-1}\left(\frac{-2.5}{5}\right)$$

$$\phi_2 = -26.5^\circ$$

$$\text{putting in eqn } \textcircled{1} \quad \bar{Z} = 5.59 \angle -26.5^\circ \Omega$$

By ohm's law

$$V = IZ$$

$$I = \frac{V}{Z} = \frac{10 \angle 0^\circ}{5.59 \angle -26.5^\circ}$$

$$\therefore n_1 L \phi_1 \times n_2 L \phi_2 = n_1 \times n_2 \angle (\phi_1 + \phi_2)$$

$$\frac{n_1 L \phi_1}{n_2 L \phi_2} = \frac{n_1}{n_2} \angle (\phi_1 - \phi_2)$$

$$I = \frac{10}{5.59} \angle 0^\circ - (-26.5^\circ)$$

As we have series circuit.

## AC Analysis of ~~RLC~~ circuit

$$\begin{aligned} \text{Voltage across resistor } V_R \\ \bar{V}_R &= \frac{VR}{I} \\ \bar{V}_R &= (1.79 \angle 26.5^\circ)(5 \angle 20^\circ) \\ \boxed{\bar{V}_R = 8.95 \angle 26.5^\circ \text{ V}} \end{aligned}$$

Voltage across capacitor  $\bar{V}_C$



$$\begin{aligned} \bar{V}_C &= \frac{V_C}{I} X_C \\ \bar{V}_C &= (1.79 \angle 26.5^\circ)(2.5 \angle -90^\circ) \end{aligned}$$

$$\boxed{\bar{V}_C = 4.47 \angle -63.5^\circ \text{ V}}$$

X-axis  $\rightarrow$  Real  
Y-axis  $\rightarrow$  Imaginary

phasor diagram:

Diagram:

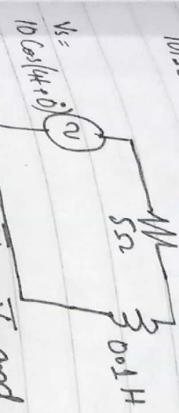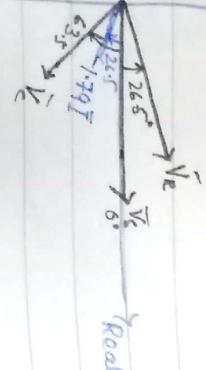

Determine phasor diagram.  
Draw we have

$$V_s = 10 \cos(4t + 0^\circ)$$

In phasor domain

$$\bar{V}_s = 10 \angle 0^\circ$$

$$X_L = j\omega L$$

$$X_L = j4(0.1)$$

$$X_L = 0.4j \Omega$$

$$|X_L| = 0.4 \Omega$$

$$\phi_2 = \tan^{-1}(4/4) = \tan^{-1}(1)$$

$$\phi_2 = 45^\circ$$

$$Z = R + jX_L$$

$$V_s = 10 \angle 0^\circ$$

$$Z = 5 + 0.4j$$

$$|Z| = 5.01$$

$$\phi = \tan^{-1}(0.4/5)$$

$$\phi = 4.57^\circ$$

$$\boxed{\frac{V_s}{Z} = 5.01 \angle 4.57^\circ}$$


$$\begin{aligned} I &= \frac{V_s}{Z} = \frac{10 \angle 0^\circ}{5.01 \angle 4.57^\circ} \\ I &= 1.99 \angle -4.57^\circ \end{aligned}$$

(53)

$$\begin{aligned}\bar{V}_R &= \bar{I} \bar{R} \\ \bar{V}_R &= ((1.099) L^{-45.7^\circ}) (5 L 0^\circ) \\ \bar{V}_R &= 9.95 L^{-45.7^\circ}\end{aligned}$$

$$\bar{V}_L = \bar{I} \bar{X}_L$$
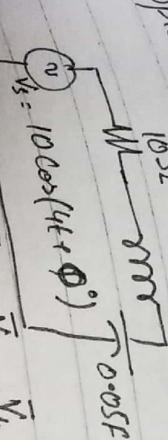
$$\begin{aligned}\bar{V}_L &= (1.099 L^{-45.7^\circ})(0.4 L 90^\circ) \\ \bar{V}_L &= 0.796 L^{-85.43^\circ}\end{aligned}$$



Topic :- AC Analysis of RLC circuit  
Determine diagram of current (Lead or Lag)  
Find the relation of current (Source).  
with respect to voltage (Source).

$$\begin{aligned}\text{Sol: } V_s &= 10 \cos(4t + 0^\circ) \\ \bar{V}_s &= 10 L 0^\circ\end{aligned}$$

$$\begin{aligned}Z_1 &= R \\ Z &= Z_1 + Z_2 + Z_3 \quad \rightarrow \quad ① \\ X_L &= j\omega L = 4j \\ |X_L| &= 4\end{aligned}$$


$$X_C = \frac{1}{j\omega C} = \frac{1}{(0.05)(4)} = -5j$$

$$|X_C| = 5$$

$$\begin{aligned}\phi_L &= \tan^{-1}(4/2) = 45^\circ \\ \phi_C &= -90^\circ\end{aligned}$$

(54)

RLC circuit

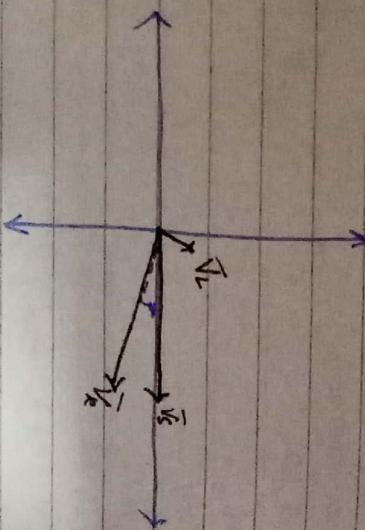

(55)

$$\phi_c = \tan^{-1}(\frac{y}{x}) = \tan^{-1}\left(\frac{-5}{4}\right) = \tan^{-1}(-1.25)$$

$$\bar{V}_L = \bar{I} X_L \\ (0.995)(15.4) (4 L 90^\circ)$$

$$\bar{V}_L = 3.98 L 95.4^\circ \text{ volts}$$

$$X_L = 4 L 90^\circ \\ X_C = -5 L -90^\circ$$

Now putting values in eq ①

$$\bar{Z} = 10 + 4j - 5j$$

$$\bar{Z} = 10 - j$$

$$|Z| = \sqrt{(10)^2 + (1)^2}$$

$$|Z| = 10.04$$

$$\phi_Z = \tan^{-1}(y/x) = \tan^{-1}(-\frac{1}{10})$$

$$\phi_Z = -5.71^\circ$$

$$\bar{Z} = 10.04 L -5.71^\circ$$

$$\bar{I} = \frac{\bar{V}_L}{\bar{Z}} = 10 L 0^\circ$$

$$\bar{I} = 0.995 L 5.71^\circ \text{ Amps}$$

$$\bar{V}_R = \bar{I} \bar{R} = (0.995 L 5.71^\circ)(10 L 0^\circ)$$


$$\bar{V}_R = 9.95 L 5.71^\circ \text{ Volts}$$

(56)


$$\bar{V}_C = \bar{I} X_C \\ (0.995 L 5.71^\circ) (5 L 90^\circ) \\ \bar{V}_C = 4.975 L -84.29^\circ \text{ Volts}$$

In inductor current will always lag

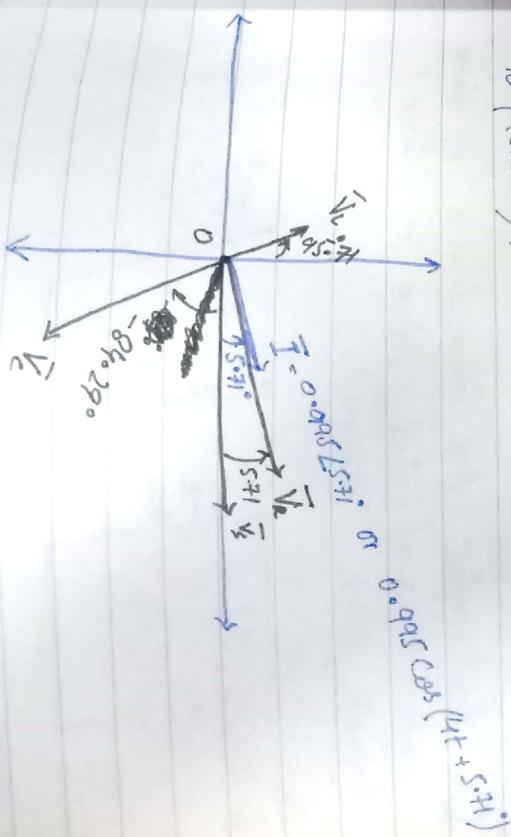- \* In capacitor current will lead voltage  $90^\circ$  (pure capacitor) (ideal)
- \* In inductor current will lag voltage  $90^\circ$  (ideal).



(57)

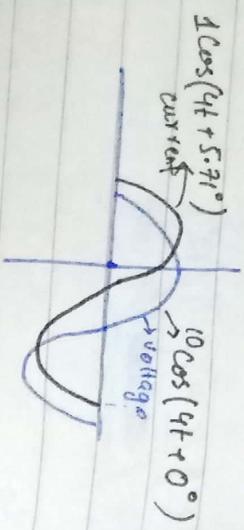

The current is leading  $5.71^\circ$  to voltage

$$G_1 = \frac{1}{R} \quad (\text{conductance}) \quad \text{unit } \text{mho}$$

$$B = \frac{1}{X} \quad (\text{Susceptance})$$


$X \rightarrow$  Reactance

$$Y = \frac{1}{Z} \quad (\text{Admittance})$$

$$\begin{aligned} X_L &= j\omega L = 4j \\ |X_L| &= \tan^{-1}(4/0) = \phi_L = 90^\circ \\ \phi_L &= 90^\circ \\ X_L &= 4L \angle 90^\circ \\ X_C &= \frac{1}{j\omega C} = \frac{1}{0.04j} \end{aligned}$$

Q. Determine the impedance of a network and find the current through each branch

$$V_s = \cos(\omega t + \phi)$$

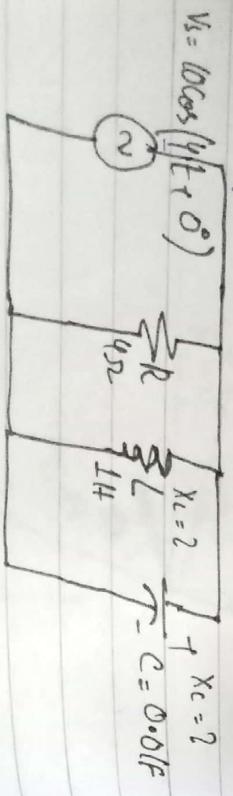

(58)

$$\begin{aligned} Z_1 &= R \\ Z_2 &= X_L \\ Z_3 &= X_C \\ \text{solution:} \\ V_s &= 10 \cos(4t + 0^\circ) \\ \bar{V}_s &= 10 \angle 0^\circ \\ \text{In phasor domain:} \\ \bar{V}_s &= 10 \angle 0^\circ \end{aligned}$$

$$Z_1 = R$$

$$Z_2 = X_L$$

$$Z_3 = X_C$$

$$X_L = j\omega L = 4j$$

$$|X_L| = \sqrt{4^2/0} = 90^\circ$$

$$\phi_L = 90^\circ$$

$$X_C = \frac{1}{j\omega C} = \frac{1}{0.04j}$$

$$X_C = -25j$$

$$|X_C| = 25$$

$$\phi_C = -90^\circ$$

$$\bar{X} = 25 \angle -90^\circ$$

As in parallel.

$$\frac{1}{Z} = \frac{1}{Z_1} + \frac{1}{Z_2} + \frac{1}{Z_3}$$

$$\frac{1}{Z} = \frac{1}{R} + \frac{1}{4} + \frac{1}{(-25j)}$$

$$\frac{1}{Z} = 0.25 - 0.25j + 0.04j$$

$$Z = 1 / (0.25 - 0.25j)$$

(59)

Rationalize we get

$$Z_r = \frac{(0.25)^2 + (0.21)^2}{(0.25)^2 - (0.21)^2} = 2.4 + 2j \text{ } \Omega$$

• Graphs

Q

$$|Z_r| = 3.012$$

$$\phi_r = \tan^{-1}(2/4) = \tan^{-1}(2/2.4)$$

$$\phi_r = 39.8^\circ$$

$$\overline{Z}_r = 3.012 \angle 39.8^\circ$$

Now, current through branch

$$I_R = \frac{V_s}{R} = \frac{10 \angle 0^\circ}{4 \angle 0^\circ}$$

$$\boxed{I_R = 2.5 \angle 0^\circ \text{ Amps}}$$

$$I_L = \frac{V_s}{X_L} = \frac{10 \angle 0^\circ}{4 \angle 90^\circ}$$

$$\boxed{I_L = 2.5 \angle -90^\circ \text{ Amps}}$$


$$I_C = \frac{V_s}{X_C} = \frac{10 \angle 0^\circ}{25 \angle -90^\circ}$$

$$\boxed{I_C = 0.5 \angle 90^\circ \text{ Amps}}$$

(60)


Relation  $\frac{V}{I} \text{ vs Impedance & Frequency}$

$$Z = R, X_L, X_C$$

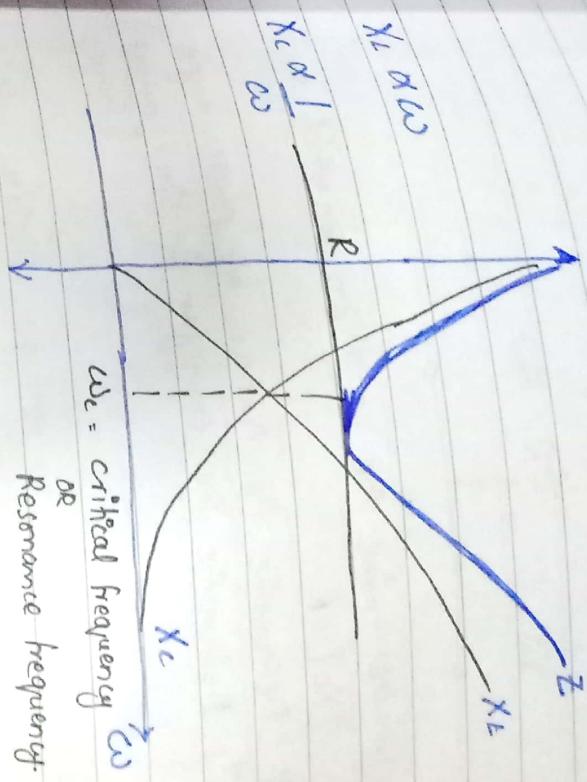

(6.1)

## Topic - Design of RC Network.

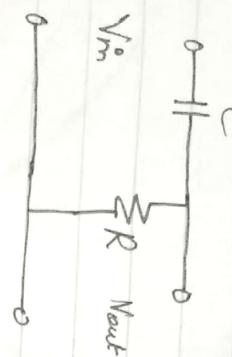

Q. S. i) Determine the condition for which the

$$|X_C| = R.$$

ii) Determine the Nature of phase angle

iii) Determine the transfer function =  $\frac{V_{out}}{V_{in}}$

As we have by voltage divider rule

$$\frac{V_{out}}{V_{in}} = \frac{R}{X_C + R} \times V_m$$

$$\frac{V_{out}}{V_m} = \frac{R}{X_C + R} = \frac{R}{\frac{1}{j\omega C} + R}$$

$$\frac{V_{out}}{V_m} = \frac{\frac{R}{j\omega C + R}}$$

$$\frac{V_{out}}{V_m} = \frac{R}{R - j\omega C}$$

$$\frac{V_{out}}{V_m} = \frac{R}{R(1 - j\frac{\omega C}{R})} \rightarrow \text{Transfer function}$$

$$\frac{V_{out}}{V_m} = \frac{1}{1 + j\frac{\omega C}{R}}$$

$$\text{Rationalizing } 1 + j\frac{\omega C}{R}$$

$$\frac{V_{out}}{V_m} = \frac{1}{\sqrt{1 + (\frac{\omega C}{R})^2}}$$

$$\frac{V_{out}}{V_m} = \frac{1}{\sqrt{1 + (\frac{\omega C}{R})^2}} + j\frac{\omega C}{R} \sqrt{1 + (\frac{\omega C}{R})^2}$$

→ magnitude

$$\phi = \tan^{-1} \left( \frac{\omega C / R}{1 + (\frac{\omega C}{R})^2} \right)$$

$$\phi = \tan^{-1} \left( \frac{1}{\sqrt{1 + (\frac{\omega C}{R})^2}} \right)$$

$$\tan \phi = \frac{\omega C}{R}$$

$$R \tan \phi = \omega C$$

(6.2)

(63)

when  $\phi = 45^\circ$ 

$$\tan 45^\circ = 1$$

Therefore

$$R = |X_C|$$

So when we have  $\phi = 45^\circ$  therefore

we get

$$R = |X_C|$$

Design RC phase shifter network to obtain  $60^\circ$  phase shift make necessary assumption if required.

(let)  $f = 100 \text{ kHz}$

$R = 1k\Omega$ ,  $C$  for capacitance.

Now  $|X_C| = \frac{1}{2\pi f C} \rightarrow (6)$

$$|X_C| = \frac{1}{2\pi f C}$$


$$|X_C| = \frac{R \tan \phi}{(1 \times 10^3) \tan 60^\circ} = 1 \times 10^3 (\sqrt{3})$$

$$|X_C| = 1730$$

By eqn (6)

$$C = \frac{1}{2\pi f |X_C|} = \frac{1}{2\pi (100 \times 10^3)(1730)}$$

$$C = 4.19 \times 10^{-10} \text{ F}$$

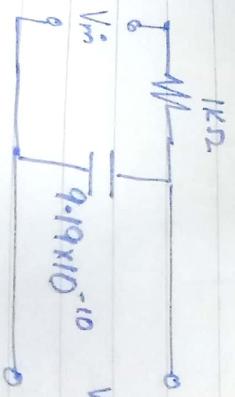


The output will be  $60^\circ$  phase shift.

Topic: Sinusoidal & Steady State

(66)


Topic: Super Position Theorem.

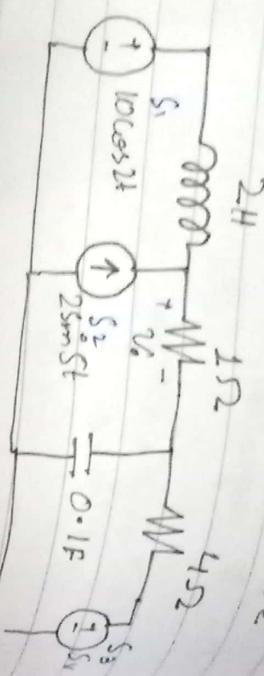

Determine  $V_o$

Solution:

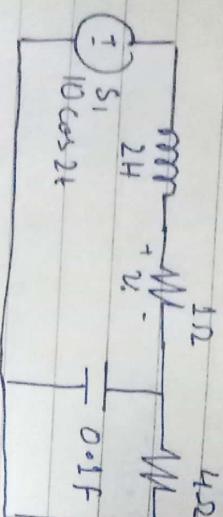Step 01: Considering  $S_1$  as a single active source and eliminating  $S_2 \& S_3$  we have circuit



$$Z_1 = \frac{R X_C}{R + X_C}$$

$$Z_1 = \frac{(4)(-5j)}{(4) + (-5j)} = -\frac{20j}{4 - 5j}$$

$$Z_1 = -\frac{20j(4 + 5j)}{(4)^2 + (5)^2}$$

$$Z_1 = -\frac{4j}{20j(4 + 5j)}$$

$$Z_1 = -20(4j - 5)$$

$$Z_1 = \frac{20}{4j} (5 - 4j)$$

$$\bar{S}_1 = 10∠0^\circ$$

$$\bar{Z}_1 = 2.044 - 2j$$

$$\bar{Z}_1 = |Z| / \phi$$

$$|Z| = \sqrt{(2.044)^2 + (2)^2}$$


$$|Z| = 3.015$$

$$\phi = \tan^{-1}\left(\frac{-2}{2.044}\right)$$

$$X_C = -S_1^\circ$$

$$X_C = 5L - 90^\circ$$

$$Z_1 = R \parallel X_C$$

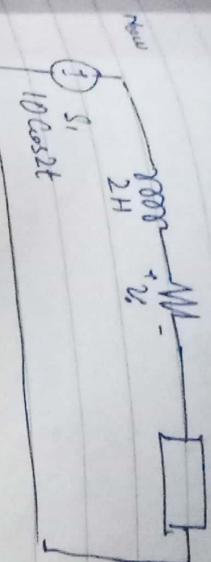

(67)

$$\phi = \text{_____} - 39.80$$

$$\bar{Z}_1 = 3.15 \angle -39.80$$

$$\bar{I}_T = \frac{\bar{S}_1}{\bar{Z}_T} = \frac{10 \angle 0^\circ}{3.97 \angle 30.17^\circ}$$

~~$$V_o = Z_T \bar{I}_T$$~~

~~$$Z_T = 3.15 \angle 30.17^\circ$$~~

Now for total impedance  $\bar{Z}_T$  as resistor, inductor and  $Z_1$  are in series

$$\bar{Z}_T = R + X_L + Z_1$$

$$\bar{Z}_T = 1 + j_1^\circ + 2.44 - j_1^\circ$$

$$\bar{Z}_T = 3.44 + j_1^\circ$$

~~$$Z_1 = 3.44 \angle 30.17^\circ$$~~

$$\phi = 30.17^\circ$$

$$\bar{Z}_1 = 3.44 \angle 30.17^\circ$$

(68)

$$\bar{I}_T = 2.51 \angle -30.17^\circ$$

Now we want  $V_o$  as in series

$$\text{current is same}$$

$$\bar{V}_o = (\bar{I}_T)(R)$$


$$\bar{V}_o = (2.51 \angle -30.17^\circ)(1 \angle 0^\circ)$$

$$\bar{V}_o = 2.51 \angle -30.17^\circ$$

or in time domain

$$V_o = 2.51 \cos(2t - 30.17^\circ)$$

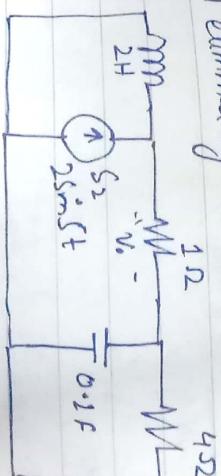STEP 02:  
Now considering  $S_2$  as a active source  
and eliminating  $S_1$  &  $S_3$ .



$$S_2 = 2 \sin 5t$$

$$S_3 = 2 \angle -90^\circ$$


$$V_m \cos(\omega t + \phi) \Rightarrow V_m \angle \phi$$

$$V_m \sin(\omega t + \phi) \Rightarrow V_m \angle 90^\circ$$

$$V_m \cos(\omega t + \phi - 90^\circ) \Rightarrow V_m \angle \phi - 90^\circ$$

$L = 2 \text{ H}$ 

(69)

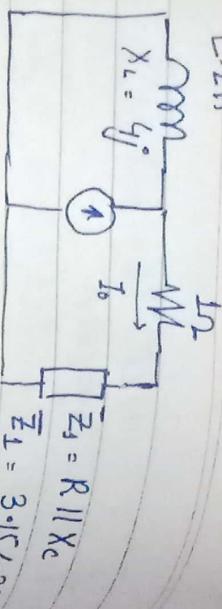

~~Note:~~  $R = 1\Omega$   $\text{parallel}$   $Z_1 = 1/\omega$  series

$$\frac{\bar{Z}_2}{\bar{Z}_1} = \frac{R + jX_C}{jX_L} = \frac{1 + j0.25}{j4} = 140^\circ + j3.15 \times 10^{-3} \text{ ohm}$$

As  $R = 1\Omega$  and  $Z_1$  are in series

$$Z_2 = R + Z_1 = 1 + 2.44 - 2j$$

$$Z_2 = 3.44 - 2j$$

By current divider rule

$$I_o = \left( \frac{X_L}{X_L + Z_2} \right) \times I_m = \frac{4}{4 + 3.44 - 2j} I_m$$

$$I_o = \left( \frac{4j}{4j + 3.44 - 2j} \right) \times I_m$$

$$I_o = \left( \frac{4j}{3.44 + 2j} \right) \times I_m$$

$$I_o = \left[ \frac{4j(3.44 - 2j)}{(3.44)^2 + (2)^2} \right] \times I_m$$

$$I_o = \frac{4}{15.83} (3.44 + 2j)$$

(70)

$$\text{Now } \bar{V}_o = 0.25 (2 + 3.44j) \times I_m = 0.50 + 0.86j \times I_m$$

$$\bar{I}_{o'} = 0.98 \angle -30.17^\circ \text{ Amps}$$

$$\bar{I}_{o'} = 1.98 \text{ A across } R = 1\Omega$$


$$\text{for } \bar{I}_o (\bar{R}) \quad \bar{V}_o = 1.98 \angle -30.17^\circ \times 1 \angle 0^\circ$$

$$\bar{V}_o = 1.98 \angle -30.17^\circ$$


$$V_o = 1.98 \cos(5t - 30.17^\circ) \text{ in time domain}$$

Step 03. Consider  $S_3$  as an active source

eliminating  $S_1$  and  $S_2$

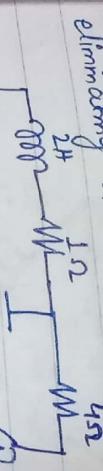

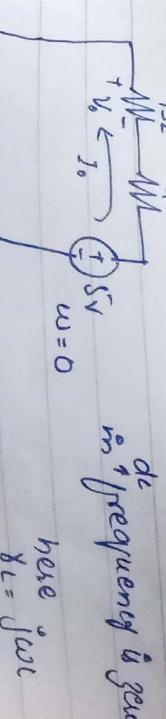As the therefore inductor short & capacitor open



here  
 $X_L = j\omega L$   
 $w = 0$

$$V_o = \frac{1}{5} \times S_3 = \frac{1}{5} \times 8 \text{ volt}$$

$V_o = 1 \text{ volt.}$

(71)


Due to opposite polarity  
 $V_o = -1$  volts

Now  
 Adds all three  $V_o$  to find total  
 $V_o$

$$V_o = 2.51 \cos(2t - 30^\circ) + 1.098 \cos(5t - 30^\circ) - 1$$

Ans

Topic 2 - Thévenin Equivalent circuit

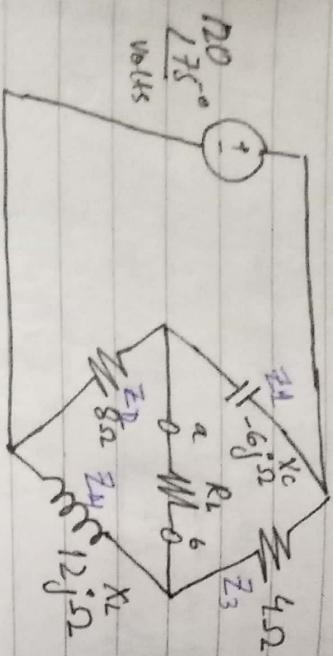

Determine Thévenin equivalent circuit.


Solution -

$$Z_{TH} = ?$$

$$V_{TH} = ? = V_{ab} = ?$$

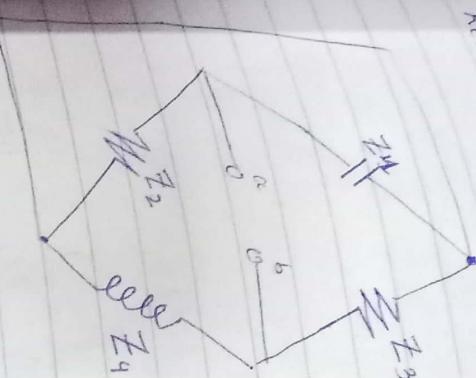(72)

For source voltage and load resistor  $R_L$ ,  
 remove



\*  $Z_1$  &  $Z_2$  are in parallel -

\*  $Z_3$  &  $Z_4$  are in parallel.  
 So we find  $Z_{12} = Z_1 \parallel Z_2$  &  $Z_{34} = Z_3 \parallel Z_4$ .

$$\frac{1}{Z_{12}} = \frac{1}{Z_1} + \frac{1}{Z_2} = \frac{1}{-6j} + \frac{1}{8}$$

$$\frac{1}{Z_{12}} = \frac{8 - 6j}{(-48j)} = -\frac{1}{6j}$$

~~$$Z_{12} = -\frac{1}{6j} = -0.16666666666666666 \text{ ohms}$$~~

(73)

$$Z_{12} = -48j = -24j^{\circ}$$

$$Z_{12} = -24j \times \frac{4-3j}{4+3j}$$

$$Z_{12} = 24j(3j-4)$$

$$Z_{12} = \frac{(4)^2(3)^2}{24(3-4j)}$$

$$Z_{12} = 0.96(3-4j)$$

$$Z_{12} = 2.88 - 3.84j$$

$$\frac{1}{Z_{34}} = \frac{1}{2_3} + \frac{1}{Z_4} = \frac{1}{4} + \frac{1}{12j} = \frac{12j+4}{48j}$$

$$Z_{34} = \frac{48j}{12j+4} = \cancel{\frac{12j}{3j+1}}$$

$$Z_{34} = \frac{(3j+1)}{12j} \cdot \frac{(3j+1)}{(3j+1)}$$

$$Z_{34} = \frac{12}{12} \left( \frac{3+j}{j} \right)^2$$

$$Z_{34} = \frac{12}{10} (3+j)$$

$$Z_{34} = 1.2 (3+j)$$

$$Z_{34} = 3.6 + 1.2j$$

(74)

$Z_{12}$  and  $Z_{34}$  are in series  
 $(2.88 - 3.84j) + (3.6 + 1.2j)$

$$Z_{TH} = \frac{2.88}{6.48} = 2.68j$$

$$Z_{TH} = \sqrt{(6.48)^2 + (-2.68)^2}$$

In phasor

$$|Z_{TH}| = \sqrt{7^2}$$

$$\text{Phase} = \tan^{-1} \left( \frac{-2.68}{6.48} \right)$$

$$\phi = 40^\circ$$


$$\phi = -22.46^\circ$$

$$Z_{TH} = 7 / 22.46^\circ$$

Now for  $V_{ab}$ 

$$\frac{V_a}{V_b} = \frac{Z_1}{Z_2 + Z_3} = \frac{6L90^\circ}{8L0^\circ}$$
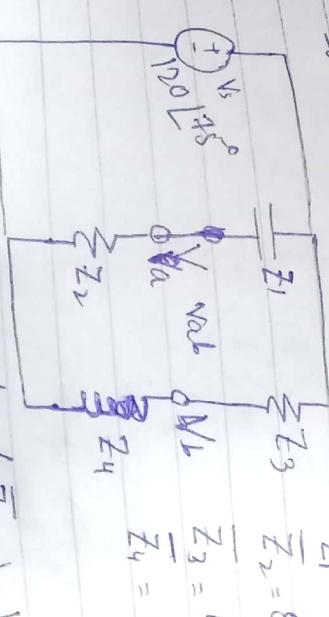
$$\frac{V_a}{V_b} = \frac{4L0^\circ}{12L90^\circ}$$



$$V_a = \left( \frac{Z_1}{Z_2 + Z_3} \right) \times V_s$$

$$V_a = \frac{6L90^\circ}{8L0^\circ} V_s$$

$$V_a = \frac{48}{2(-3+4)} V_s$$

(75)

$$V_a = \frac{4}{4} (4 + 3j) \times V_s$$

$$V_a = \frac{4}{4} \left( \frac{4 - 3j}{4 + 3j} \right) (4 + 3j) \times V_s$$

$$V_a = \frac{4}{25} (4 + 3j) \times V_s$$

$$V_a = 0.16 (4 + 3j) \times V_s$$

$$V_a = \left( 0.64 + 0.48j \right) \times V_s$$

$$V_a = 0.8 \angle 36.86^\circ \times 120 \angle 75^\circ$$

$$V_a = 96 \angle 111.86^\circ$$

$$x = r \cos \theta$$

$$y = r \sin \theta$$

$$\text{#}$$

$$V_a = 96 \left( \cos 111.86^\circ + j \sin 111.86^\circ \right)$$

$$V_b = \left( \frac{Z_4}{Z_3 + Z_4} \right) \times V_s$$

$$V_b = \frac{12j}{12j + 4} \times V_s$$

$$V_b = \frac{12j}{4 + 12j} (4 - 12j) \times V_s$$

$$V_b = \frac{12j}{(4 + 12j)^2} (4j + 12) \times V_s$$

(76)

$$V_b = \frac{12}{160} (12 + 4j) \times V_s$$

$$V_b = 0.075 (12 + 4j) \times V_s$$

$$V_b = (0.9 + 0.3j) \times V_s$$

$$V_b = 0.94 \angle 18.43^\circ \times 120 \angle 75^\circ$$

$$V_b = 112.08 \angle 93.43^\circ$$

$$V_b = 112.08 \left( \cos 93.43^\circ + j \sin 93.43^\circ \right)$$

$$V_b = -6.748 + j 112.59$$

$$V_b = V_b - V_a = ?$$

$$V_{ab} = -6.748 + 112.59j + 35.74 - 89.09j$$

$$V_{ab} = 28.992 + 23.50j$$

$$V_{ab} = 37.032 \angle 39.027^\circ \text{ Volts}$$

$$\sqrt{V_{TH}} = V_{ab}$$

$$\boxed{\sqrt{V_{TH}} = \sqrt{7.122 \angle 46^\circ}}$$

R

## Topic c - AC power

### \* Instantaneous power.

Power in watts at any instant of time

$$P(t) = V(t) \times I(t)$$

when

$$\begin{aligned} V(t) &= V_m \cos(\omega t + \phi_v) \\ i(t) &= I_m \cos(\omega t + \phi_i) \end{aligned}$$

Now

$$\begin{aligned} P(t) &= V_m \cos(\omega t + \phi_v) \times I_m \cos(\omega t + \phi_i) \\ P(t) &= V_m I_m [\cos(\omega t + \phi_v) + \cos(\omega t + \phi_i)] \\ &\quad \cdot \cos \alpha \cos \beta + \frac{1}{2} [\cos(\alpha - \beta) + \cos(\alpha + \beta)] \end{aligned}$$

$$P(t) = V_m I_m \frac{1}{2} [\cos(\alpha - \phi_v - \phi_i) + \cos(\alpha + \phi_v + \phi_i)]$$

$$P(t) = \frac{1}{2} V_m I_m \cos(\phi_v - \phi_i) - \frac{1}{2} V_m I_m \cos(2\omega t + \phi_v + \phi_i)$$

### \* Average Power

The average power (in watts) is the instantaneous power over a period of time

$$P_{av} = \frac{1}{2} V_m I_m \cos(\phi_v - \phi_i)$$


$$P_{av} = \frac{1}{2} \bar{V}_m \bar{I}_m \cos(\phi_v - \phi_i)$$

$$\begin{aligned} \bar{V} &= V_m \angle \phi_v \\ \bar{I} &= I_m \angle \phi_i \end{aligned}$$

$$\bar{V} \times \bar{I} = \frac{1}{2} V_m I_m \angle (\phi_v + \phi_i)$$

$\rightarrow$  Average Power in Polar form.

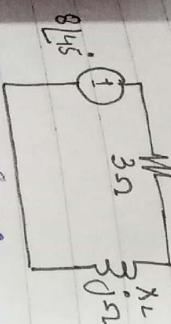Q. Determine the average power drawn by resistor & inductor in R-L circuit; Power drawn by resistor & inductor



Solution:

$$\begin{aligned} \bar{V} &= 12 \angle 0^\circ \\ \bar{I} &= 12 \angle 0^\circ \\ \bar{R} &= 3 \angle 0^\circ \\ \bar{L} &= 3j \angle 90^\circ \end{aligned}$$

$$\bar{I} = \frac{1}{2} \angle 18^\circ 43'$$

~~$$\begin{aligned} \bar{I} &= 3.62 \angle 18^\circ 43' \\ &= 3.62 \angle 18^\circ 43' \end{aligned}$$~~

~~$$\begin{aligned} P_R &= \frac{1}{2} (845^\circ) (245^\circ) \\ &= 218^\circ 43' \end{aligned}$$~~

$$P = \sqrt{I} I^2 R$$


Solt.

$$\frac{Z}{2} = R + jX_L$$

$$\frac{Z}{2} = 3 + j^{\circ}$$

$$|Z| = \sqrt{(3)^2 + (1)^2}$$

$$|Z| = 3.162$$

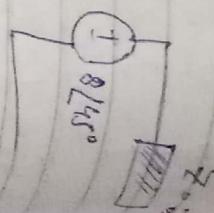

$$\phi_2 = \tan^{-1}(1/3) = 18^\circ 43'$$

$$\bar{Z} = 3.162 \angle 18^\circ 43'$$

-

$$\bar{I}_m = \frac{8 \angle 45^\circ}{3.162 \angle 18^\circ 43'}$$

$$\bar{I}_m = \frac{2.53}{2.053} \angle 26.57^\circ$$

:

Find Power delivered to load  $26.53^\circ$

$$P_L = \frac{1}{2} (I_m)^2 X_L = \frac{1}{2} (2.53)^2 \times 1 / 26.53^\circ$$

$$\bar{P}_L = \frac{1}{2} (I_m)^2 \angle 26.53^\circ = 3.20 \angle 116.53^\circ$$

Ans

Ques: Calculate Power

$$\bar{P}_{av} = \frac{1}{2} V_m \bar{I}_m * \angle (\phi_2 - \phi_1)$$

$$\bar{P}_{av} = \frac{1}{2} (8 \angle 45^\circ) (3.162 \angle 18^\circ 43')$$

$$\bar{P}_{av} = \frac{1}{2} (8 \angle 45^\circ) (3.162 \angle 18^\circ 43') \angle 26.57^\circ$$

$$\text{Now Power across branches } \frac{V_m}{R} = \frac{1}{2} \left( \frac{1}{I_m} \right)^2 R = \frac{1}{2} \left( \frac{1}{2.53} \right)^2 \times 1$$

$$\begin{cases} 12 \sin t & \text{when } 0 \leq t \leq \pi \\ 0 & \text{when } \pi \leq t \leq 2\pi \end{cases}$$

Effective OR RMS value of Periodic Circuit

$$V_{rms} = \sqrt{\frac{1}{T} \int_0^T V(t)^2 dt}$$

$$V_{rms} = \sqrt{\frac{1}{T} \int_0^T V^2 dt}$$

$$I_{rms} = \sqrt{\frac{1}{T} \int_0^T I^2 dt}$$

The effective value of periodic current is the value of DC current that produces same amount of heat in a resistor as produced by periodic current, also known as Root mean square value of current.

Q. Determine the RMS value of voltage wave form shown in figure.

$V(t)$



$$V_{rms} = \sqrt{\frac{1}{T} \left[ \int_0^{\pi} (12 \sin t)^2 dt + \int_{\pi}^{2\pi} 0^2 dt \right]}$$

$$V_{rms} = \sqrt{\frac{1}{T} \int_0^{\pi} (144 \sin^2 t) dt}$$

$$V_{rms} = \sqrt{\frac{144}{2\pi} \int_0^{\pi} \frac{1}{2} (1 - \cos 2t) dt}$$

$$V_{rms} = \sqrt{\frac{144}{2\pi} \left[ \frac{1}{2} \left[ t - \frac{1}{2} \sin 2t \right] \right]_0^{\pi}}$$

$$V_{rms} = \sqrt{\frac{144}{4\pi} \left( \pi - \frac{1}{2} \sin 2\pi \right)}$$

$$V_{rms} = \sqrt{\frac{144}{4\pi} (\pi)}$$

$$V_{rms} = 6 \text{ Volts.}$$

Ans

#### (i) Real Power e-

Actual power consumed  
also called Active power measured by  
watts.

$$P = \text{Vrms} \text{ I rms} \cos \phi$$

#### (ii) Reactive Power e-

Amount of power that move back  
and forth from source to load but  
consumed measured in VA.

$$Q = \text{Vrms} \text{ I rms} \sin \phi$$

power factor  $\sigma$

$$\begin{array}{c} Q \\ \parallel \\ \text{Vrms} \\ \parallel \\ S = \sqrt{P^2 + Q^2} \\ \parallel \\ \phi_v - \phi_i = 90^\circ \end{array}$$

#### (iii) Apparent Power e-


Total power drawn by load from  
a source including active and  
reactive component measured in VA.

$$S = \text{Vrms} \times \text{I rms}$$

#### POWER TRIANGLE e-

$$P = S \cos \phi$$

$$Q = S \sin \phi$$

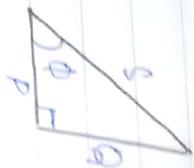


Relation B/w Real, Reactive & Apparent

Power e

$$S^2 = P^2 + Q^2 \quad \text{Magnitude}$$
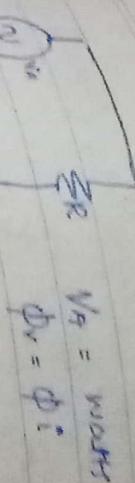
$$S^2 = P^2 + Q^2 \quad \text{complex form}$$



$$V_A = I \cdot Z_L$$

$$\phi_v = \phi_i$$