

Image

✓ PMT \rightarrow Pole Mount Transformer

If the voltages & angles of the three coils are same then it is called three phase.


Mathematical:

$$V_a = V_m [0^\circ]$$

$$V_b = V_m [120^\circ]$$

$$V_c = V_m [-120^\circ]$$


, THREE PHASE SYSTEM

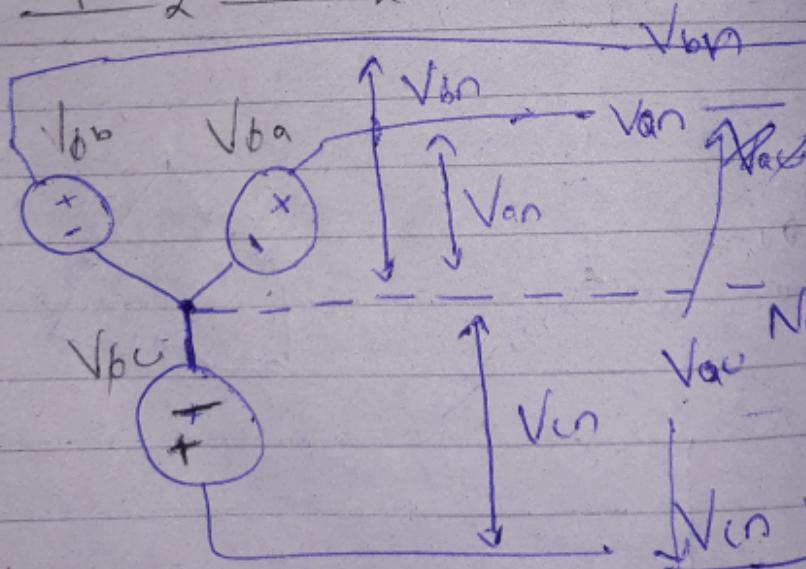

Balanced Y-Three phase source

at Transformer

giles
are
feed.

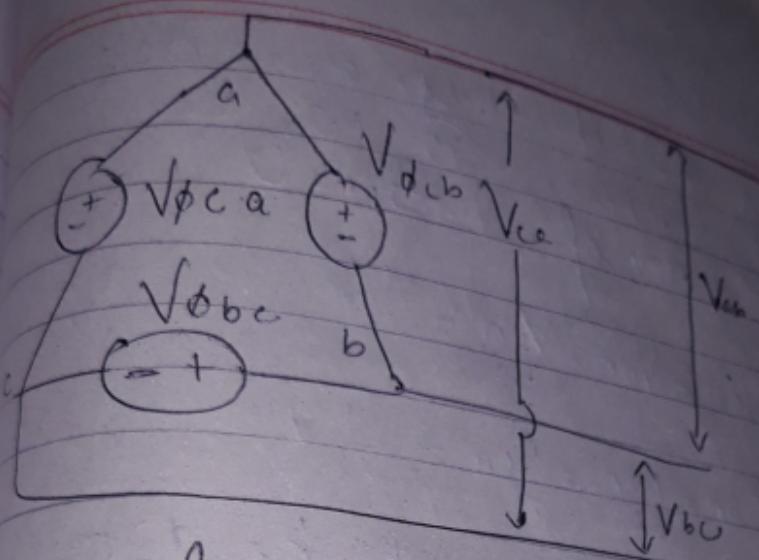

Beforce Δ three phase source:

$\nabla \phi$ phase voltage = Voltage per phase
(potential difference develop in phase winding)

Neutral

V_{nb}

Line
Source

∇_L - Line voltage = potential diff b/w any two-phases-

Y:

- In Y - If there are balanced then there is no current in neutral. $\therefore \delta_n = 0$

$$\text{V}_{an} = \text{V}_{bn} + \text{V}_{cn} = V_0$$

$$\therefore \overline{I}_{ba} = \overline{I}_{an} = I_{co} = \overline{I}_\phi$$

- Phase shift must be 120° .

$$\begin{aligned} & \text{At } \delta_\phi = 230^\circ, \quad V_{ba} = 230^\circ \\ & \quad \overline{V}_{ba} = \overline{V}_{an} \\ & \quad \overline{V}_k = \overline{V}_{an} \end{aligned}$$

$$V_L = V_{ab} = V_{bc} = V_{ca}$$

In Y - condition

$$\boxed{\overline{I}_L = \overline{I}_\phi}$$

balanced
circuit

$$V_{ab} = ?$$

$$V_{ab} = V_{an} - V_{bn}$$

$$V_{an} = 398 \angle -30^\circ$$

$$V_L = 398 \angle -30^\circ$$


$$V_{bc} = 398 \angle 90^\circ$$

$$V_{ca} = 398 \angle -150^\circ$$

$$V_{ab} \neq V_{bc} + V_{ca} = 0 \quad \text{①}$$

$$(398 \angle -30^\circ) + (398 \angle 90^\circ) \\ + (398 \angle -150^\circ) = 0$$

$$\checkmark =$$

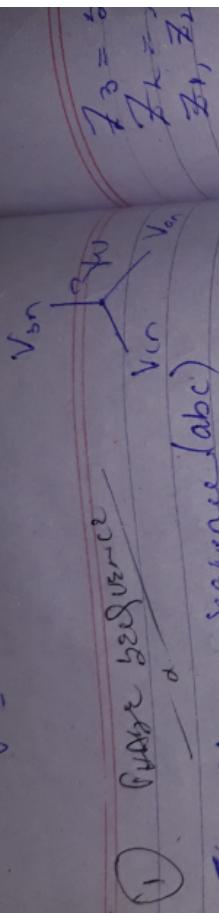


• ~~abc~~ phase sequence (abc)


$V_{an} = V_m \angle 0^\circ, V_{bn} = V_m \angle 120^\circ, V_{cn} = V_m \angle 120^\circ$

+ve phase sequence (a, b)

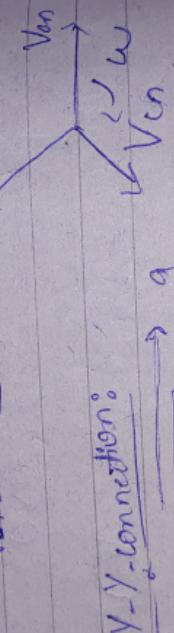$V_{an} = V_m \angle 0^\circ, V_{bn} = V_m \angle -120^\circ, V_{cn} = V_m \angle 120^\circ$




Y-Y connection:

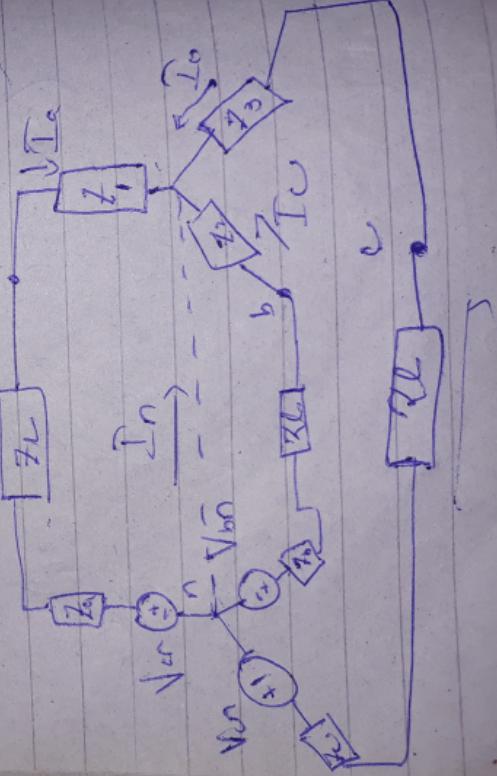

Z_0 = source winding Impedance
 Z_L = line impedance
 Z_1, Z_2, Z_3 (Impedance of each phase)


$$Z_P = Z_2 + Z_1 + Z_3$$

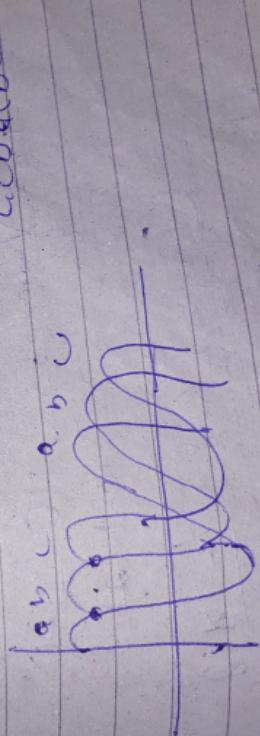For balanced phases
if phases in balance, mean
impedance of each phase
are equal if magnitude imp



$$V_a = \sqrt{100} \quad V_{ba} = \sqrt{100} \cdot \frac{1}{\sqrt{3}} = \frac{10}{\sqrt{3}}$$
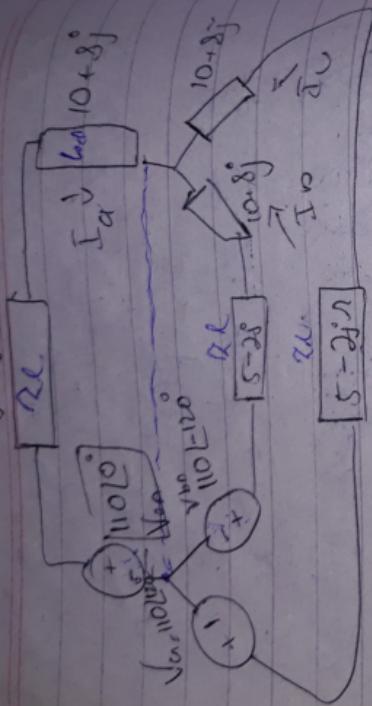
$$V_a = \sqrt{100} \quad V_{ba} = \sqrt{100} \cdot \frac{1}{\sqrt{3}} = \frac{10}{\sqrt{3}}$$



$$Q_{12}$$

$$\frac{T_a - V_{ba}}{Z_1} \Rightarrow \frac{110 \angle 0^\circ}{10 + 8j + 5 - 8j} \Rightarrow \frac{110 \angle 0^\circ}{16.1 \angle 21.8^\circ}$$



$$\boxed{T_a - V_{ba} \Rightarrow 6.8 \angle -21.8^\circ}$$

$$T_b = \frac{V_{ba}}{Z_2} \Rightarrow \frac{110 \angle -120^\circ}{16.1 \angle 21.8^\circ}$$

$$\boxed{T_b \Rightarrow 6.83 \angle -141.8^\circ}$$

$$\boxed{T_c = 6.83 \angle 98.2^\circ}$$

BALANCE Y-D

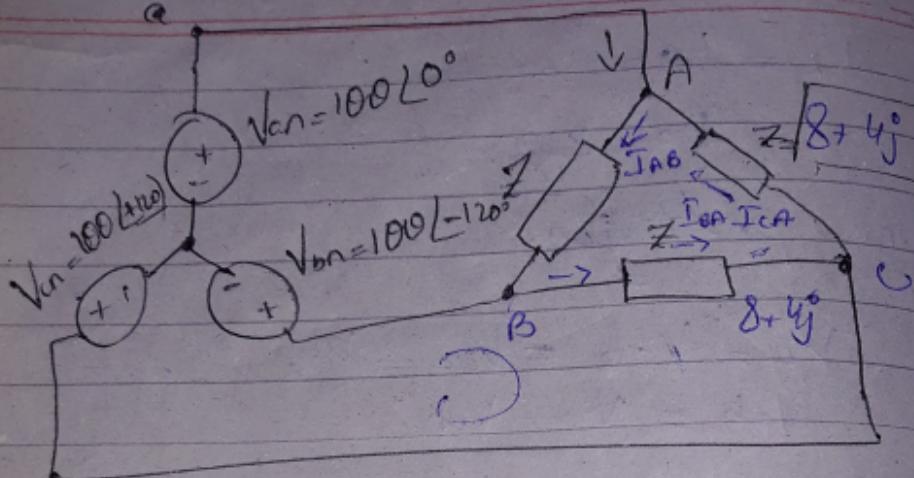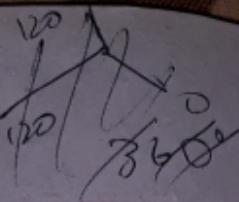

Determine the value of V_{AB} , I_{AB} , I_{BC} , I_{CA}

$$\Rightarrow \boxed{Z = 8 + 4j}$$

$$V_{AB} = V_{Aa} - V_{Ba} \\ \Rightarrow 100 \angle 20^\circ - 100 \angle 120^\circ$$

$$\boxed{V_{AB} \Rightarrow 173.20 \angle 30^\circ}$$

$$\boxed{I_{AB} \Rightarrow \frac{V_{AB}}{Z} \Rightarrow 19.37 \angle 3.43}$$


BALANCE

D-Y

FREQUENCY RESPONSE

$H(\omega)$, the frequency Response is the variation in the behaviour of ckt with signal frequency

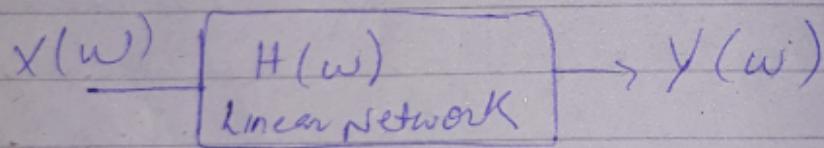* The behaviour observe over frequency of i/p Signal ω , that change in a amplitude -



$H(\omega) \Rightarrow$ Phasor output
Phasor input.

$H(\omega) = \frac{Y(\omega)}{X(\omega)}$ This frequency dependent Ratio is called Transfer fraction or Natural function.

$H(\omega)$

① Zero

The numbers are functions

- zero
- in

② Pole

(ω_p)

ω

of

free

①

$$H(\omega) = |H(\omega)| e^{j\phi}$$

① Zeros:

- The Roots of the ~~Roots~~
numerators polynomial of $H(\omega)$
are called zeros of transfer
function -
• Zeros are the value of ' ω ' that
make $H(\omega) = 0$
about

② Poles:



- Poles are the value of
' ω ' that makes $H(\omega) = \infty$
• The roots of the denominator
polynomial are called poles
of transfer function -

Frequencies Response:

- ① convert all element into frequency
of variable -

(2)

$$H(\omega) = \frac{Y(\omega)}{X(\omega)}$$

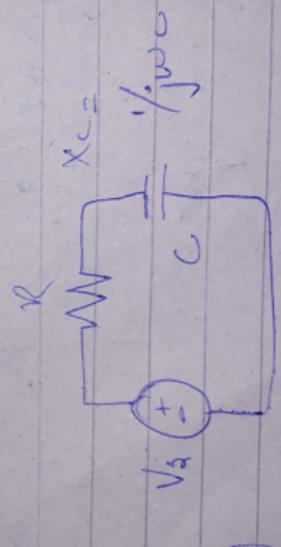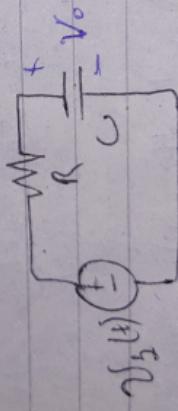② Determine $|H(\omega)|$ ③ Determine ϕ of $H(\omega)$ ④ Plot curves $|H(\omega)|$ vs ω
of ϕ vs ω Determine Frequency Response
of given circ.

(1)

$$S = 5 + j\omega$$

$$\textcircled{2} \quad H(\omega) = \frac{X(\omega)}{Z_1 + Z_2}$$

$$H(\omega) = \frac{V_o}{V_i}$$

$$V_o = V_{in} \left(\frac{Z_2}{Z_1 + Z_2} \right)$$

$$\Rightarrow V_{in} \left(\frac{1/j\omega C + R}{j\omega C + R} \right)$$

$$V_o \Rightarrow \left(\frac{1}{1 + j\omega CR} \right) V_{in}$$

$$H(\omega) = \frac{1}{1 + j\omega CR}$$

$$H(\omega) = \frac{1}{1 + j(\omega/\omega_0)} \quad \omega_0 = \frac{1}{RC}$$

$$H(\omega) = \frac{j(\omega/\omega_0)}{1 + (\omega/\omega_0)^2}$$

$$1 + \left(\frac{\omega}{\omega_0} \right)^2$$

$$f = -tc$$

$$H(\omega) = \frac{1}{1 + \left(\frac{\omega}{\omega_0}\right)^2} = \frac{1}{1 + \left(\frac{\omega}{2\pi/100}\right)^2}$$

$$|H|^3 = \frac{m^3}{m^2} = m$$

$$H(\omega) = \sqrt{1 + \left(\frac{\omega}{\omega_0}\right)^2} + i \left(\frac{\omega/\omega_0}{1 + (\omega/\omega_0)} \right)$$

$$\Rightarrow \sqrt{\frac{1 + (m/\omega_0)}{1 + (m/\omega_0)^2}}$$

$$H = \sqrt{1 + \left(\frac{m}{n}\right)^2}$$

$$j = \tan^{-1} \left(\frac{\omega/\omega_0}{1 + (\omega/\omega_0)} \right)$$


$$\varphi = -\tan^{-1} \left(\frac{\omega}{\omega_0} \right)$$

$\omega = 0$

$$\omega = \infty$$

$$|H(\omega)|$$

$$\omega / \omega_0)^2$$

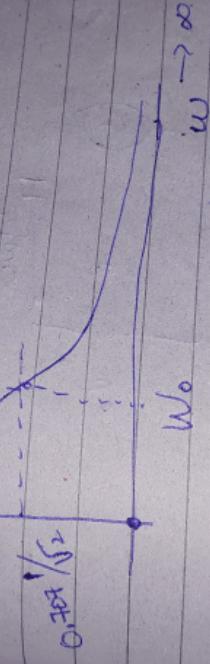

$\omega \rightarrow 0$


ω_0

$\omega \rightarrow \infty$

ω'


ω_0 = Critical freqency

$$\varphi$$

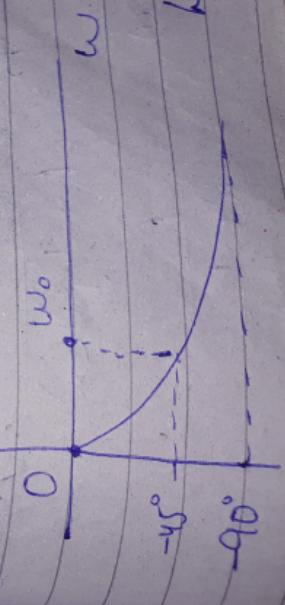


Low pass
Gain

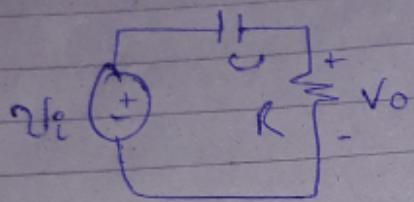~~YSLAO~~
Frequency Response OF (CR, R_1, V_f)



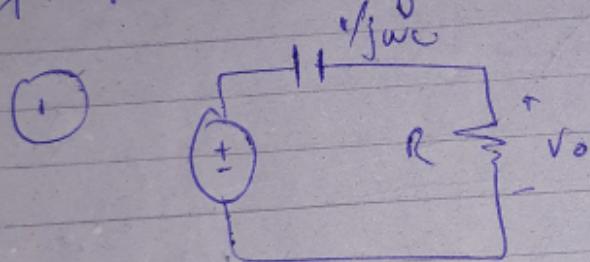Determine Transfer Function &
Poles & zeros:



②

$$H(\omega) = \frac{V_o(\omega)}{V_i(\omega)} = \frac{V_o}{V_i}$$

$$|H(\omega)| \Rightarrow \boxed{\quad}$$

$$V_o = \frac{R}{(R + 1/j\omega C)} \times V_i$$

$$|H(\omega)| \Rightarrow$$

$$H(\omega) \Rightarrow \frac{R}{R + \frac{1}{j\omega C}}$$

$$\boxed{|H(\omega)|}$$

$$H(\omega) \Rightarrow Rj\omega +$$

$$\Rightarrow \frac{(j\omega/\omega_0)}{(j\omega/\omega_0 + 1)}$$

$$\Rightarrow 1 + \frac{(j\omega/\omega_0)}{(1 + j\omega/\omega_0)} \times \frac{(1 - j\omega/\omega_0)}{(1 - j\omega/\omega_0)}$$

$$\Rightarrow \frac{\omega^2/\omega_0^2 + \omega^2/\omega_0^2}{1 + (\omega/\omega_0)^2}$$

$$\Rightarrow \frac{\omega^2/\omega_0^2}{1 + (\omega/\omega_0)^2} + \frac{\omega^2/\omega_0^2}{1 + (\omega/\omega_0)^2}$$

$$|H(\omega)| \Rightarrow \sqrt{\left(\frac{(\omega/\omega_0)^2}{1 + (\omega/\omega_0)^2}\right)^2 + \left(\frac{\omega/\omega_0}{1 + (\omega/\omega_0)^2}\right)^2}$$

$$|H(\omega)| \Rightarrow \sqrt{\frac{(\omega/\omega_0)^2 + (\omega/\omega_0)^2}{[1 + (\omega/\omega_0)^2]^2}}$$

$$\Rightarrow \frac{(\omega/\omega_0)^2}{1 + (\omega/\omega_0)^2} \times \frac{1}{1 + (\omega/\omega_0)^2}$$

$$\Rightarrow \frac{(\omega/\omega_0)^2}{1 + (\omega/\omega_0)^2}$$


$$|H(\omega)| = \frac{\omega/\omega_0}{1 + (\omega/\omega_0)}$$

$$\theta \Rightarrow \tan^{-1} \left(\frac{\omega}{\omega_0} \right)$$


$\omega = \infty$

$$\frac{\omega/\omega_0}{1 + (\omega/\omega_0)} > 1$$

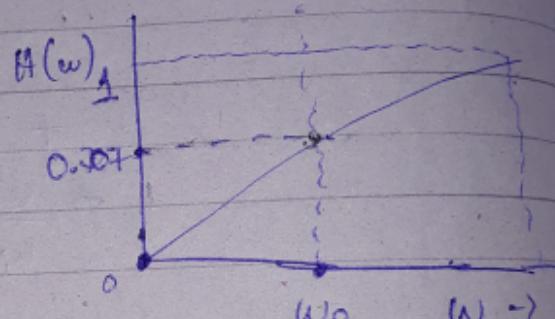- ✓ $\omega = 0$
- ✓ $\omega = \infty$
- ✓ $\omega = \omega_0$



A_p, P

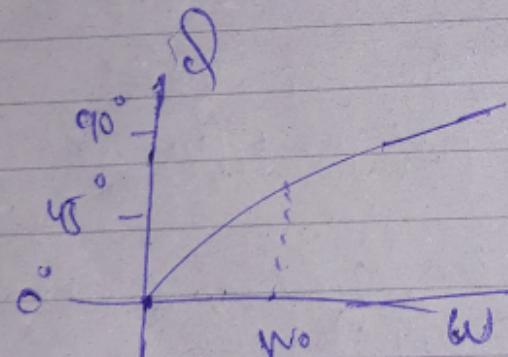

$\omega = 0$
 $\omega = \omega_0$
 $\omega = \infty$

High pass filter

true

$$\frac{1}{\sqrt{2}} = 0.707$$


$\omega \rightarrow \infty$

$$\omega/\omega_0$$




$$\omega/\omega_0$$

$$H(\omega) \rightarrow 1$$

L.P. P

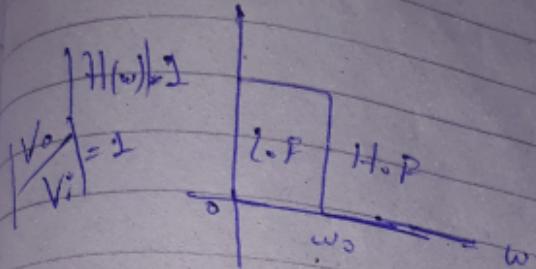

B.P.S

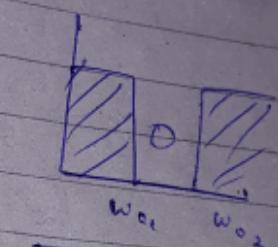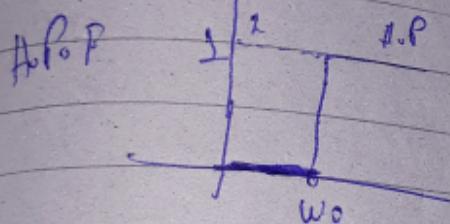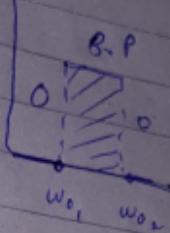

$$B(w) \geq w_{01} - w_{02}$$

$$\omega/\omega_0 = 0$$

$\omega = 0$ zero

$$1 + j \frac{\omega}{\omega_0} = 0$$

$$\omega_0 - 10^j = 0$$


$$\omega_j = -\omega_0$$

$$\omega_2 = -\omega_0/j$$

$$z \rightarrow j \frac{\omega_0}{j^2}$$

$\boxed{\omega \geq \omega_0}$ pole

Series RLC Response:

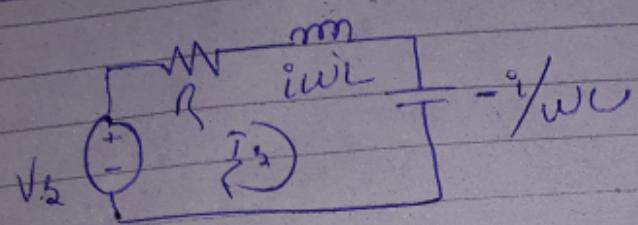


Resonance condition is occurs at frequency $\omega = \omega_0$ where the $X_C = X_L$ & magnitude of impedance Z reduce to $Z = R$, the alt current at Resonance frequency is max in ckt.

$$\frac{V_s(\omega)}{I_s(\omega)} = Z$$

$$= R + j(\omega L - 1/\omega C)$$

at resonance frequency

$$\omega L - \frac{1}{\omega C} = 0$$

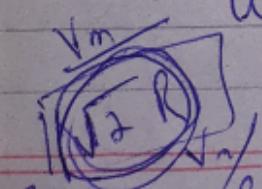

I_m $I_{r.m.s}$ $I_{c.r.m.s}$ $I_{r.m.s}$ $I_{c.r.m.s}$

$$\omega_L = 1/w_c$$

$$\omega^2 = 1/LC$$


$$\omega = 1/\sqrt{LC}$$

$$\omega = 1/\sqrt{RC}$$

$$I(\omega) = \frac{V(\omega)}{Z}$$

$$= \frac{V(\omega)}{R + j(\omega L - 1/w_c)}$$

$$|I(\omega)| = \frac{|V(\omega)|}{\sqrt{R^2 + (\omega L - 1/w_c)^2}}$$

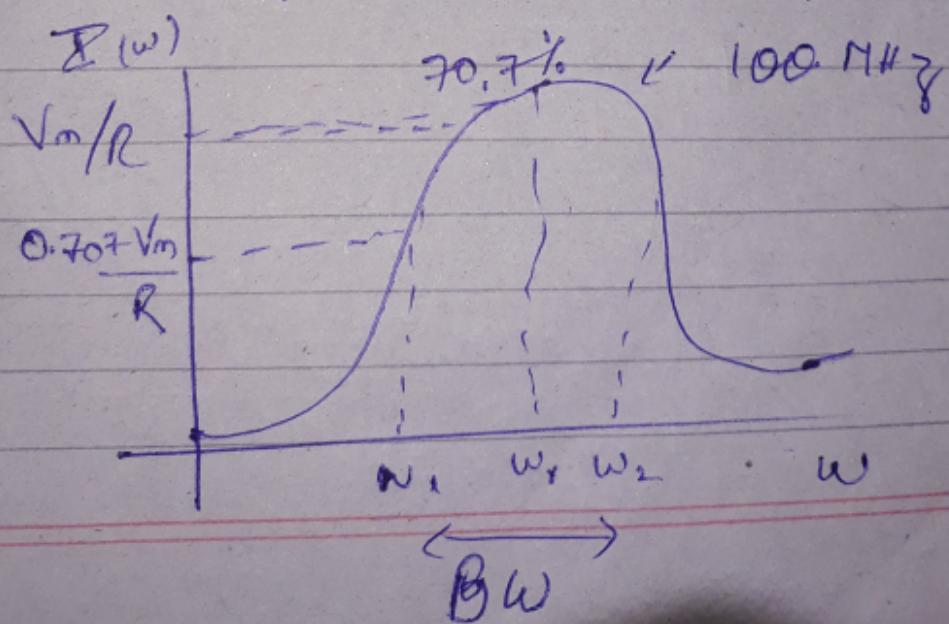

ω_1 & ω_2 are called cutoff.
are called ~~so~~ or half power frequency.

$$BW = \omega_2 - \omega_1$$

$$\omega_r = \sqrt{\omega_1 \omega_2}$$

At ω_r the impedance is pure resistive so that the current & voltage are in phase & forms the power factor is to unity.

QD.

PASSIVE FILTERS

IDEAL RESPONSE

S_{H_0}

$$\omega_0 = \frac{1}{LC}$$

Filter type	$ H(0) $	$ H(\infty) $	$ H(\omega_r) $
-------------	----------	---------------	-----------------


Low Pass	1	0	$\text{1st order } 1/\sqrt{2}$
----------	---	---	--------------------------------

High Pass	0	1	$\text{1st order } 1/\sqrt{2}$
-----------	---	---	--------------------------------

Band pass	0	0	$\text{1st order } 1/\sqrt{2}$
-----------	---	---	--------------------------------

Band stop	1	1	$\text{2nd order } 1/\sqrt{2}$
-----------	---	---	--------------------------------

$$j\omega L \quad 1/j\omega C$$

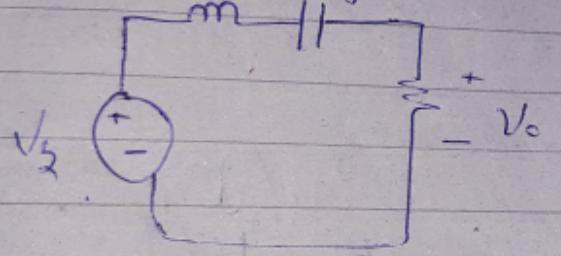

$$\frac{V_o}{V_s} \Rightarrow \frac{R}{R + j\omega L + \frac{1}{j\omega C}}$$

$$\Rightarrow \frac{R}{R + j\omega \left(\omega - \frac{1}{\omega C} \right)}$$

$$\Rightarrow \frac{R}{R + j\omega \left(\omega - \frac{1}{\omega_0^2} \right)}$$

$$= \frac{R}{R + jL \left(\frac{\omega^2 - \omega_0^2}{\omega} \right)}$$

$$\Rightarrow \frac{1}{1 + jL/R \left(\frac{\omega^2 - \omega_0^2}{\omega} \right)}$$

$$\Rightarrow 1 - jL/R \left(\frac{\omega^2 - \omega_0^2}{\omega} \right)$$

$$\frac{1}{1 + \left(L/R \left(\frac{\omega^2 - \omega_0^2}{\omega} \right) \right)^2}$$

$$\Rightarrow \frac{1}{1 + \left(\frac{L}{R} \left(\frac{\omega^2 - \omega_0^2}{\omega} \right) \right)^2} - \frac{jL/R \left(\frac{\omega^2 - \omega_0^2}{\omega} \right)}{1 + \left(\frac{L}{R} \left(\frac{\omega^2 - \omega_0^2}{\omega} \right) \right)^2}$$

$$|H(\omega)| = \sqrt{\left(\frac{1}{1 + \left(\frac{L}{R} \left(\frac{\omega^2 - \omega_0^2}{\omega} \right) \right)^2} \right)^2 + \left(\frac{jL/R \left(\frac{\omega^2 - \omega_0^2}{\omega} \right)}{1 + \left(\frac{L}{R} \left(\frac{\omega^2 - \omega_0^2}{\omega} \right) \right)^2} \right)^2}$$

$$\sqrt{\frac{\left(1 + \left(\frac{L}{R} \left(\frac{\omega^2 - \omega_0^2}{\omega} \right) \right)^2 \right)^2}{\left(1 + \left(\frac{L}{R} \left(\frac{\omega^2 - \omega_0^2}{\omega} \right) \right)^2 \right)^2}}$$

$$|H(\omega)| \Rightarrow \sqrt{?}$$

$$\omega = 0$$

$$\omega = \omega_0$$

$$\omega = \infty$$

$$|H(0)| \Rightarrow 0$$

$$|H(\infty)| \Rightarrow 0$$


$$|H(\omega_0)| \Rightarrow$$

$$|H(\omega)| \Rightarrow \sqrt{\frac{1}{\omega^2 + \left(\frac{1}{C} \left(\frac{\omega^2 - \omega_0^2}{\omega}\right)^2\right)}}$$

$$\omega = 0$$

$$\begin{aligned} \omega &= \omega_0 \\ \omega &= \infty \end{aligned}$$

$$\begin{cases} |H(0)| \xrightarrow{\omega \rightarrow 0} 0 \\ |H(\infty)| \xrightarrow{\omega \rightarrow \infty} 0 \\ |H(\omega_0)| \xrightarrow{\omega \rightarrow \omega_0} 1 \end{cases}$$

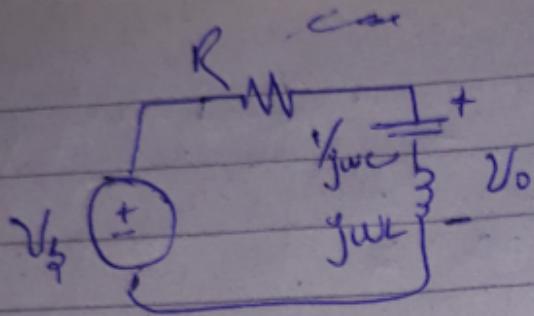


$$\frac{V_o}{V_s} = \frac{j(\omega L - 1/wc)}{R + j(\omega L - 1/wc)}$$

$$\Rightarrow \frac{j(\omega L - 1/wc)}{R + j(\omega L - 1/wc)} \times \frac{R - j(\omega L - 1/wc)}{R - j(\omega L - 1/wc)}$$

$$\Rightarrow \frac{Rj\left(\omega L - \frac{1}{wc}\right) + \left(\omega L - \frac{1}{wc}\right)^2}{R^2 + \left(\omega L - \frac{1}{wc}\right)^2}$$
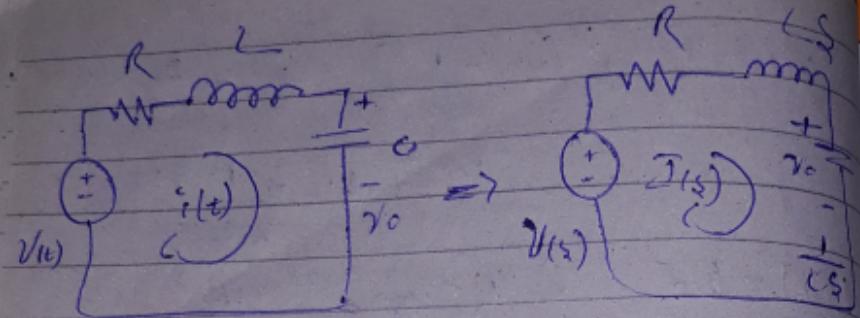
$$\Rightarrow \frac{Rj\left(\omega L - \frac{1}{wc}\right)}{R^2 + \left(\omega L - \frac{1}{wc}\right)^2} + \frac{\left(\omega L - \frac{1}{wc}\right)^2}{R^2 + \left(\omega L - \frac{1}{wc}\right)^2}$$



\therefore Determine $V_o(t)$ when System is source free

$$-V(t) + iR + L \frac{di}{dt} + V_C = 0$$

$$L \frac{di}{dt} + iR + V_C = V(t)$$

$$LC \frac{d^2 V_C}{dt^2} + RLC \frac{dV_C}{dt} + V_C = V(t)$$

$$C \frac{d^2 V_C}{dt^2} + \frac{R}{L} \frac{dV_C}{dt} + \frac{1}{LC} V_C = \frac{1}{LC} V(t)$$

Part 2:

$$-V_S + I_{IS} R + I_{IS} L S + V_o = 0$$

$$I_{IS} (R + L S) + V_o = V_S$$

$$\frac{\omega^2}{\omega_0^2} + \frac{S}{\omega_0}$$

$$\frac{R + \omega_0}{\omega_0^2}$$




$$I(S) \downarrow \frac{1}{j} X_L = L S$$

$$I(S) \downarrow \frac{1}{j} X_C = \frac{1}{C S}$$

Loop

CIRCUIT ANALYSIS WITH LAPLACE

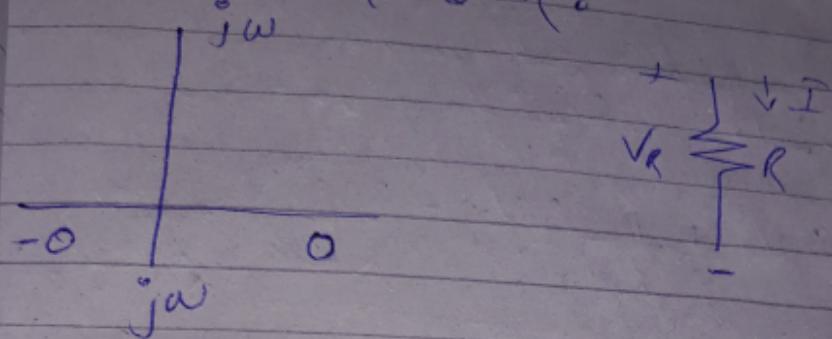

$$S = \sigma + j\omega$$

damping factor complex freq

undamped natural freq

$$V_R(t) = I(t)R$$

$$V(s) = I(s)R$$

in

Laplace

time signal \Rightarrow frequency signal

Initial condition are zero

$$V_L(t) = \frac{L di(t)}{dt} \xrightarrow{\text{Laplace}}$$

$$V_L(s) = \frac{L s}{I(s)}$$

$$i_L = \frac{dV_L(t)}{dt} \xrightarrow{\text{Laplace}}$$

$$I(s) = CSV_L$$

$$V(s) \xrightarrow{\text{Laplace}} i(s)$$

$i(t)$
Source free

$$I(s) \xrightarrow{\text{Laplace}} X_C = \frac{1}{C s}$$

$$\therefore I_s = CSV_0$$

$$CSV_0(R + LS) + V_0 = VS$$

$$RCSV_0 + LCS^2V_0 + V_0 = VS$$

$$LC \left(S^2V_0 + \frac{R}{L}SV_0 + \frac{V_0}{LC} \right) = \frac{VS}{LC}$$

$$\frac{V_0}{VS} = \left(S^2 + \frac{R}{L}S + \frac{1}{LC} \right) = \frac{1}{LC}$$

$$\frac{V_0}{VS} = \frac{\frac{1}{LC}}{\left(S^2 + \frac{R}{L}S + \frac{1}{LC} \right)}$$

$$\mathcal{L}\left\{ \frac{d}{dt}f(t) \right\} = SF(s) + F(0)$$

$$\mathcal{L}\left\{ \int f(t) dt \right\} = \frac{1}{s} F(s) + F(0)$$

$$i = C \frac{dV}{dt}$$

$$I(s) = CSV_0$$

Laplace
Fourier
 $Z - \text{Transform}$

$$\frac{V(t)}{I(t)} = X_L$$

$$\frac{V_L(s)}{I(s)} = LS$$

$$X_L = j\omega L$$

$$X_C = \frac{1}{j\omega C}$$

$$\mathcal{L}\{e^{-at}\} = \frac{1}{s+a} \quad e^{at} = \frac{1}{s-a}$$

$H(s)$ = Transfer function.

$$H(s) = \frac{(s+z_1)(s+z_2)(s+z_3)\dots}{(s+p_1)(s+p_2)(s+p_3)\dots}$$

$$= \frac{1}{(s+a_1)(s+a_2)} \Rightarrow \frac{A_1}{(s+a_1)} + \frac{A_2}{(s+a_2)}$$

$$\Rightarrow \mathcal{L}^{-1}\left(\frac{A_1}{s+a_1}\right) + \mathcal{L}^{-1}\left(\frac{A_2}{s+a_2}\right) \quad \text{Partial fraction}$$

$$\boxed{v_o = A_1 e^{-a_1 t} + A_2 e^{-a_2 t}}$$

$$s = \frac{R}{2L} \pm \sqrt{\left(\frac{R}{2L}\right)^2 - \frac{1}{LC}}$$

$$\zeta = \omega \pm \sqrt{\omega^2 - \omega_0^2}$$


$$v(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t}$$

$$v_o \quad \text{Laplace} \rightarrow s = \dot{\phi} + \omega j \quad (\text{continuous signals})$$

$$\text{Fourier} \rightarrow \omega = \omega j \quad (\text{both})$$

$$Z\text{-Trans} \rightarrow Z = \gamma e^{j\omega} \quad (\text{Discrete signals})$$

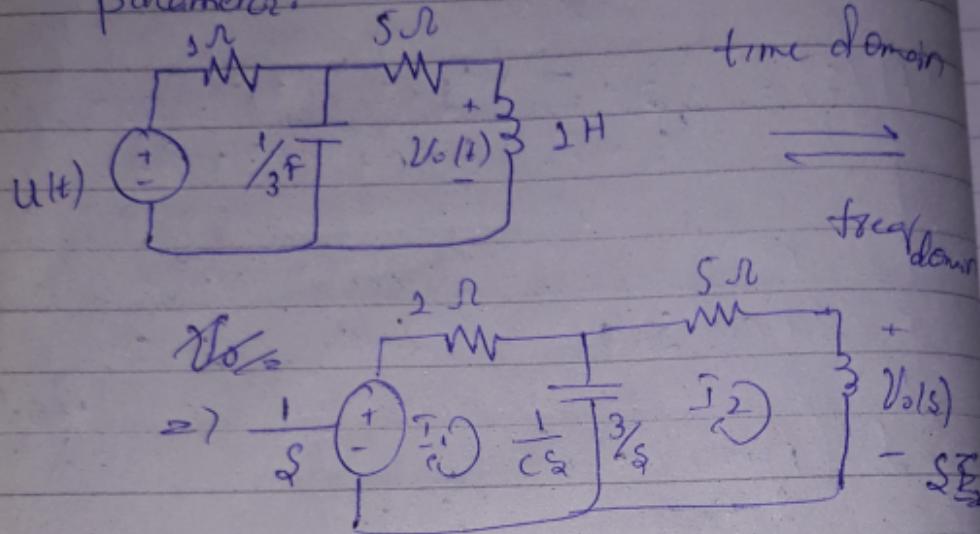• Determine the unknown $U(t)$
parameter:



Applying KVL in Loop 1:

$$-\frac{1}{s} + \bar{I}_2 \times 1 + (\bar{I}_1 - \bar{I}_2) \frac{3}{s} = 0$$

$$\frac{1}{s} = \bar{I}_1 + \frac{3}{s} \bar{I}_1 - \frac{3}{s} \bar{I}_2$$

$$\boxed{\frac{1}{s} = \left(1 + \frac{3}{s}\right) \bar{I}_1 - \frac{3}{s} \bar{I}_2} \quad \rightarrow ①$$

App KVL in loop 2:

$$5\bar{I}_2 + s\bar{I}_2 + (\bar{I}_2 - \bar{I}_1) \frac{3}{s} = 0$$

$$(5+s)\bar{I}_2$$

$$\begin{aligned} & (5+s+3)s \\ & s(s+5) \end{aligned}$$

$$\bar{I}_1 =$$

$$\bar{I}_2 =$$

Putting in ①

$$\frac{1}{s} =$$

$$\frac{1}{s} = \frac{5}{3}$$

$$\frac{1}{s} =$$

$$\bar{I}_2 s$$

$$V_L = L \frac{d}{dt}$$

$$U_{L(s)} = L \frac{d}{ds}$$

$$U_{L(s)} = L$$

domain
 \rightarrow
 freq down
 $\downarrow +$
 $\uparrow - V_0(s)$
 $- s \underline{I_2}$

$$(5+s)I_2 + \frac{3}{s}I_2 - \frac{3}{s}I_1 = 0$$

$$\left(5+s+\frac{3}{s}\right)I_2 = \frac{3}{s}I_1$$

$$s\left(s+5+\frac{3}{s}\right)I_2 = 3I_1$$

$$I_1 = \frac{s}{3} \left(s+5+\frac{3}{s}\right)$$

$$I_1 = \left(\frac{5}{3}s + \frac{s^2}{3} + 1\right)I_2$$

Putting in Eq(A)

$$\frac{1}{s} = \left(\frac{1+3}{s}\right) \times \left(\frac{5s}{3} + \frac{s^2}{3} + 1\right) I_2 - \frac{3}{s} I_2$$

$$\frac{1}{s} = \frac{5}{3}s + \frac{s^2}{3} + 1 + 5 + s + \cancel{\frac{3}{s}} - \cancel{\frac{3}{s}} I_2$$

$$\frac{1}{s} = \left(\frac{s^2 + 8s + 18}{3}\right) I_2$$

$$V_0 = I_2 s$$

$$I_2 s = \cancel{\frac{3}{s}} \frac{3}{s^2 + 8s + 18}$$

$$V_0 = \frac{3}{s^2 + 8s + 18}$$

$$= 0$$

• $V_L = L \frac{di}{dt}$

$$V_{L(s)} = L \frac{dI(s)}{dt} - L \dot{I}(0)$$

$$V_{L(s)} = L \dot{I}$$

when
 $\dot{I}(0) = V$

$$V_0 = \frac{3}{s^2 + 8s + 18}$$

$$= \frac{3}{(s+4)^2 + 2}$$

$$= \frac{3}{(s+4)^2 + (\sqrt{2})^2}$$

$$= \frac{3}{\sqrt{2}} \times \frac{\sqrt{2}}{(s+4)^2 + (\sqrt{2})^2}$$


$$\therefore \int e^{-at} \sin bt \rightarrow \frac{b}{(s+a)^2 + b^2}$$

$$\mathcal{L}^{-1}\{V_0(s)\} = s^{-1} \frac{3\sqrt{2}}{\sqrt{2}(s+4)^2 + (\sqrt{2})^2}$$

$$V_0(t) = \frac{3}{\sqrt{2}} e^{-4t} \sin \sqrt{2} t$$

An:


\underline{V}_0

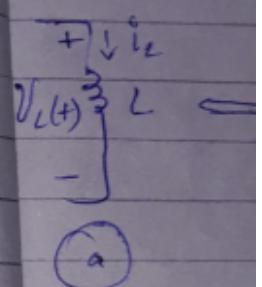


$$V_L(t) =$$

$$\underline{V}_L$$



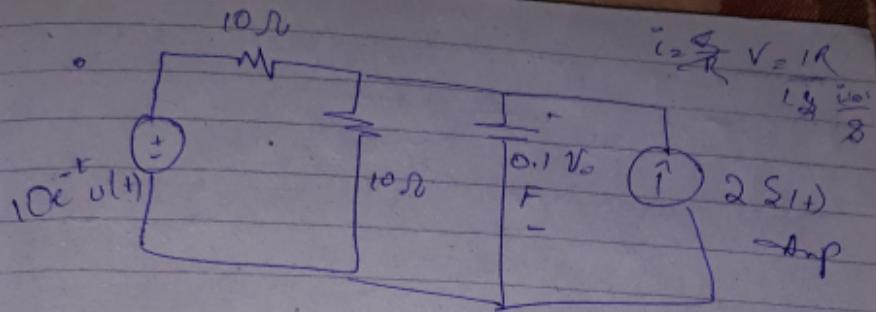

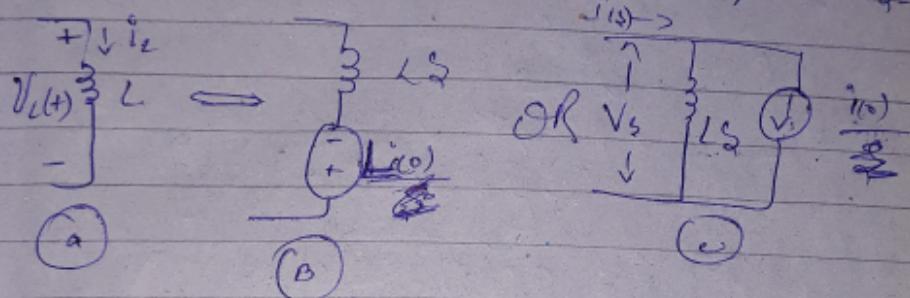Determine $V_L(0)$ when $U_L(0) = 5 \text{ Volts}$



$$V_L = L \frac{di}{dt} \quad ; \quad L V_L = L L \frac{di}{dt}$$

$$+ (\sqrt{2})^2$$


$$\begin{aligned} V_L(s) &= L \left[s \bar{I}(s) - \bar{i}(0) \right] \\ \boxed{V_L(s)} &= L s \bar{I}(s) - L \bar{i}(0) \\ &\Rightarrow \text{self energy to fig b} \end{aligned}$$

An:

$$\begin{aligned} \text{OR:} \\ V_L(s) + L \bar{i}(0) &= L s \bar{I}(s) \end{aligned}$$

$$\boxed{\frac{V_L}{Ls} + \frac{\bar{i}(0)}{s} = \bar{I}(s)}$$

self energy to fig c

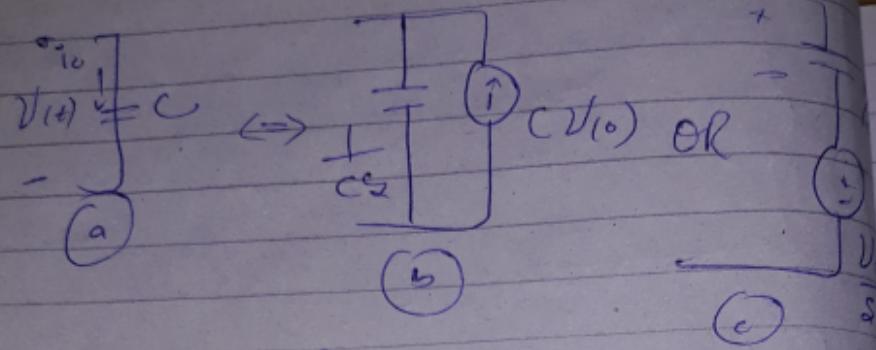

$$i_C = C \frac{dV}{dt}$$


$$L i_C = L \left\{ \frac{dV}{dt} \right\}$$

$$\bar{I}(s) = C \left[s V(s) - V(0) \right]$$

$$\boxed{\bar{I}(s) = (s V(s) - V(0)) \text{ OR}}$$

$$\bar{I}(s) + C V(0) = (s V(s)) \quad (b)$$
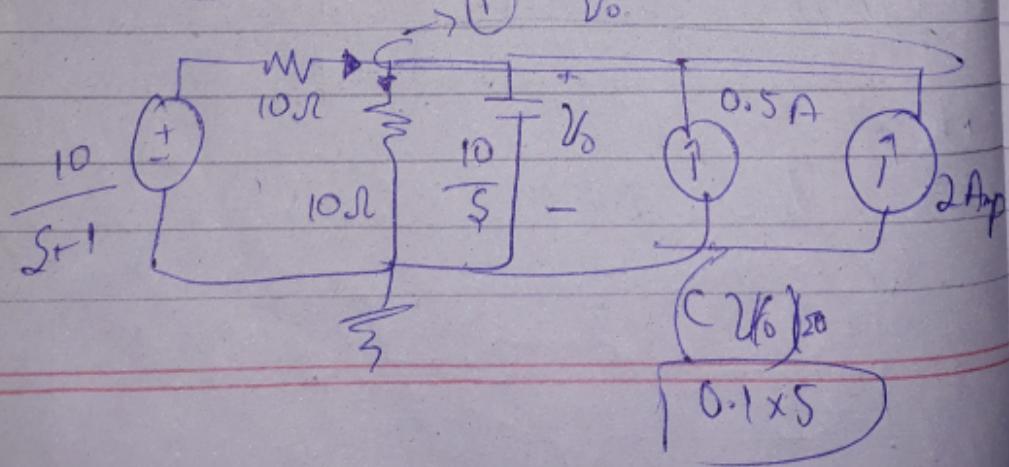
$$\boxed{\frac{\bar{I}(s)}{C} + \frac{V(0)}{s} = V(s)} \rightarrow (c)$$



L Applying KCL at Node ①

$$\frac{10}{s+1} - \frac{V_o}{10} + 0.5 + 2 = \frac{V_o}{10} + \frac{10}{s}$$

$$\frac{10}{s+1} - \frac{V_o}{10} + 0.5 + 2 = \frac{V_o}{10} + \frac{10}{s}$$

$$\frac{1}{s+1} + 0.5 + 2 - \frac{10}{s} = \frac{V_o}{10} + \frac{V_o}{10}$$

$$\frac{1}{s+1} + 2.5 - \frac{10}{s} = \frac{V_o}{5}$$

$$\Rightarrow \frac{s + 2.5s(s+1) - 10(s+1)}{(s+1)s} = \frac{V_o}{5}$$

$$\Rightarrow \frac{s + 2.5s^2 + 2.5s - 10s - 10}{(s+1)s} = \frac{26}{5}$$

$$\Rightarrow \frac{2.5s^2 - 6.5s - 10}{(s+1)s} = \frac{V_o}{5}$$

$$\Rightarrow V_o = \frac{12.5s^2 - 32.5s - 50}{(s+1)s}$$

$$\Rightarrow \frac{5}{2} \left\{ \frac{5s^2 - 13s - 20}{(s+1)s} \right\}$$

\$1700
14 6x82

2844



$$= \frac{5}{2} \left\{ s - \frac{(18s+20)}{s(s+1)} \right\}$$

$$\Rightarrow \frac{5}{2}$$

$$\Rightarrow \frac{5}{2} \left[s - f(n) \right]$$

$$\begin{array}{c} s^2 + s \\ \hline 5s^2 + 13s - 20 \\ - 5s^2 - 5s \\ \hline - 18s - 20 \end{array}$$

$$\Rightarrow \frac{5}{2}$$

$$f(n) = \frac{A}{s} + \frac{B}{s+1}$$

$$\frac{18s+20}{s(s+1)} = A(s+1) + B(s)$$

$$\boxed{18s+20 = A(s+1) + B(s)}$$

when $s = 0$

$$\Rightarrow \frac{5}{2} \left[5 - \left\{ \frac{20}{s} + \frac{2}{s+1} \right\} \right]$$

$$\Rightarrow \frac{5}{2} \left\{ 5 \delta(t) - 20 u(t) - 2e^{-t} u(t) \right\}$$

3S-20

S

S-20

$$\bullet \cancel{\text{If}} \quad \cdot 1 \Rightarrow \delta(t)$$

$$\bullet \frac{1}{s} \Rightarrow u(t)$$

$$\bullet \frac{1}{s+a} \Rightarrow e^{at} u(t)$$

ELECTRICAL NETWORK ANALYSIS

ELECTRIC CIRCUIT

E.M.F

Current

Resistance

$$V = IR$$


MAGNETIC CIRCUIT

M.N.F

magnetic flux

Reluctance

$$\text{mmf} = \Phi R$$

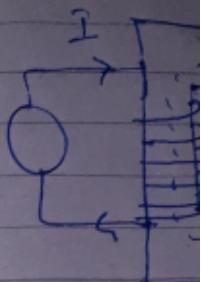


MMF:

Magnetic motive force - It is like emf, mmf is responsible to establish magnetic flux in core.

Mathematically

$$\text{m.m.f} = N \cdot I$$

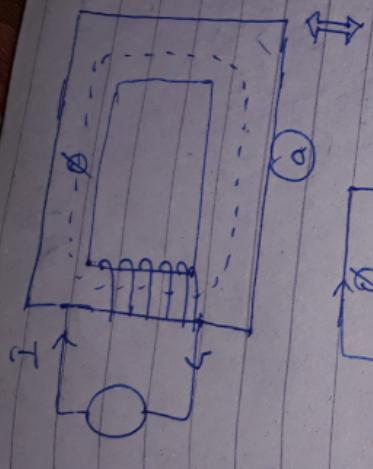where "N" is the number of turns of coils 'I' amount of current (A) - unit of m.m.f is (A.T)
Ampere-Turns -



$\frac{d\phi}{dt} = -\text{ic flux}$
 ence
 ϕR

- Schematic Representation
 of diagram a

It is in terms of ohms law for
 magnetic
 in

$$mmt \cdot \phi n$$

where

ϕ is the magnetic flux
 (web)
 n is Reluctance offered
 in establishment of magnetic
 flux Unit AT/web

$$R = \frac{1}{\mu A}$$

↖
Permeability

$$\int H_0 dL_s$$

$$R_{\text{core}} = \mu_{\text{core}} \cdot C_{\text{core}}$$

$\frac{1}{\mu_0} \cdot \frac{H_0 \cdot L_s}{R_1 + R_2}$

$$\text{magf} = \phi (R_1 + R_2)$$

* Magnetic flux density (B)


$$B = \frac{\Phi}{A} \quad (\text{weber/m}^2)$$

* Magnetic Flux Density (H)

$$H = \frac{\text{mmt}}{L} \quad A \text{ T/m}$$

$$\boxed{B = \mu H}$$

Response of RLC Circuit

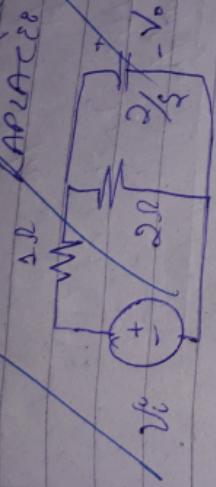

Linear
Saturation

Linear

Saturation

$$R_s \quad H_s \quad Q_s$$

-H

H

B

Coax


Magnetic Flux Density (B)

$$B = \frac{\phi}{A} = \text{wb/m}^2$$

Magnetic Flux Intensity (H):

$$H = \text{mamp}/\text{m}$$

\Rightarrow Magnetically Coupled Circ.

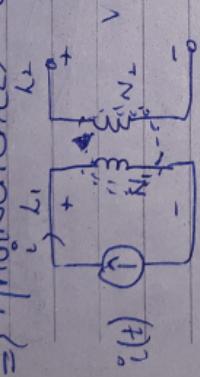

ϕ_{12} "secondary"

ϕ_1 is the

new A/c

$$\therefore V_1 = N_1 \frac{d\phi}{dt}$$

$$\therefore V_1 = k$$

Case I:

Two coils of inductance L_1 & L_2 are placed in close contact, first coil (primary coil) excited with $i(t)$ time varying current causing magnetic flux in primary winding on secondary coil - very in close contact, the flux also energize secondary coil -

ϕ_{11} is magnetic flux due to primary coil present in primary

$$\phi_{11} = \phi_{11} + \phi_{12}$$

(4):

ϕ_{i2} , "Secondary" "secondary coil" "
 ϕ_i is the total magnetic flux.

Now A/C TO FARADAY'S LAW:

$$\therefore V_1 = N_i \frac{d\phi_i}{dt} \text{ if } V_1 = \frac{d\phi_i}{dt} \times \frac{di_1}{dt}$$



$$\text{so } V_1 = L \frac{di_1}{dt} \quad \text{where } L = \frac{N_i \phi_i}{dt}$$

(self Inductance)

$$\therefore V_2 = N_2 \frac{d\phi_{i2}}{dt} \text{ if } V_2 = \frac{d\phi_{i2}}{dt} \times \frac{di_2}{dt}$$

$$\text{so } V_2 = N_2 \frac{di_2}{dt}$$

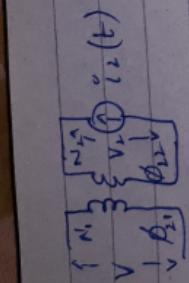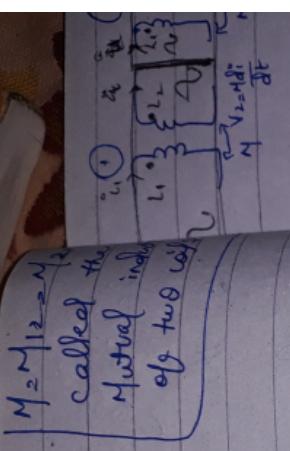(where N_2 is the mutual inductance
in Secondary coil due to primary
coil flux)



Case : \tilde{V}_1 From the fig

$$\text{Circuit coupling}$$

$$N_2 \frac{di_2}{dt} = N_2 \frac{d\phi_{22}}{dt} \quad \text{If } V_2 = N_2 \frac{d\phi_{22}}{dt} \times \frac{di_2}{dt}$$


$$\text{So } V_2 = L_2 \frac{di_2}{dt}$$

$$\therefore V_{12} = N_1 \frac{d\phi_{21}}{dt} \quad \text{If } V_1 = N_1 \frac{d\phi_{21}}{dt} \times \frac{di_2}{dt}$$

$$\text{So } V_1 = N_1 \frac{di_2}{dt}$$

TOTAL INDUCTION:
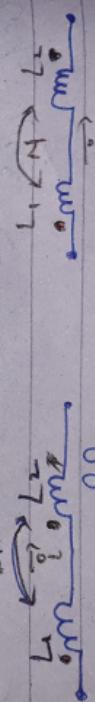
$$L_1 + L_2 = 2M = \text{Total Inductance.}$$




Series adding

$$L_1 + L_2 = -2M = \text{Total Inductance}$$

The
ref induct
two coils

$\frac{di_2}{dt}$

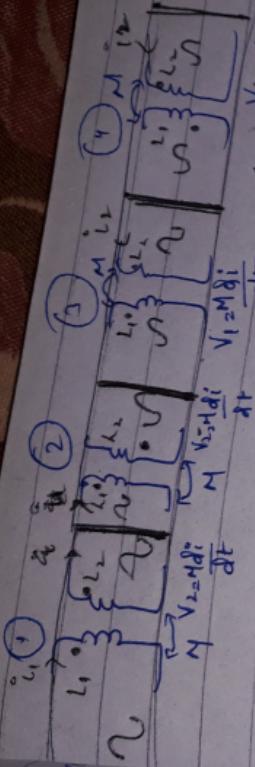

Coupling coefficient K
See it in book clearly

$$M = K \sqrt{L_1 L_2} \quad \text{when } 0 < K < 1$$

if $K < 0.5$ (lose coupled coil)
if $K = 1$ (Perfect coupled coil)
if $K > 0.5$ (tightly coupled coil)

Q: Determine I_1 & I_2

