

Assignment

- ABDUL AZIZ AHMED
- D-19-Es-97
- ECD
- See -A


COLPITTS OSCILLATOR:

• DESIGN:

The Colpitts Oscillator design uses two centre-tapped capacitors in series with a parallel inductor to form its resonance tank circuit producing sinusoidal oscillations.

In many ways the Colpitts oscillator is opposite to Hartley oscillator - the tank circuit consists of an LC sub-circuit connected with the input (base) & the output (collector) terminals - thereby producing a sinusoidal output waveform.

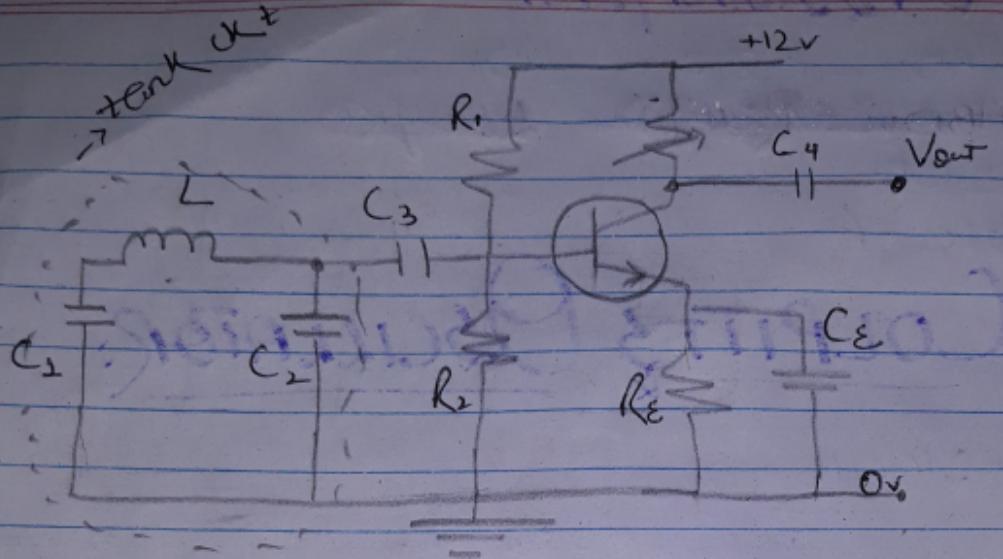- can be made by a transistor or by an op-amp -



C E configuration:

Working:

The emitter terminal of the transistor is effectively one connected with the capacitor C_1 & C_2 which are in series. C_E makes a voltage divider arrangement. When the power supply is firstly applied through the capacitor's E_F charged up E_F then simply discharge through the coil L . This will produce oscillations in the base E_F amplified at the collector terminal.

The frequency of oscillations for a Colpitts oscillator is determined by the resonant frequency of the LC tank ckt & is given as-

$$f_r = \frac{1}{2\pi\sqrt{LC_T}}$$

$$\therefore C_T = \frac{1}{C_1} + \frac{1}{C_2}$$

With NO PHASE SHIFT


The configuration of the transistor amplifier is of a Common Emitter Amplifier with the output signal 180° out of phase

w.r.t the input signal. The additional $+180^\circ$ phase is obtained by a tank ckt (two capacitors in series & one inductor in parallel). produces overall phase shift of the ckt being zero or 360°

Ans

RC Oscillator Circuit:

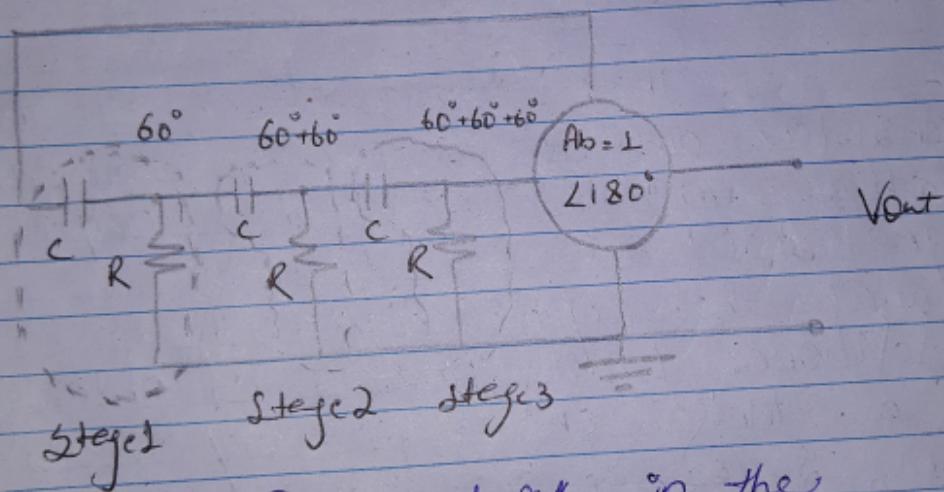
RC oscillator's use a combination of an RC network to produce oscillations due to the phase shift between the stages.



The RC network in the first stage produces a phase shift of 90° ideally. But practically less than 90° . In this RC circuit output voltage leads the input by some angle θ . For making a phase shift of 180° for oscillations at least two single-poles must be used in RC

oscillator design-

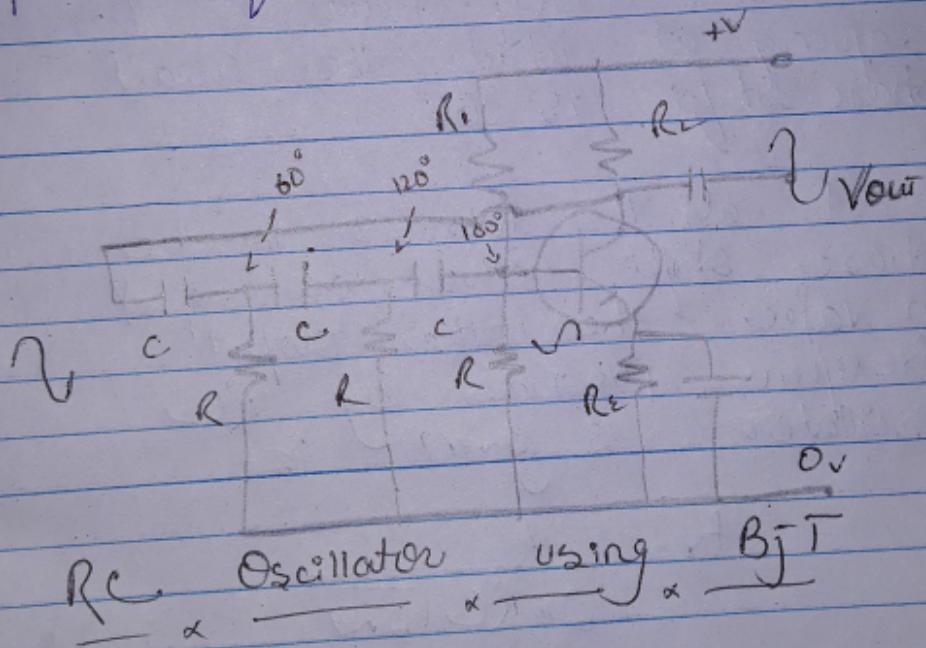In reality you have to cascade 3 phase RC to attain 180° phase. Then by connecting these RC networks in series a chosen frequency & this forms the basis of "phase shift oscillator"-




The basic RC oscillator also known as phase-shift oscillator produces a sine wave output signal using regenerator feedback obtained from the resistor-capacitor combination-

O_c

The resistor-capacitor feedback network can be connected as shown above to produce a leading phase shift or interchanged to produce a lagging phase shift but the outcome is still the same as the sine wave oscillations only occur at the frequency at which the overall phase-shift is 360°

60°

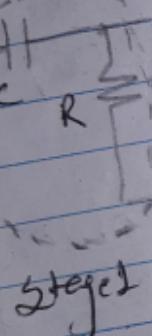

If all the R's, C's in the phase shift network are equal in value - then the output frequency produced by RC oscillator is given as -

$$f_{rc} = \frac{1}{2\pi RC \sqrt{2N}}$$

N = no of RC stages (3) -

For 180° we can also design RC oscillator using an op-amp.

Sing