

Image

AFTER MID^o


P.P


OPERATIONAL AMP:

INTRODUCTION:


An op-Amp is very ^{high} gain differential Amplifier with high input impedance & low output impedance. Op-Amp is used to provide voltage, amplitude changes (amplitude, polarity, oscillators, filters circuits & many type of instrumentation etc.) An op-Amp contains no of differential amplifier stages to achieve very high voltage gain.

Construction:

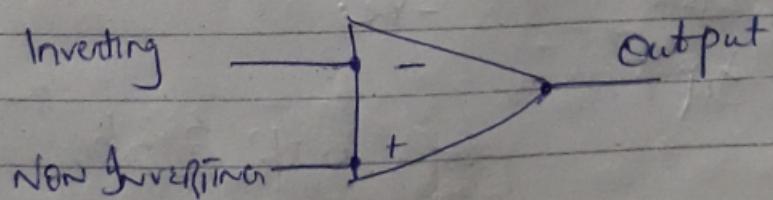


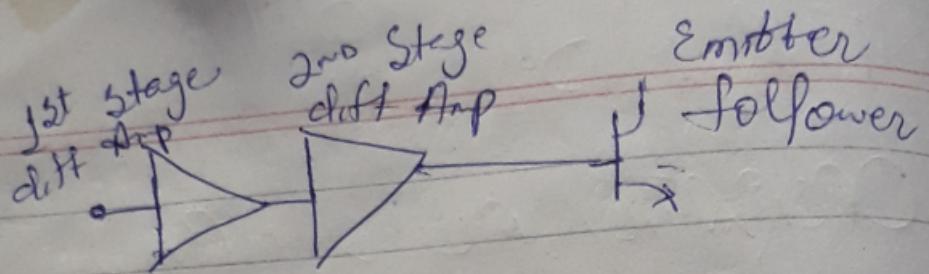


Op-Amp:

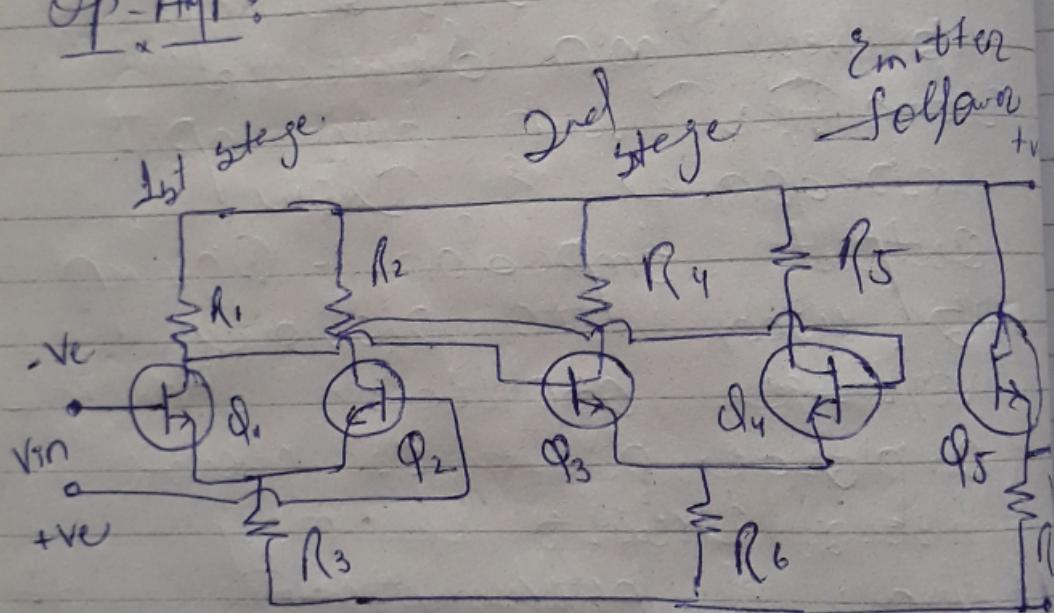

double stage diff .amp

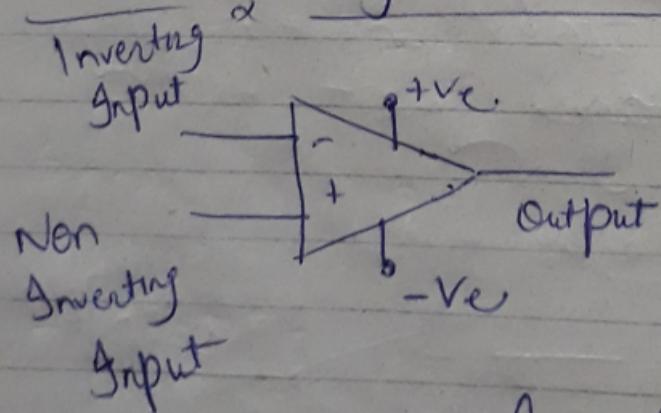

op Amp symbol

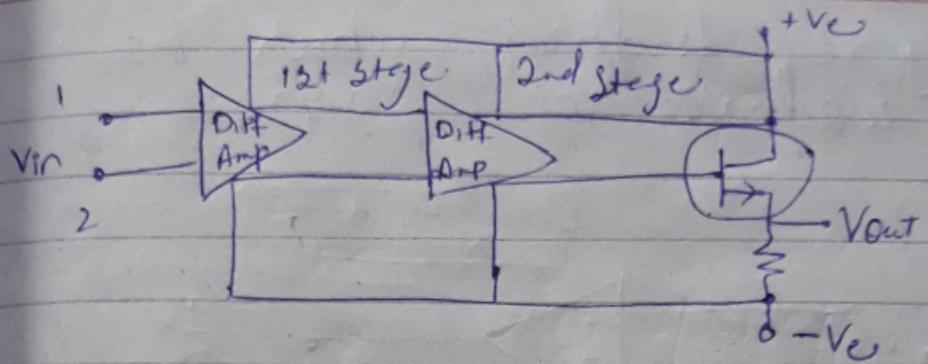


Negative Feedback in An OP-Amp

Almost all op-Amp ckt's includes negative feedback from the output to the inverting input through resistor or capacitor - without negative feedback an op-amp would have very little practical use.


NOTE:

An open loop op-Amp ckt has no-negative feedback & extremely high gain - In close loop op-Amp ckt has

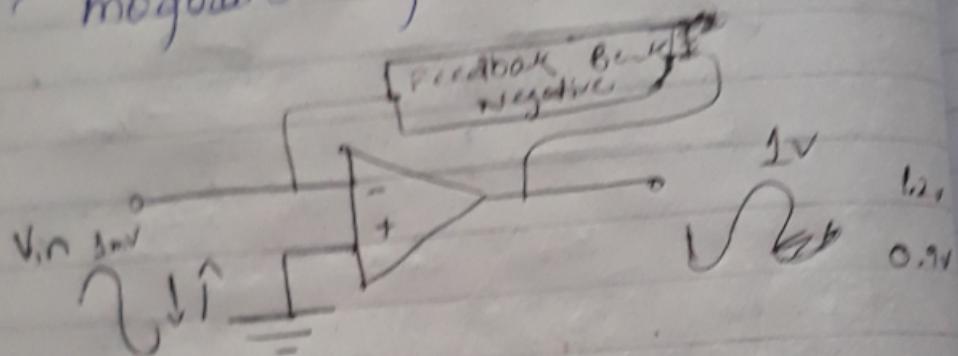negative feedback which has moderate value gain.



Inverting Amps

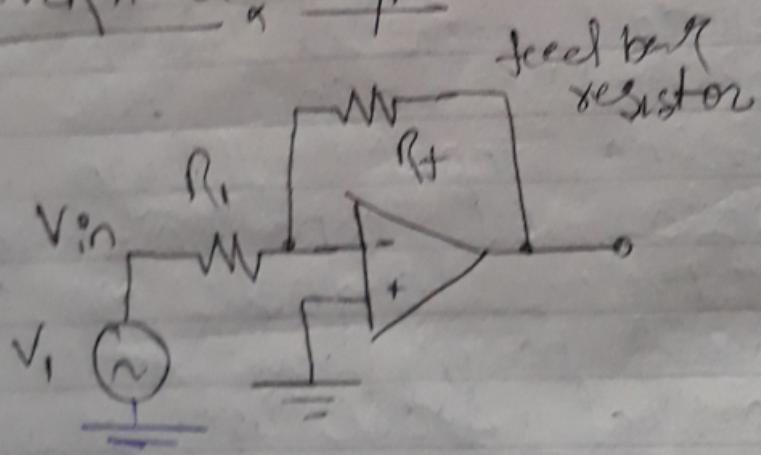

Signal V_s is applied through resistor R_2 to the (-) input.

The output is then connected back to the same

(-) Minus input through Resistor R_f . The (+) input is connected to the ground. The output appear 180° out of phase with the input.

It is widely used constant gain multiplier ckt. The output is obtained by multiplying the input by the fixed or constant gain, set by the input Resistor R_i & feedback resistor R_f . The output is also being inverted from the input. Mathematically it is represented as:

$$V_o = -\left(\frac{R_f}{R_i}\right) V_i$$

$$\boxed{A_v = -\frac{R_f}{R_i}}$$

Prob:


$$R_1 = 100k, R_f = 500k, V_i = 2V$$

$$V_o = ?$$

$$\boxed{V_o = -10V}$$

$$\begin{array}{c} -10V \\ \curvearrowleft \end{array}$$

• Unity Follower:

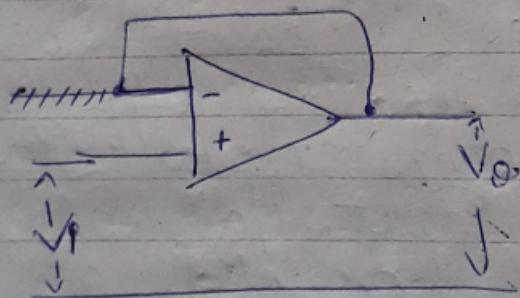


$$\boxed{V_o = V_i}$$

The unity-follower ckt as shown in fig provides gain of unity(1) with no polarity or phase reversal.

The output is the same polarity & magnitude as the input.

SUMMING AMPLIFIER:

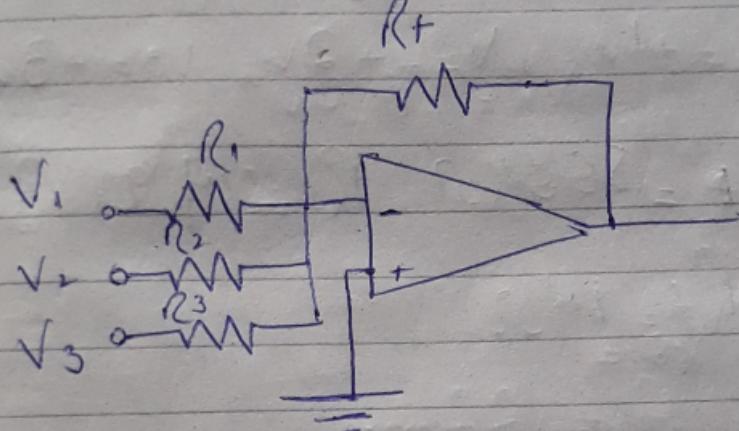

$$V_o = - \left[\frac{R_f}{R_1} V_1 + \frac{R_f}{R_2} V_2 + \frac{R_f}{R_3} V_3 \right]$$

The circuit shown in fig is a three input summing amplifier which provides algebraically (adding) summing of three voltages.

Rrob:

calculate the output voltage
of an op-Amp summing
Amp for the following
sets of voltages & Resistors

$$V_1 = +1V, V_2 = +2V, V_3 = +3V$$

$$R_f = 500k\Omega, R_1 = 1M\Omega, R_3 = 1M\Omega$$


$$R_f = 1M\Omega$$

$$V_o = - \left[\frac{R_f}{R_1} V_1 + \frac{R_f}{R_2} V_2 + \frac{R_f}{R_3} V_3 \right]$$

$$\boxed{V_o = -7V}$$

MULTI STAGE GAIN

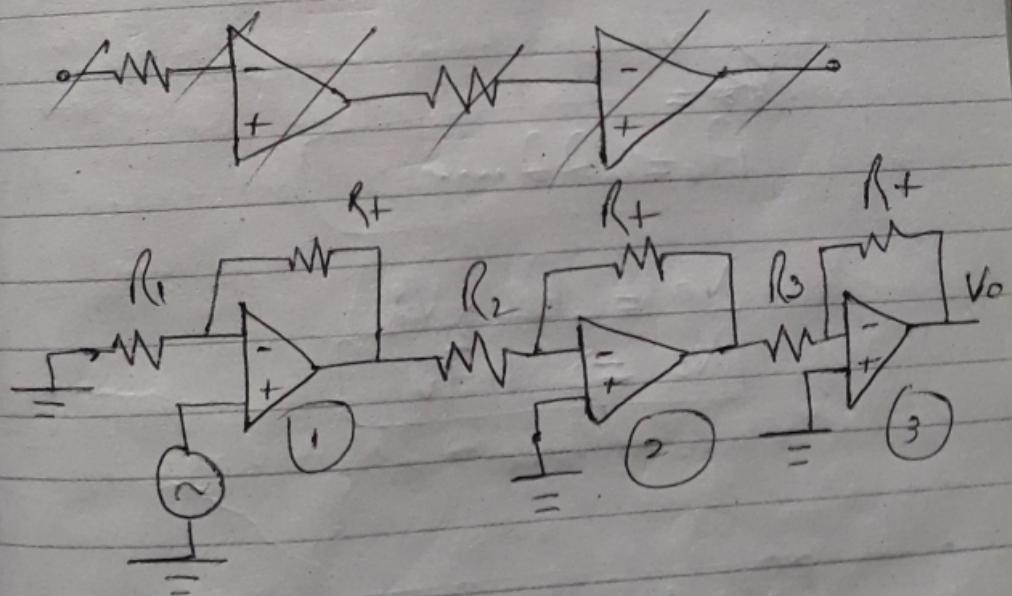when a no of stages are connected in series, the overall gain is the product of the individual stage gain.



$$A = A_1 \cdot A_2 \cdot A_3$$
$$A = \left(\frac{R_f + 1}{R_1} \right) \left(\frac{-R_1}{R_2} \right) \left(\frac{-R_2}{R_3} \right)$$

Ques:

calculate the o/p voltage
using the ckt shown in
(Fig - i) for resistor components

$$R_f = 470 \text{ k}\Omega, R_i = 4.3 \text{ k}\Omega$$
$$R_2 = 33 \text{ k}\Omega \text{ & } R_3 = 33 \text{ k}\Omega$$

$$V_i = 80 \text{ mV}$$

Multistage chain- $V_o = ?$

$$\frac{A_o}{A_v} = 22 \dots$$

$$V_o = A_v \times V_i$$

$$V_o \Rightarrow 1.7 \text{ V}$$

One stage

$$V_{o1} = \left(\frac{R_f}{R_i} + 1 \right) \times V_i$$
$$= 8.8 \text{ mV}$$

R_f & R_i

$$10 = 1 + \frac{R_f}{R_i}$$

$$\left(1 + \frac{R_f}{R_i}\right) = 10$$

Fig: i) Show the connection of an LM-124 quad op-amp as a three stage amplifier with gain of $\frac{+10}{+18}$ & -27 . Use 270K ^{Feedback} resistor for all three ckt's what o/p voltage will result for an o/p input of 50mV.

$$\boxed{V_o = A_1 \times A_2 \times A_3 \times V_i}$$

$$A_1 = 1 + \frac{R_f}{R_i}$$

$$\therefore \boxed{R_i = 30K\Omega}$$

$$A_2 = -\frac{R_f}{R_2}$$


$$\therefore \boxed{R_2 = 15K\Omega}$$

$$\therefore \boxed{R_3 = 10K\Omega}$$

Google scholar
Smart circuit

$$\therefore V_o = 0.729V$$

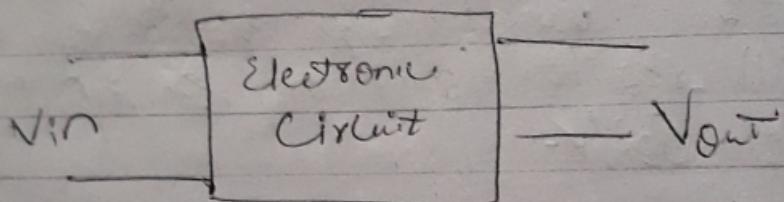
$\times \quad \alpha \quad \alpha \quad \alpha \quad \alpha$



Design Electronic ckt that produce the derive output for given input voltages-

$$V_{in} = [V_1, V_2, V_3]$$

$$V_{out} = [3V_1 - 2V_2 + V_3]$$

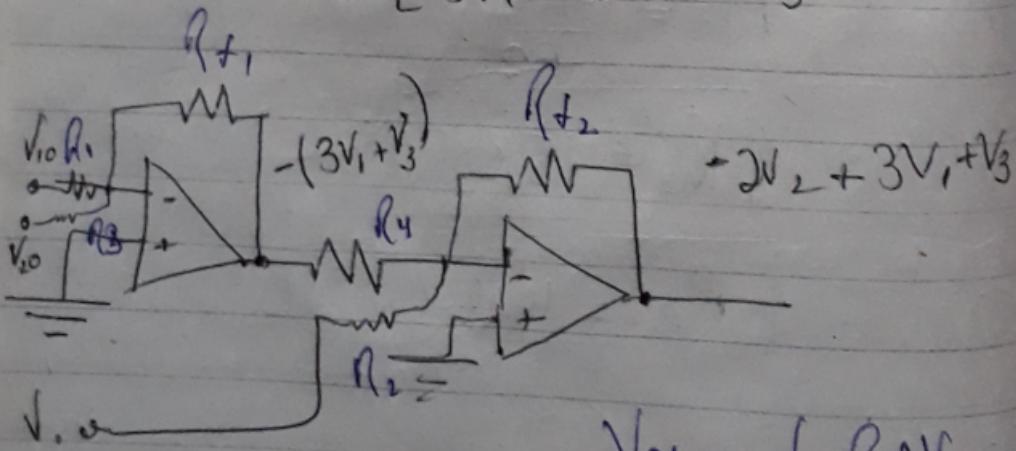

$$V_{o2} = -\left(\frac{R_f V_1 + R_5}{R_1}\right)$$

$$\left(\frac{-R_f}{R_i} \right) + \left(1 + \frac{R_f}{R_i} \right) + \left(1 + \frac{R_f}{R_o} \right)$$

$$-2V_2 = (3V_1) \cdot (V_3)$$

$$R_f = 10k\Omega, R_i = 3.3k\Omega, R_o = 10k\Omega$$

$$V_{O2} = - (3V_1 + V_2)$$


$$R_{f2} = 10k\Omega$$

$$R_{f2} = 2$$

$$\frac{R_{f2}}{R_4} = R_{f2} = 10k\Omega$$


$$R_2 = 5k\Omega$$

$$V_{O2} = -2V_2 + 3V_1 + V_3$$

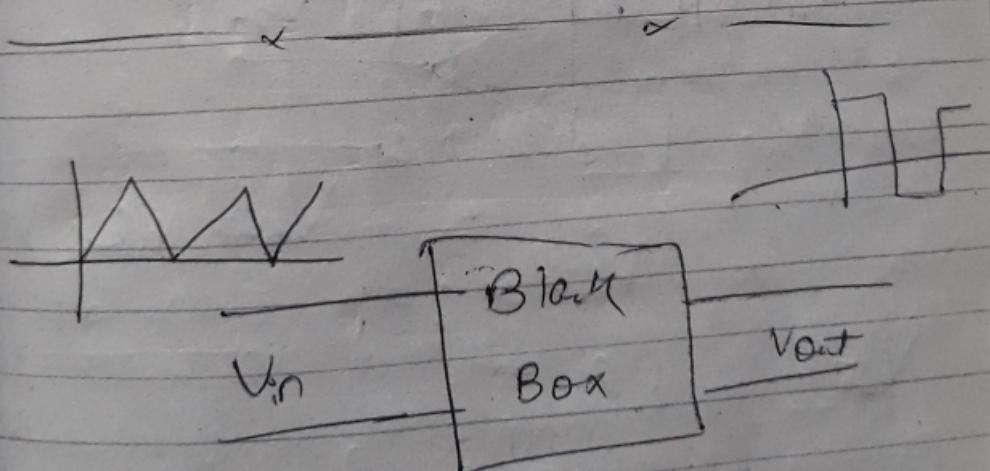

Op-Amp:

COMPARATOR:

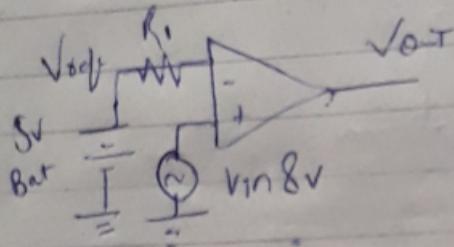

Application:


convert b/w



DIF:

Remember that an op-amp is made of differential amp. & the open-loop gain is extremely high - if the voltage diff \sim b/w the two inputs is more than few millivolts, the output swings into saturation at ± 15 or the other of two power supply voltage.


The inverting input is grounded.




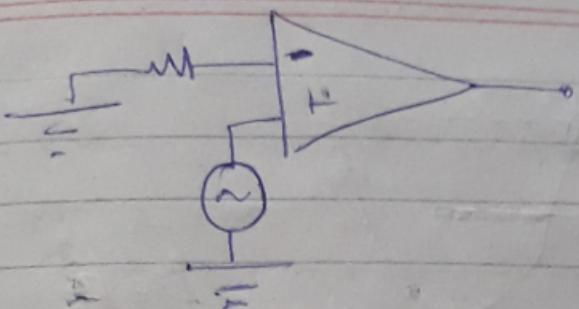


This is shown in Fig(1). Then the signal on the non-inverting input swings slightly positive, the output goes all the way to the value of the positive power supply. When the signal swings slightly negative, the output goes to the value of negative supply voltage.

NOTE:

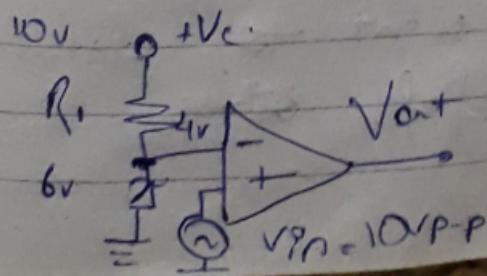Thus the o/p changes value when the input crosses 0-



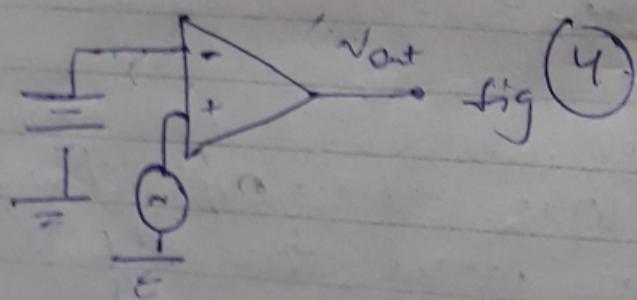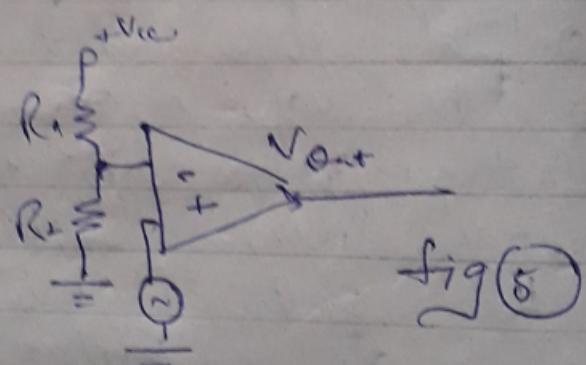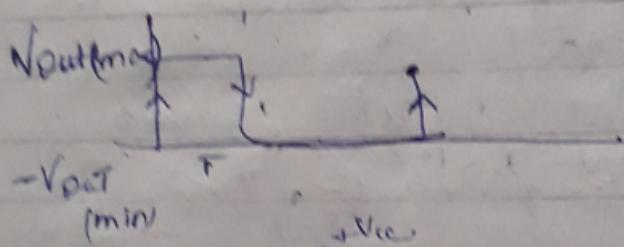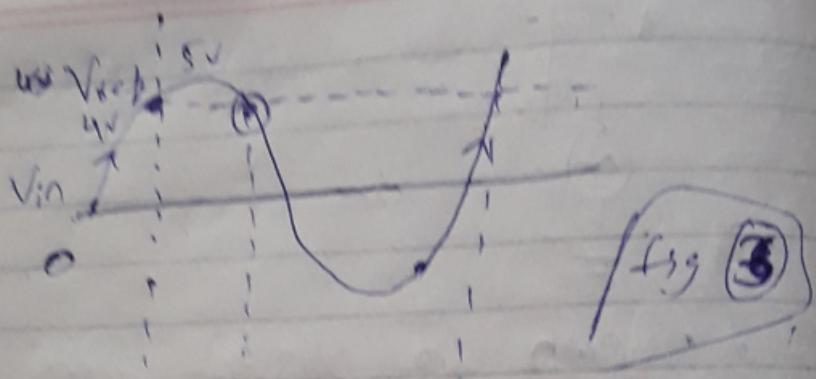


If you want to detect
a voltage for other

$$V_{ref} = \left(\frac{R_2}{R_1+R_2} \right) V_{cc}$$


$$\Rightarrow \left(\frac{20k}{36k+20k} \right) 10$$

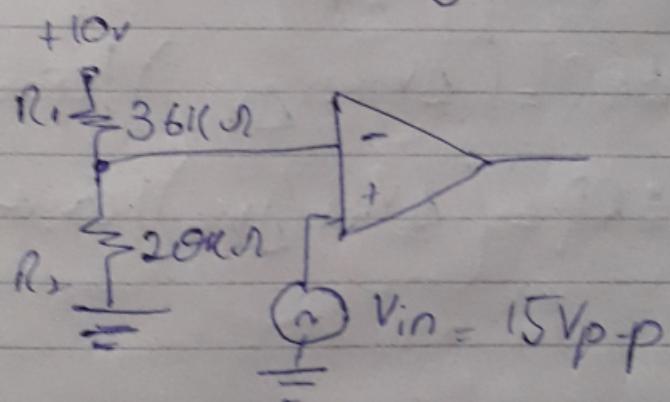than $3.5V$, all we have to do is to establish a reference voltage on the inverting input as shown in fig ②, ③, ④ - when the input crosses the reference value the output swing as shown in fig ③.



$$V_{ref} = \left(\frac{R_2}{R_1+R_2} \right) \times 10$$



$$V_{ref} = 3.5V$$

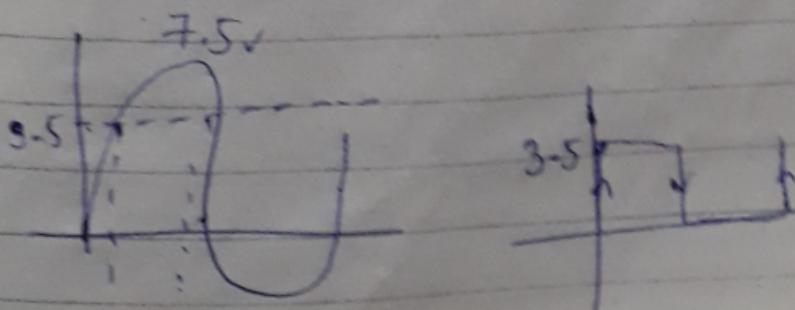

Thermistor \rightarrow Temp sensor

Comparators (Application)

\Rightarrow Temp sensor (CT)

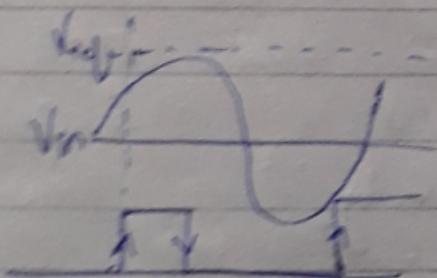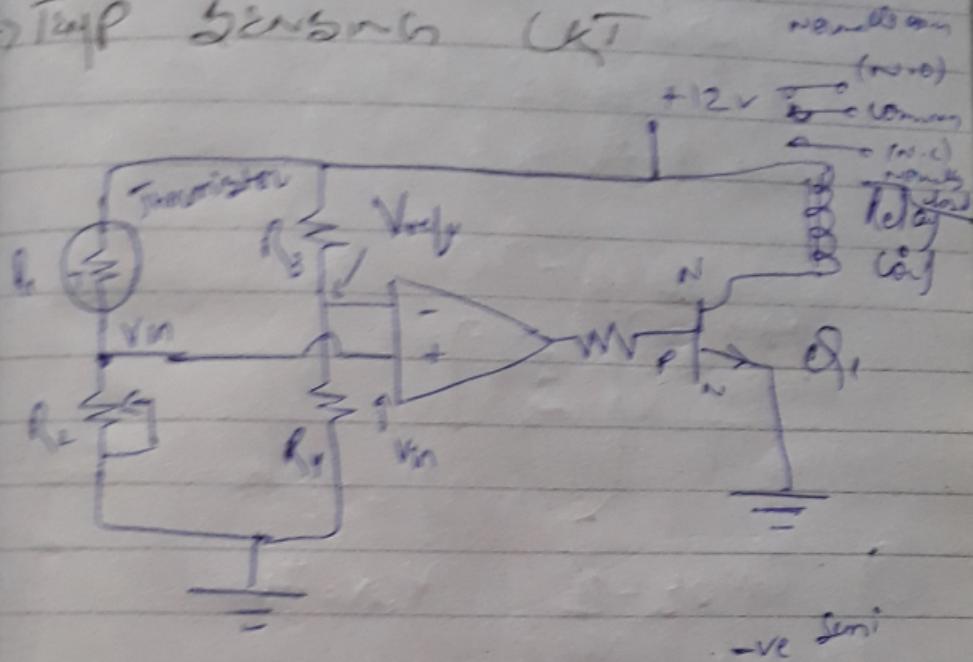


Temp ↑
Resist ↓
Conduct ↑

Saturation:
C-Switch

⑩ Case-I

$V_{in} = 5V$

Temp ↓
Resistance ↑
conductivity ↓

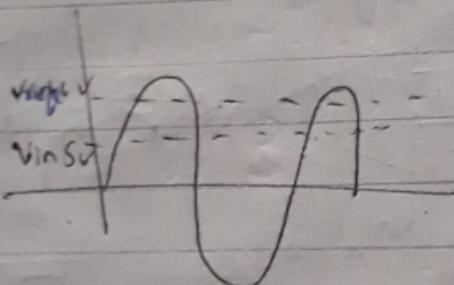


⑪

Case-II


$V_{in} = 7V$

Temp ↑
Resistance ↓
conductivity ↑

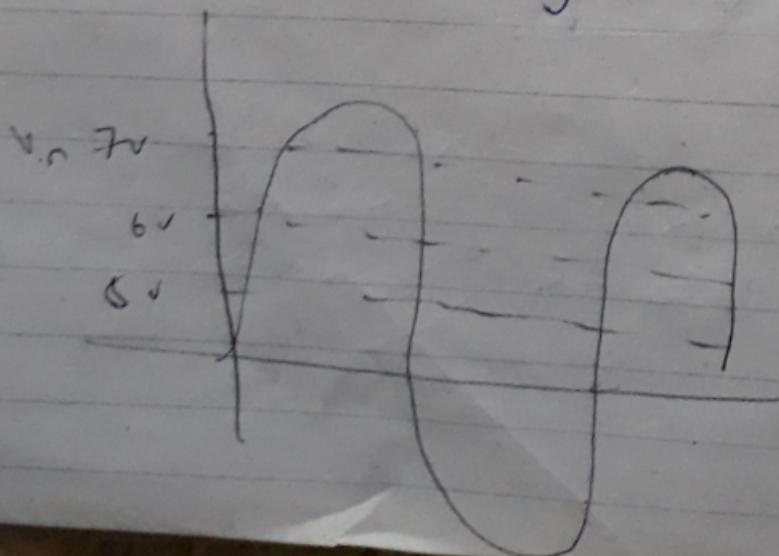


$$-\frac{R_f}{R_1} V_1 - \frac{R_f + R_1 - R_2}{R_3} \frac{V_2}{R_2}$$

$$-V_o /$$

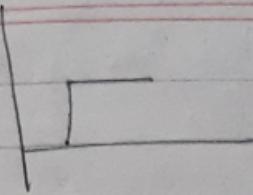

VOLTAGE SUBTRACTION:

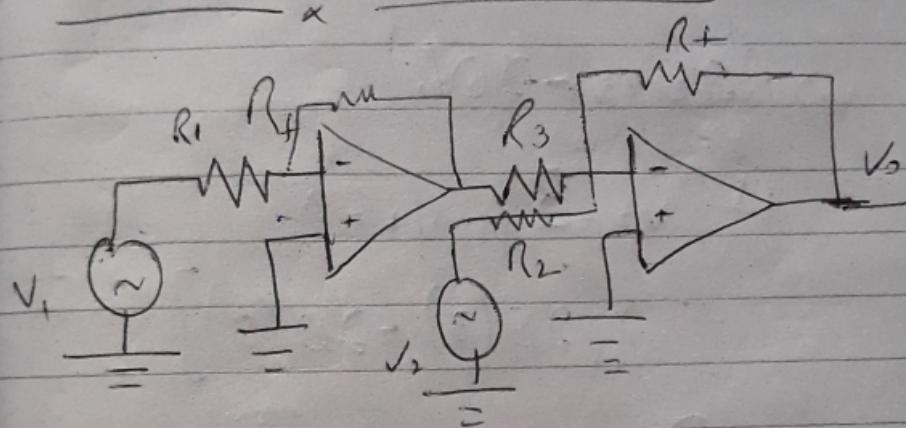

$$V_o = -\frac{R_f}{R_3} \left(-\frac{R_f \cdot V_1}{R_1} \right) + \frac{R_f}{R_2} V_2$$

$$\Rightarrow -\left[\frac{-R_f V_2}{R_2} - \frac{R_f}{R_3} \frac{R_f}{R_1} V_1 \right]$$

Determine the ~~com~~ value of V_o
with the components:

$$R_2 = 50 \text{ k}\Omega$$

$$R_1 = 100 \text{ k}\Omega$$

$$R_3 = 500 \text{ k}\Omega$$

$$V_o = ?$$

$$R_f = 1 \text{ M}\Omega$$

$$\Rightarrow \left(\frac{R_F}{R_2} V_2 - \frac{R_F}{R_2} \times \frac{R_F V_1}{R_1} \right)$$

$$\Rightarrow \left(\frac{1 \times 10^6}{50k} V_2 - \frac{1M \Omega}{500k} \times \frac{1M \Omega}{100k} V_1 \right)$$

$$\Rightarrow (20V_2 - 20V_1)$$

If $V_2 = 3$, $V_1 = 5$


$$\Rightarrow [20(3) - 20(5)]$$

Settling Rate:

If we apply square wave at the input of op-amp. at the rising edge settling transition of the square wave the voltage changes infinitely fast & they are fast op-amp can't change rapidly.

Result:

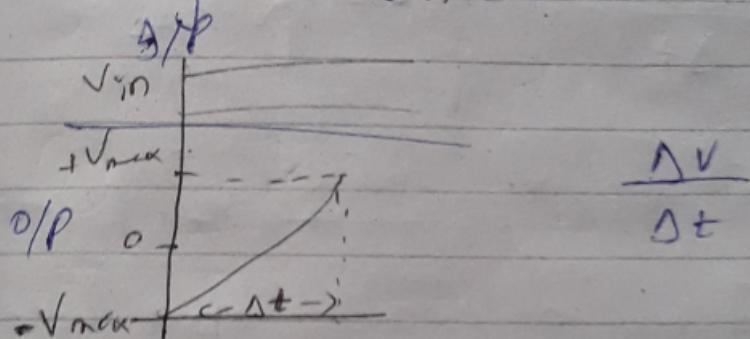There should be slightly non-vertical slope produced on the O/P. This can be measured by Slew rate - (change in voltage over the change in time)



Prob: The output of an op-amp changes from $2.5v$ to $12.3v$ in a time of $2.8ms$.
Find slew rate.

$$= \frac{\Delta V}{\Delta t} = 3.5 \times 10^6$$
$$= 3.5v/\mu\text{sec}$$

REPEAT. PROBLEM:

$$V_1 = 1.3\text{V}$$


$$V_2 = 6.9\text{V}$$

$$\Delta t = 3.1 \mu\text{sec}$$

$$\frac{\Delta V}{\Delta t} \Rightarrow 1.80 \text{V}/\mu\text{sec}$$

DIFFERENTIAL GAIN:

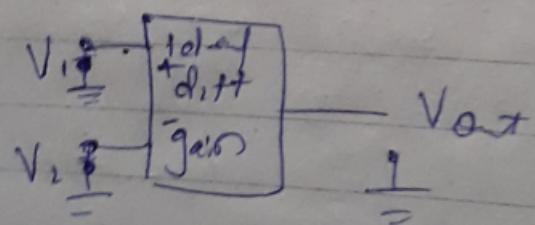A_{iv} \Rightarrow differential input gain



The V_1 & V_2 are the two inputs while V_{out} is the single ended output. Each signal is measured w.r.t ground. In an ideal diff amplifier, the output voltage is

proportional to the difference between the two input signals.

This means we can write

$$V_{out} = A_{id}(V_1 - V_2) \quad A_{id} \text{ is the}$$

gain with which diff amp amplifies the difference b/w the two input signals. Hence

It is called differential gain of the differential amplifier so A_{id} = differential gain

$$V_{id} = (V_1 - V_2) = \text{diff in voltage in } \text{V/p.v}$$

$$\boxed{V_{out} = A_{id} V_{id}}$$

$$\boxed{A_{id} = \frac{V_{out}}{V_{id}}}$$

Generally it is expressed in dB

$$\boxed{A_{id} = 20 \log(A_{id}) \text{ in dB}}$$

COMMON MODE GAIN

|

If we apply two input voltages which are equal in all the respect to the differential amp - that is $V_1 = V_2$ then ideally o/p voltage

$$V_{out} = (V_1 - V_2) A_{od} \text{ must be zero}$$

It's not only depends on the diff voltage but also depends on the average common lvl of two inputs. Such average lvl of the two input signals is called

common mode signal Σ is
denoted by V_{cm}

$$V_{cm} = \frac{V_1 + V_2}{2} \quad V_{out} = A_{cm} V_{cm}$$

$$A_{cm} = \frac{V_{out}}{V_{cm}}$$

The output not practically zero
due to the mismatched
of the internal ckt

Common Mode Rejection Ratio (CMRR):

when the same voltage is
applied to both the inputs,
the differential amp is set to
be operated in common
mode configuration - Many
disturbance signals, noise signals
appear as common input
signals to both the input
terminal of the differential

Q1. The ability of differential
amp is to reject common
mode signal & express
by ratio called common
mode rejection ratio - CMRR
is denoted by CMRR &
mathematically


$$CMRR = \frac{A_{id}}{A_{cm}}$$

$$CMRR \text{ in db} = 20 \log \left(\frac{A_{id}}{A_{cm}} \right)$$

c/p voltage can be expressed
as in terms of CMRR

$$V_{out} = A_{id} V_{in} + A_{cm} V_{cm}$$

PROB

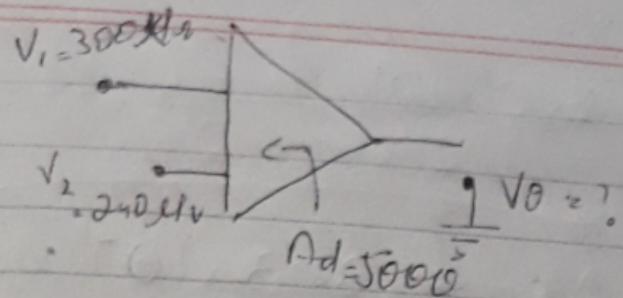

$$V_{out} = A_d(V_1 - V_2)$$

$$\Rightarrow \text{CMRR}$$

$$(i) 100$$

$$(ii) 10^5$$

Determine the output voltage of diff amp for the input voltages of 300mV & 240mV. The diff gain of an amp is 5000 & the value of CMRR is 100 & 10^5 respectively:

$$V_{cm} = 2.7 \times 10^{-4}$$

$$V_{out} = A_d(V_1 - V_2) + A_{cm}V_{cm}$$

$$\Rightarrow (5000)(V_1 - V_2) + A_{cm}\left(\frac{V_1 + V_2}{2}\right)$$

$$V_{id} = 60 \times 10^{-6}$$

$$\text{CMRR} = \frac{5000}{A_{cm}} \Rightarrow 5$$

$$A_m = 8.0 \times 10^1$$


$$N_{ow} \approx 3.13 \times 10^{-1} v$$

$$V_{out} = 313 \text{ mV}$$

why) \rightarrow (or) Page

Ay

Digital To Analog Converter:

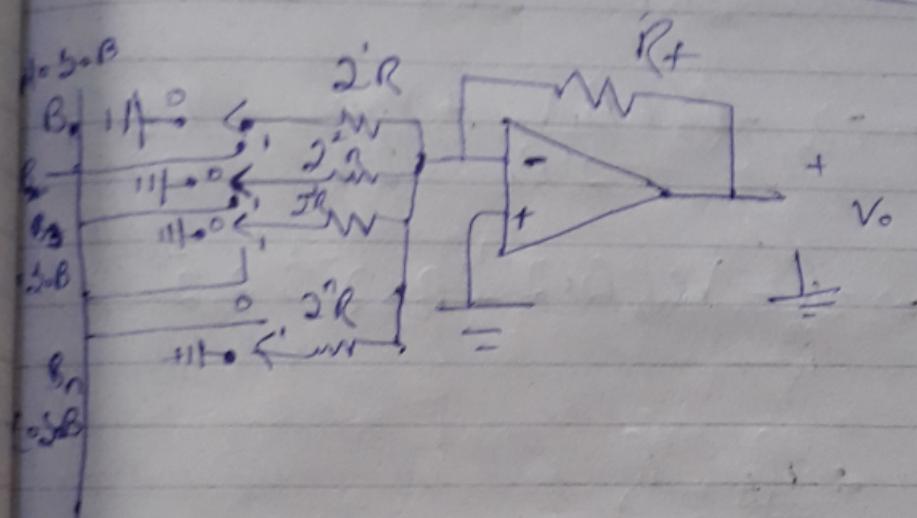

It consists of parallel binary weighted resistor

BINARY WEIGHTED RESISTOR(DAC)

Binary weighted Resistor (Bank)
is a feedback resistor R_f .
The switch position decided
the binary word [i.e. $B_1, B_2 \& B_3$]

ΔR

$$\Rightarrow \left(\frac{-R + B_1}{2^1 R_1} + \frac{-R + B_2}{2^2 R_2} + \frac{-R + B_3}{2^3 R_3} \right) \text{ } \boxed{1}$$

$$V_o \Rightarrow -R + \left(\frac{B_1 V_R}{2^1 R_1} + \frac{V_R B_2}{2^2 R_2} + \frac{V_R B_3}{2^3 R_3} \right)$$

$$V_o \Rightarrow -\frac{R + V_R}{R} \left(B_1 2^{-1} + B_2 2^{-2} + B_3 2^{-3} + \dots \right)$$

$$\therefore R_f = R$$

$$\Rightarrow -V_R \left[B_1 2^{-1} + B_2 2^{-2} + B_3 2^{-3} + \dots \right]$$

$$B_1 = 0, B_2 = 0, B_3 = 1$$

$$\Rightarrow -V_R \left[0 \times 2^{-1} + 0 \times 2^{-2} + 1 \times 2^{-3} \right]$$

$$\boxed{V_o \Rightarrow -\frac{V_R}{8}}$$


$$\begin{aligned}
 & \frac{VR}{4} + \frac{VR}{8} = \frac{3VR}{8} \\
 & \frac{VR}{4} + \frac{VR}{8} + \frac{VR}{8} = \frac{5VR}{8} \\
 & \frac{5VR}{8} = \frac{3VR}{8}
 \end{aligned}$$

Analog o/p

DIGITAL INPUTS \Rightarrow

$B_1 \ B_2 \ B_3$



0 0 0	$\rightarrow 0$
0 0 1	$\rightarrow -\frac{VR}{8}$
0 1 0	$\rightarrow -\frac{VR}{4}$
0 1 1	$\rightarrow -\frac{3VR}{8}$
1 0 0	$\rightarrow -\frac{VR}{2}$
1 0 1	$\rightarrow -\frac{5VR}{8}$
1 1 0	$\rightarrow -\frac{3VR}{4}$
1 1 1	$\rightarrow -\frac{7VR}{8}$

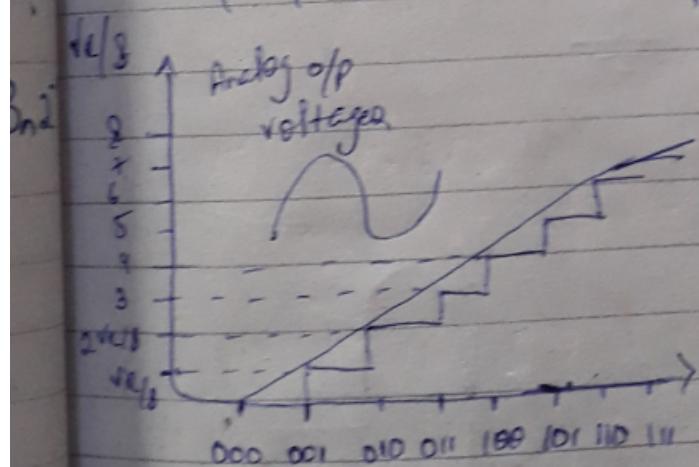


Digitized inputs
code

OP-AMP BASED CLIPPER



Negative CLIPPER

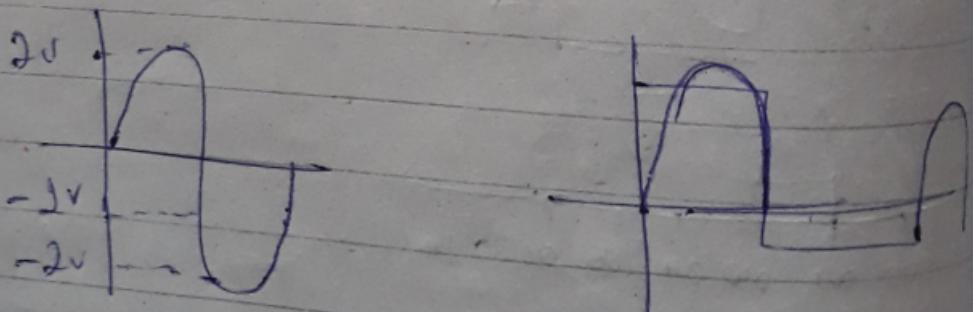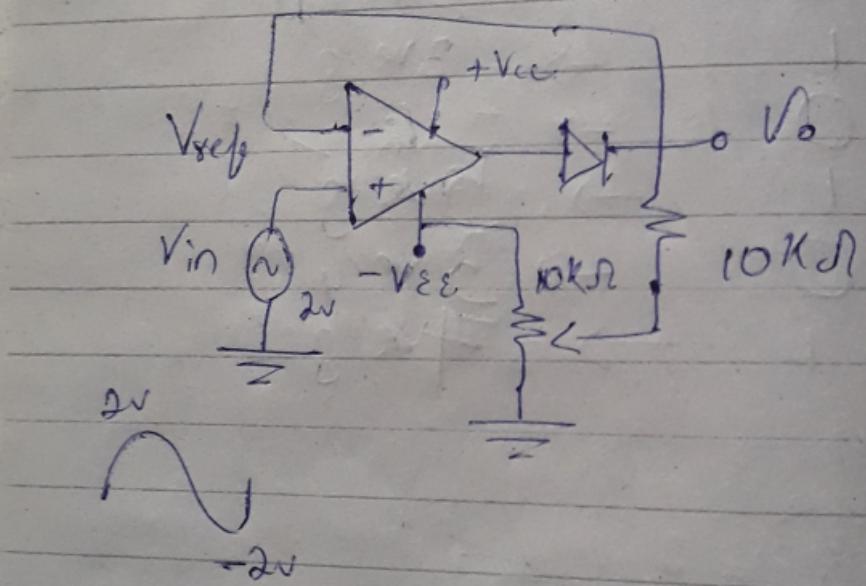

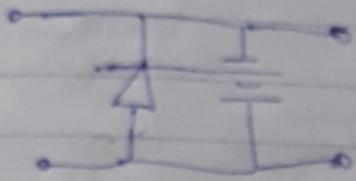

ha


Positive Clipper:

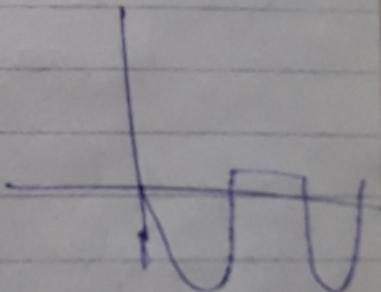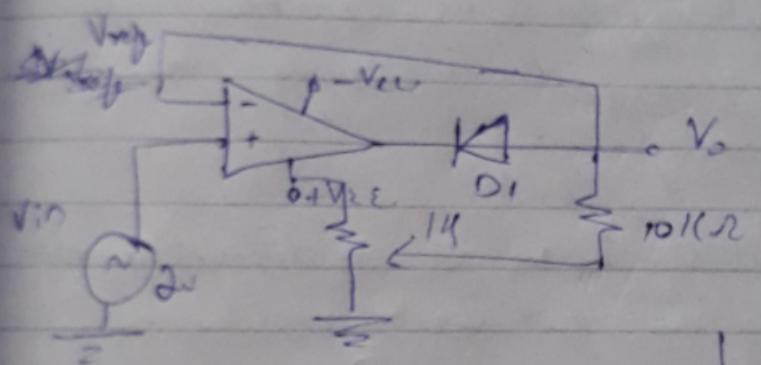

DAC

→ Resolution:

LSB

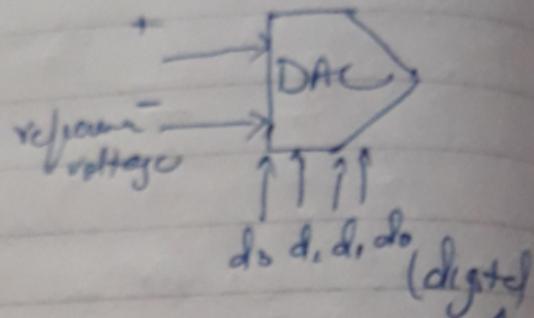

Resolution of DAC can be defined in following two ways:

i) Resolution is the no of different analog voltage value that can be provided by DAC for an n-bit DAC.

$$\text{Resolution} = 2^n$$

Hence the resolution of 4-bit DAC is $2^4 = 16$

4-bit DAC is $2^3 = 8$

Therefore resolution increases with increase in no of bits.

ii) Resolution is defined as the ratio of change in analog output voltage resulting from a change of LSB with

$$\text{Resolution} = \frac{V_{FS}}{2^n}$$

$\frac{1}{15} = 1/3$

V_{FS} = Full scale voltage.

n = number of digital inputs.

Prob: A 4bit DAC has an o/p voltage range 0-5v - calculate its resolution using the definition of resolution.

- Resolution = $\frac{V_{FS}}{2^n} \Rightarrow \frac{5}{15} = 0.33$ v

Thus an input change of one L.S.B causes the output to change by 0.33v


• THRESHOLD:

The min voltage required to turn the transistor is called threshold voltage.


• SCHMITT TRIGGER:

The Schmitt trigger

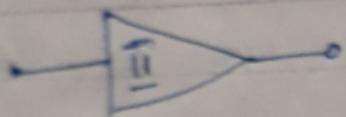is logic input type that prend
threshold voltage for rising &
falling edge. This is useful
bcz it can avoid the error's
when we have noisy input
signals from which we want
to get square wave signal



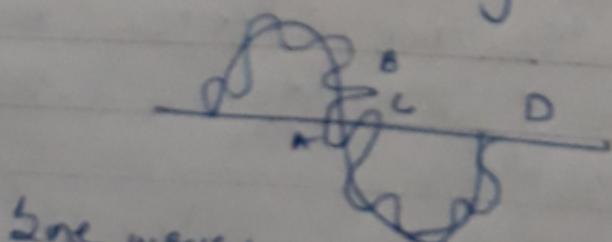
The Schmitt trigger comparator
has two voltage reference called
the upper threshold point (UTP) &
lower threshold point (LTP). bcz the
comparator is so sensitive any noise
in the signal can cause false detection
as shown in the fig:



Square wave
distorted by noise.

The True sine wave crosses zero volt at point D.
 however the noise voltages cause the waveform to cross zero at point A B C - The comparator will detect all three crossings but only one crossing should be counted.

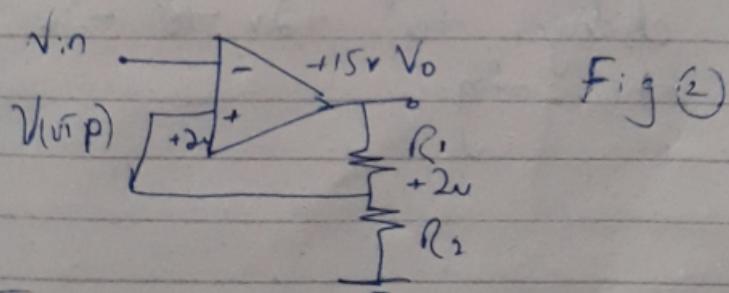The sol to the problem is to give the comparator two reference levels called the threshold points.
 for a zero but the UTP of the positive voltage but if the LTP is a negative voltage but-



In fig 1 The input voltage begins to swing the, nothing happen until the input voltage reach to +2u value of (UTP)-
 The comparator detect this crossing

If the output switches to +ve
-ve voltage -15v - by the output
switches to -ve value the
feedback loop places a negative
ref. voltage of -2v on the
non inverting input equals to the
voltage drop at R_2 , this charge
the ref. voltage fed off the
capacitor.

The input signal. If there
is no signal cause the input to
less slightly from V_{DD} above or
below $+2v$ it will not effect
the output by the ref. but
has change to $+2v$ to $-2v$ shown
in the fig:

